

Süsteemide diagnostika

2. Teoreetilised alused


2.1. Boole'i differentsiaalalgebra

- Boole'i funktsioonide differentseerimine
- Boole'i differentsiaalvõrrandid

2.2. Binaarsed otsustusdiagrammid (BDD)

2.3. Kõrgtasandi otsustusdiagrammid

Introduction to Theories: The Course Map

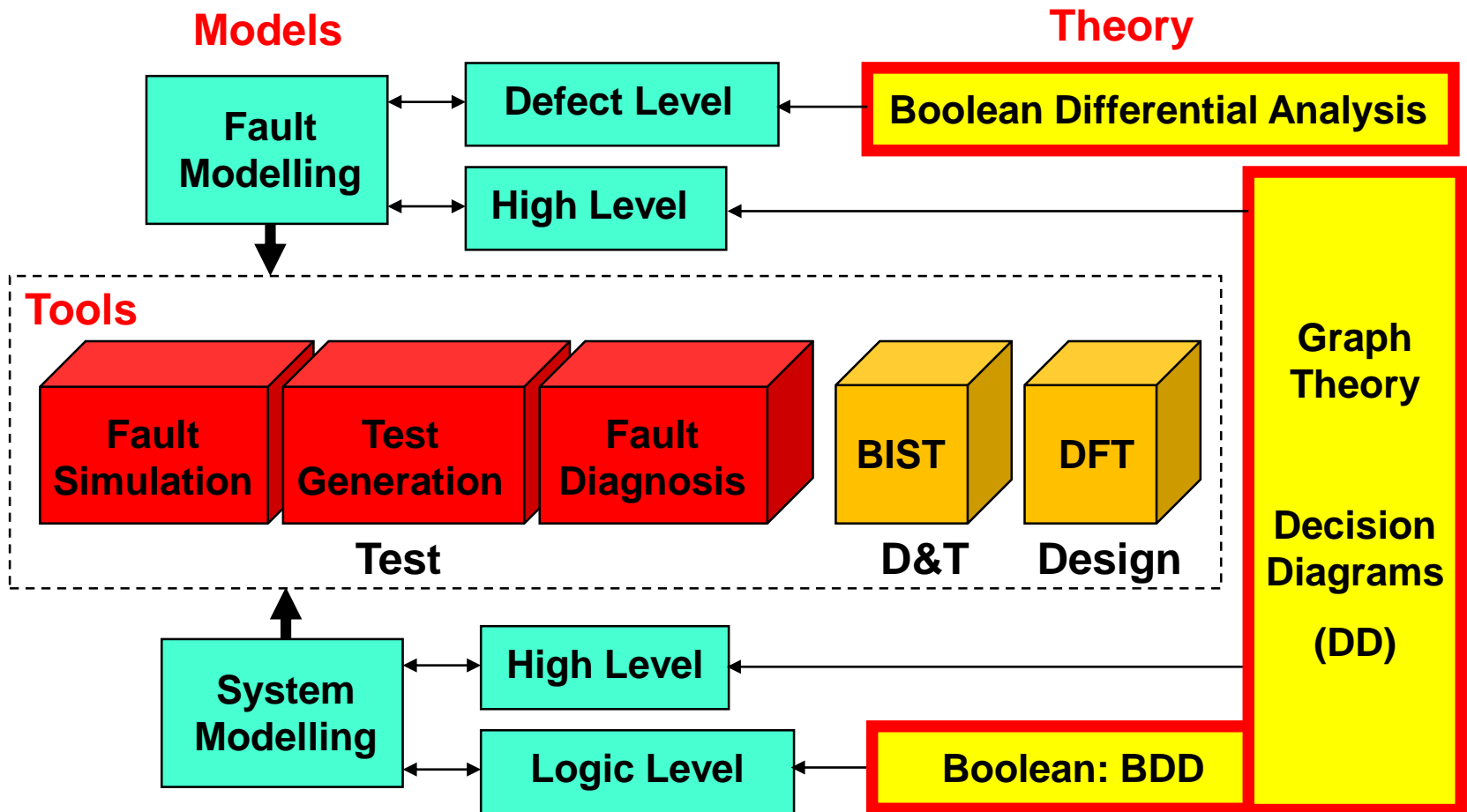

Test Related Basic Problems

Fault table (Solutions of Diagnostic equations)

Test experiment data

Fault modeling

	E ₁	E ₂	E ₃	E ₄	E ₅	E ₆	E ₇
T ₁	0	1	1	0	0	0	0
T ₂	1	0	0	1	0	0	0
T ₃	1	1	0	1	0	1	0
T ₄	0	1	0	0	1	0	0
T ₅	0	0	1	0	1	1	0
T ₆	0	0	1	0	0	1	1

How many rows and columns should be in the Fault Table?

Test generation

Fault simulation

VIRTUAL WORLD


Fault F₅ located

E ₁	E ₂	E ₃
0	0	1
0	1	0
0	1	0
1	0	1
1	0	1
0	0	0

Fault diagnosis


REAL WORLD

Formaalne testimine ja diagnostika

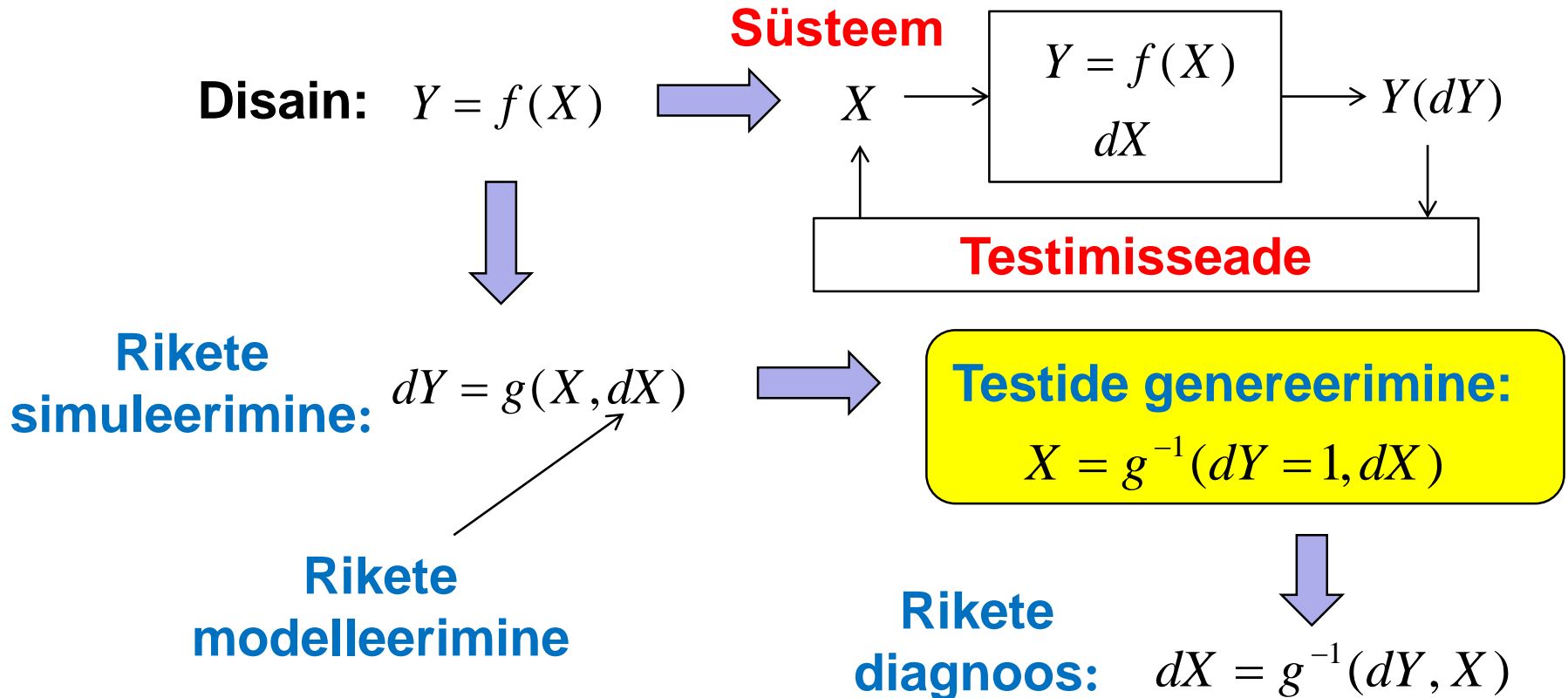


Basics: Fault Propagation Problem

Single logic gate:

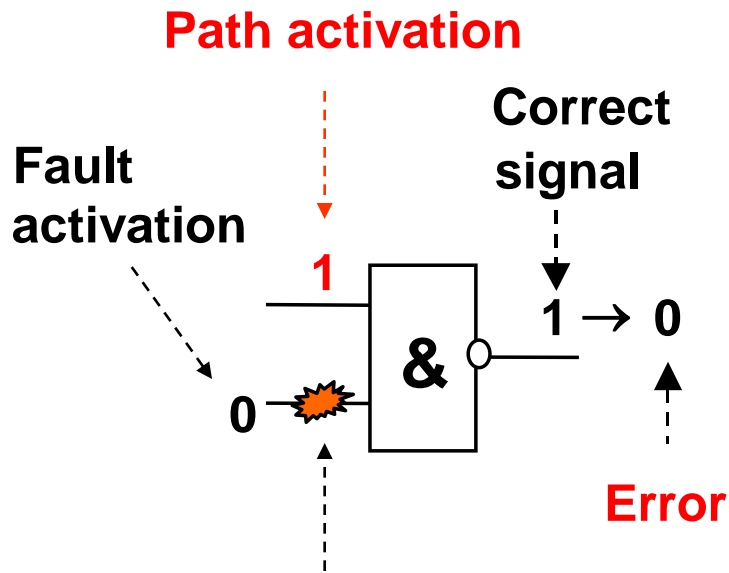

Fault "Stuck-at-1"


Logic circuit:

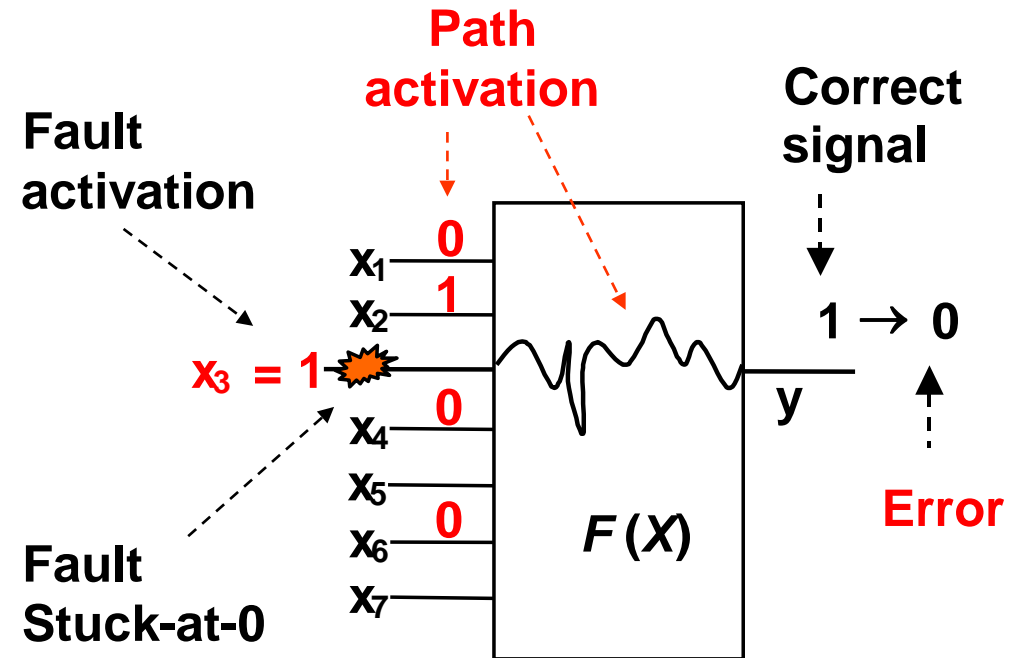

Testide genereerimine: $X = g^{-1}(dY = 1, dX)$

Gate-Level Structural Test Generation

Path activation

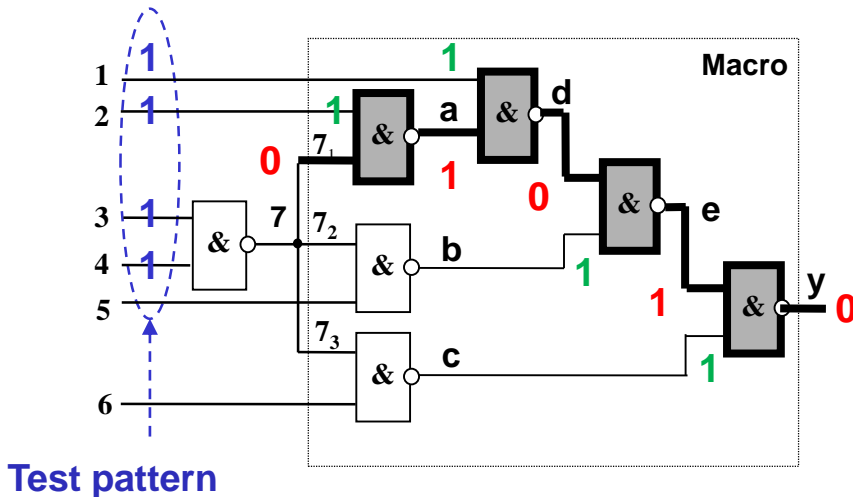

How about test generation for $x_{7,1} \equiv 0$

$$x_{7,1} = 1 \rightarrow \{b = 0, c = 0\}$$

$$b = 0 \rightarrow x_5 = 1$$

$$c = 0 \rightarrow x_6 = 1$$

Gate level test generation:

Fault sensitization (for $x_{7,1} \equiv 1$):

$$x_{7,1} = 0$$

Fault propagation:

$$x_2 = 1, x_1 = 1, b = 1, c = 1$$

Line justification:

$$x_{7,1} = 0 \rightarrow x_7 = 0 \rightarrow \{x_3 = 1, x_4 = 1\}$$

$$b = 1 \rightarrow \text{(already justified)}$$


$$c = 1 \rightarrow \text{(already justified)}$$

The expected result:

$y = 0$ - if fault is missing


$y = 1$ - if fault is present

Backtracking in Test Generation

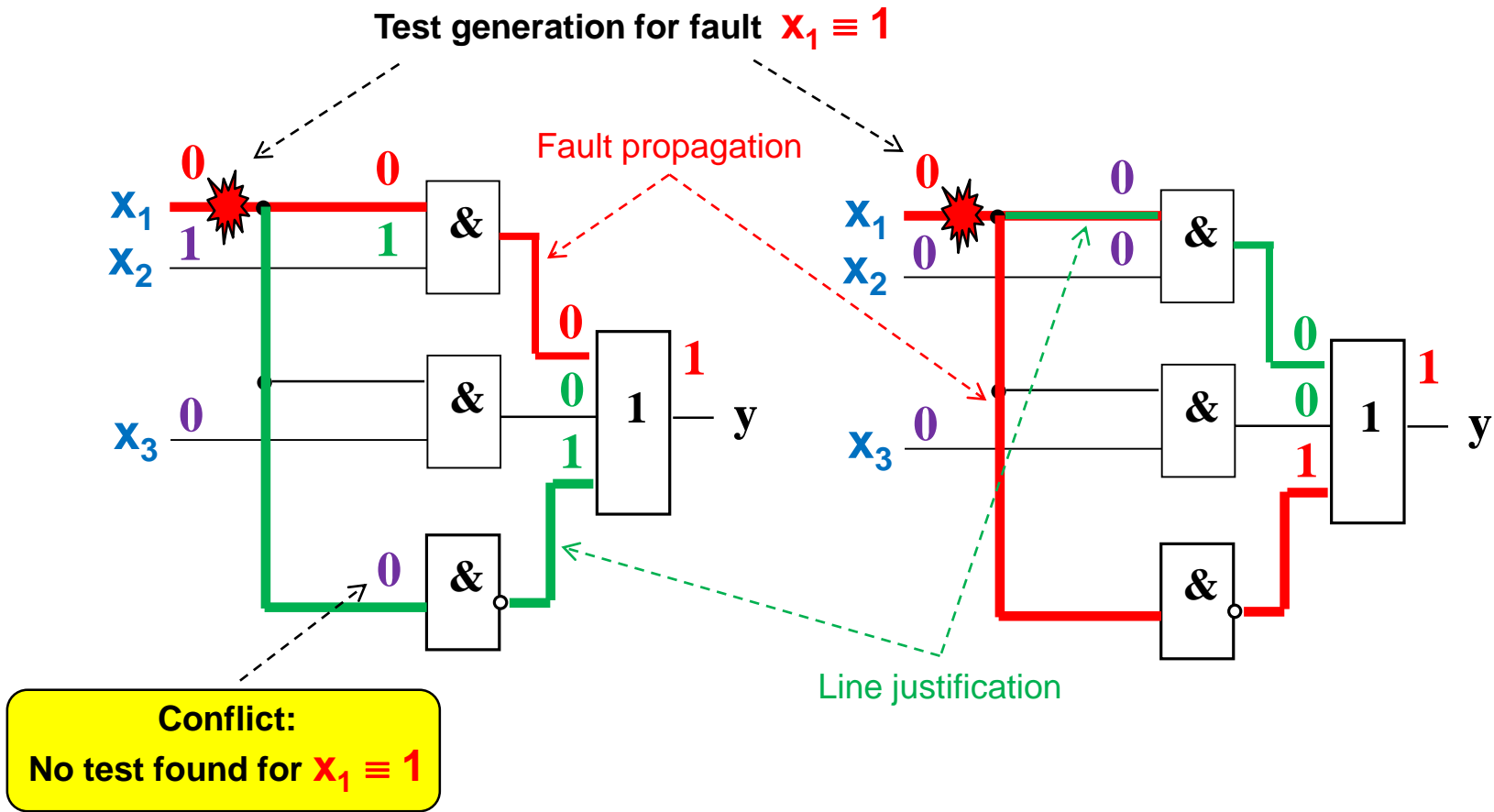

Gate-Level Structural Test Generation

Path activation

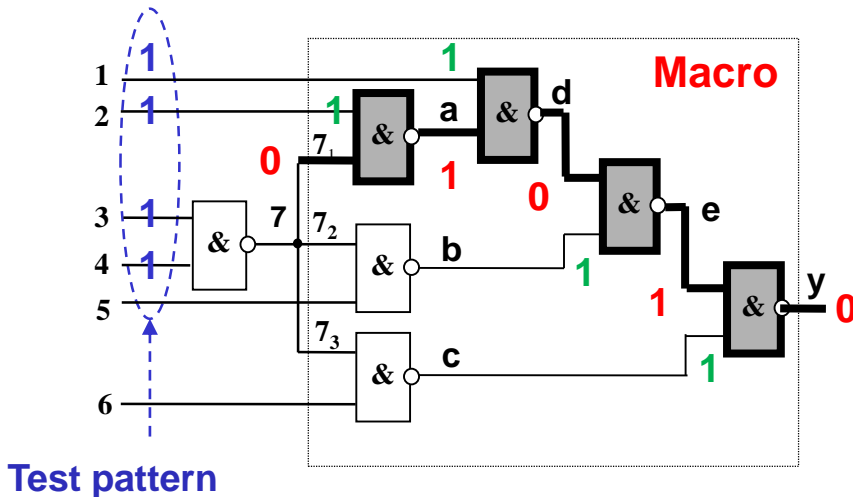

Gate level test generation:

Fault sensitization (for $x_{7,1} \equiv 1$):

$$x_{7,1} = 0$$

Fault propagation:

$$x_2 = 1, x_1 = 1, b = 1, c = 1$$

Line justification:

$$x_{7,1} = 0 \rightarrow x_7 = 0 \rightarrow \{x_3 = 1, x_4 = 1\}$$

$$b = 1 \rightarrow \text{(already justified)}$$

$$c = 1 \rightarrow \text{(already justified)}$$

Another possibility: Macro level test generation

$$y = x_6 x_{7,3} \vee (\overline{x_1} \vee x_2 x_{7,1}) (\overline{x_5} \vee \overline{x_{7,2}})$$

$$\frac{\partial y}{\partial x_{7,1}} = (\overline{x_6} \vee \overline{x_{7,3}}) (\overline{x_5} \vee \overline{x_{7,2}}) x_1 x_2 = x_1 x_2 \overline{x_7} = 1$$


The expected result:

$y = 0$ - if fault is missing

$y = 1$ - if fault is present

Boolean Derivatives

Traditional algebra: speed

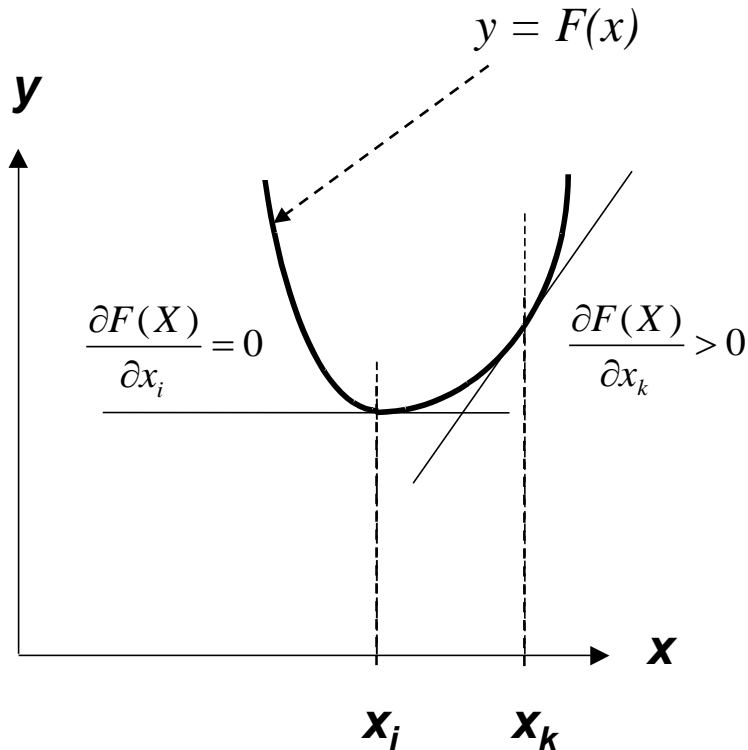

Testide genereerimine:

$$Y = f(X) \Leftrightarrow X = g^{-1}(dY = 1, dX)$$

Boolean algebra: change

$$x \in \{0,1\}, F(X) \in \{0,1\}$$

$$\frac{\partial F(X)}{\partial x_i} = 1$$

$F(X)$ will change
if x_i changes

$$\frac{\partial F(X)}{\partial x_i} = 0$$

$F(X)$ will not
change
if x_i changes

Boolean derivatives

Boolean function:

$$Y = F(x) = F(x_1, x_2, \dots, x_n)$$

Boolean partial derivative:

$$\frac{\partial F(X)}{\partial x_i} = F(x_1, \dots, x_i, \dots, x_n) \oplus F(x_1, \dots, \bar{x}_i, \dots, x_n) = 1$$

Simplified equation:

$$\frac{\partial F(X)}{\partial x_i} = F(x_1, \dots, x_i = 0, \dots, x_n) \oplus F(x_1, \dots, x_i = 1, \dots, x_n) = 1$$

Testide genereerimine: $X = g^{-1}(dY = 1, dX)$

Boolean Derivatives

Useful properties of Boolean derivatives:

For $F(x)$ not depending on x_i

$$\frac{\partial [F(X)G(X)]}{\partial x_i} = F(X) \frac{\partial G(X)}{\partial x_i}$$

$$\frac{\partial [F(X) \vee G(X)]}{\partial x_i} = \overline{F(X)} \frac{\partial G(X)}{\partial x_i}$$

Example: $x_1 x_4 (x_2 x_3 \vee x_2 \overline{x_3})$

$$F(X) = x_1 x_4 \quad G(X) = x_2 x_3 \vee x_2 \overline{x_3}$$

$$\frac{\partial [F(X)G(X)]}{\partial x_2} = x_1 x_4 \frac{\partial G(X)}{\partial x_2}$$

These properties allow to simplify the Boolean differential equation to be solved for generating test pattern for a fault at x_i

Calculation of Boolean Derivatives

Special cases for differential equations:

$$\frac{\partial F(X)}{\partial x_i} \equiv 0 \quad - \quad \text{if } F(x) \text{ is independent of } x_i$$

$$\frac{\partial F(X)}{\partial x_i} \equiv 1 \quad - \quad \text{if } F(x) \text{ depends always on } x_i$$

$$\frac{\partial F(X)}{\partial x_i} = F(x_1, \dots, x_i = 0, \dots, x_n) \oplus F(x_1, \dots, x_i = 1, \dots, x_n)$$

Examples:

$$F(X) = x_1(x_2x_3 \vee x_2\bar{x}_3) : \quad \frac{\partial F(X)}{\partial x_3} = x_1x_2 \oplus x_1x_2 \equiv 0$$

$$F(X) = x_1 \oplus x_2 : \quad \frac{\partial F(X)}{\partial x_1} = \bar{x}_2 \oplus x_2 \equiv 1$$

Calculation of Boolean Derivatives

Example:

Given: $y = x_1 x_2 \vee x_3 (\overline{x_2} x_4 \vee \overline{x_1} (x_4 \vee (x_5 \vee \overline{x_2} x_6))) \vee \overline{x_1} \overline{x_3}$

Calculation of the Boolean derivative:

$$\begin{aligned} \frac{\partial y}{\partial x_5} &= \overline{x_1 x_2 \vee x_1 x_3} \frac{\partial (x_3 (\overline{x_2} x_4 \vee \overline{x_1} (x_4 \vee (x_5 \vee \overline{x_2} x_6))))}{\partial x_5} = \\ &= \overline{x_1 x_2 \vee x_1 x_3} x_3 \frac{\partial (\overline{x_2} x_4 \vee \overline{x_1} (x_4 \vee (x_5 \vee \overline{x_2} x_6)))}{\partial x_5} = \\ &= \overline{x_1 x_2 \vee x_1 x_3} x_3 \overline{x_2} x_4 \frac{\partial (\overline{x_1} (x_4 \vee (x_5 \vee \overline{x_2} x_6)))}{\partial x_5} = \\ &= \overline{x_1 x_2 \vee x_1 x_3} x_3 \overline{x_2} x_4 \overline{x_1} \frac{\partial (x_4 \vee (x_5 \vee \overline{x_2} x_6))}{\partial x_5} = \overline{x_1 x_2 \vee x_1 x_3} x_3 \overline{x_2} x_4 \overline{x_1} x_4 x_2 x_6 \frac{\partial x_5}{\partial x_5} \end{aligned}$$

Calculation of Boolean derivatives

Finding a solution of the differential equation:


$$\begin{aligned}\frac{\partial y}{\partial x_5} &= \overline{(x_1 x_2 \vee x_1 x_3)} x_3 \overline{(x_2 x_4)} x_1 x_4 \overline{(x_2 x_6)} \frac{\partial x_5}{\partial x_5} = \\ &= (\overline{x_1} \vee \overline{x_2})(\overline{x_1} \vee \overline{x_3}) x_3 (x_2 \vee \overline{x_4}) x_1 x_4 (x_2 \vee \overline{x_6}) = \\ &= \overline{x_1} x_4 x_3 x_2 \vee \dots = 1\end{aligned}$$

Boolean vector derivatives

Multiple fault cases and fan-outs:

$$\frac{\partial F(X)}{\partial(x_i, x_j)} = F(x_1, \dots, x_i, x_j, \dots, x_n) \oplus F(x_1, \dots, \bar{x}_i, \bar{x}_j, \dots, x_n)$$

Example:

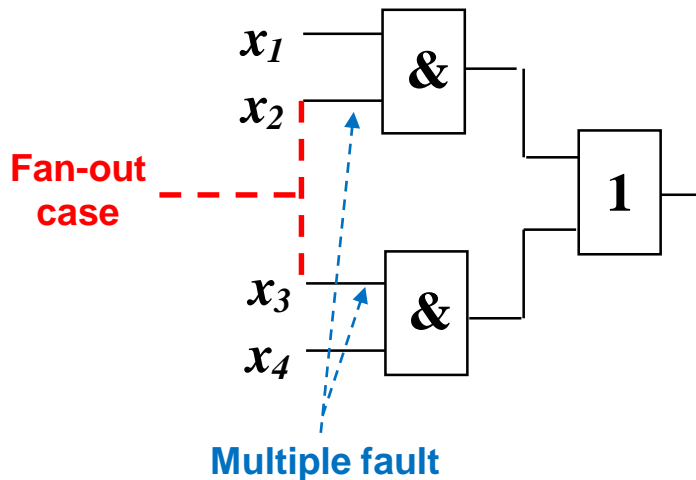


$$y = F(x_1, x_2, x_3, x_4) = x_1 x_2 \vee x_3 x_4$$

$$\frac{\partial F(X)}{\partial(x_2, x_3)} = x_1 \bar{x}_4 \vee \bar{x}_1 x_4 \vee x_1 x_4 (\bar{x}_2 \bar{x}_3 \vee x_2 x_3)$$

Boolean vector derivatives

Calculation of the vector derivatives by Carnaugh maps:
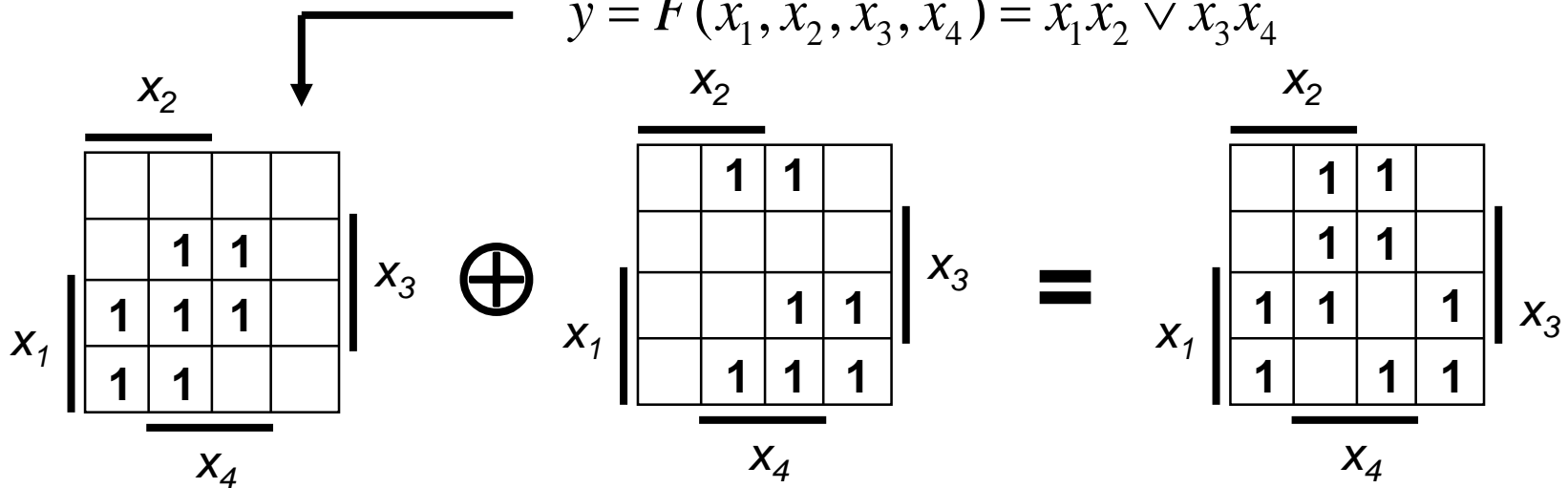
$$y = F(x_1, x_2, x_3, x_4) = x_1 x_2 \vee x_3 x_4$$



$$x_1 x_2 \vee x_3 x_4$$





$$x_1 x_2 \vee x_3 x_4$$

$$\frac{\partial F(X)}{\partial(x_2, x_3)} = x_1 \bar{x}_4 \vee \bar{x}_1 x_4 \vee x_1 x_4 (\bar{x}_2 \bar{x}_3 \vee x_2 x_3) = 1$$

Boolean vector derivatives

Interpretation of three solutions:
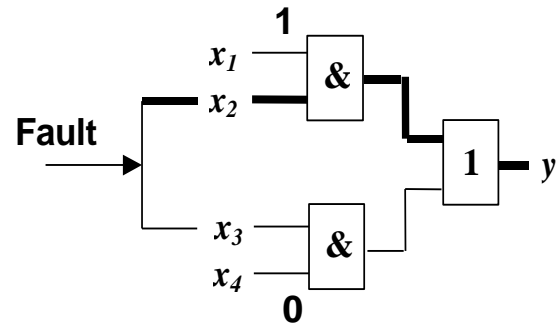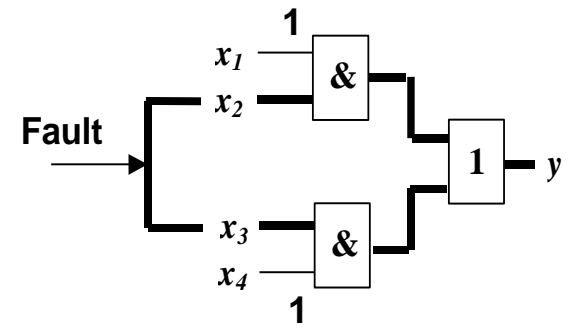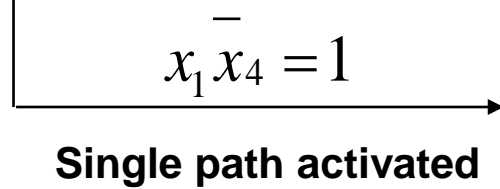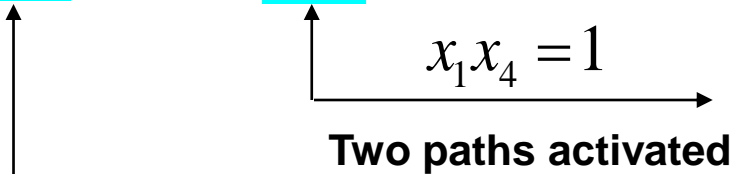
$$\frac{\partial F(X)}{\partial(x_2, x_3)} = \bar{x}_1 \bar{x}_4 \vee \bar{x}_1 x_4 \vee x_1 x_4 (\bar{x}_2 \bar{x}_3 \vee x_2 x_3) = 1$$



Multiple Boolean derivatives

$$y = x_1x_2 \vee x_3x_4$$



$$\frac{\partial y}{\partial x_3} = \bar{x}_1\bar{x}_4 \vee \bar{x}_2\bar{x}_4 = 1$$

$$\frac{\partial^2 y}{\partial x_2 \partial x_3} = \frac{\partial}{\partial x_2} \left(\frac{\partial y}{\partial x_3} \right) = x_1x_4 = 0$$

Fault in x_2 cannot mask the fault in x_3

Test for x_3


Two faults

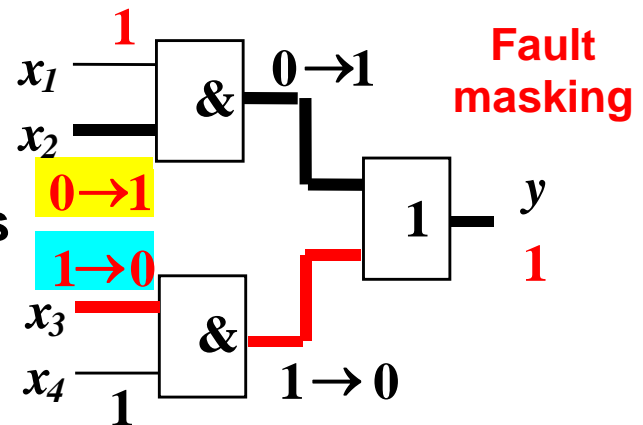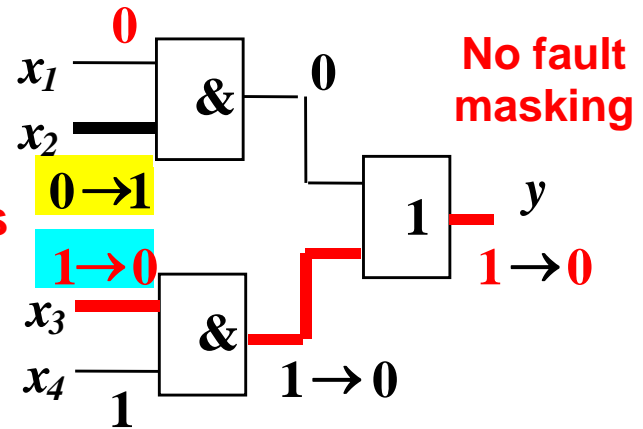

$$x_1x_4 = 1$$


Bool. derivatives for sequential circuits

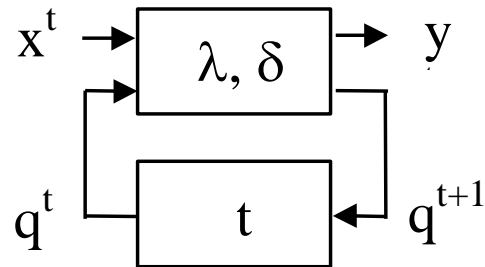Boolean derivatives for state transfer and output functions of FSM:




$$y(t) = \lambda[x(t), q(t)]$$

$$q(t+1) = \delta[x(t), q(t)]$$

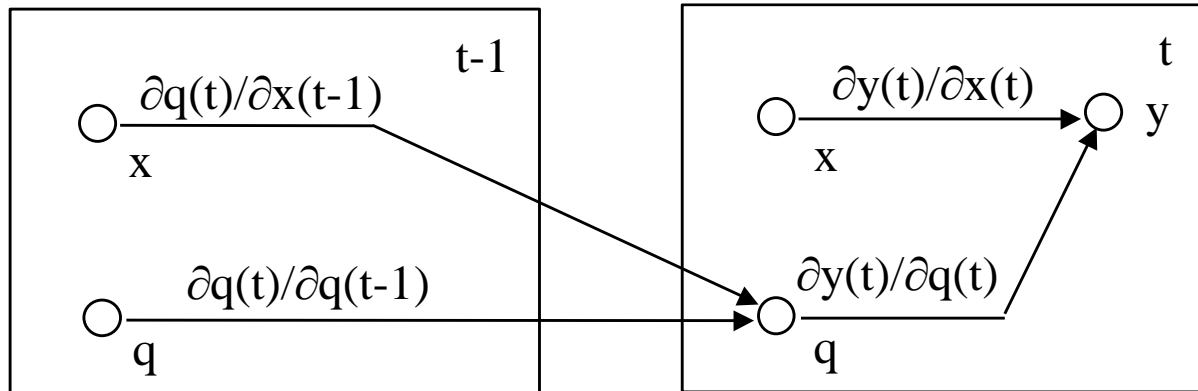

Bool. derivatives for sequential circuits

Boolean derivatives for JK Flip-Flop:

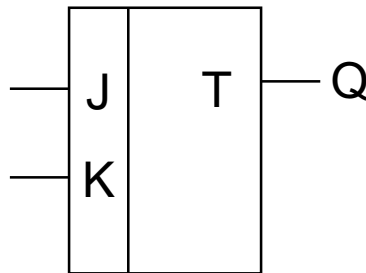

$$Q(t) = J(t)\bar{Q}(t-1) \vee \bar{K}(t-1)Q(t-1)$$

$$\frac{\partial Q(t)}{\partial J(t-1)} = \bar{Q}(t-1)$$

$$\frac{\partial Q(t)}{\partial K(t-1)} = Q(t-1)$$

The erroneous signal will propagate from inputs to output

The erroneous signal was stored in the previous clock cycle

$$\frac{\partial Q(t)}{\partial Q(t-1)} = K(t-1)J(t-1) \vee \bar{K}(t-1)\bar{J}(t-1)$$

Derivatives for complex functions

Boolean derivative for a complex function:

$$\frac{\partial F_k(F_j(X), X)}{\partial x_i} = \frac{\partial F_k}{\partial F_j} \frac{\partial F_j}{\partial x_i}$$


Hierarchical solution:

$$\frac{\partial y}{\partial x_4} = \frac{\partial y}{\partial x_1} \frac{\partial x_1}{\partial x_3} \frac{\partial x_3}{\partial x_4}$$

Additional condition:

$$\frac{\partial x_2}{\partial x_3} = 0$$

Example:

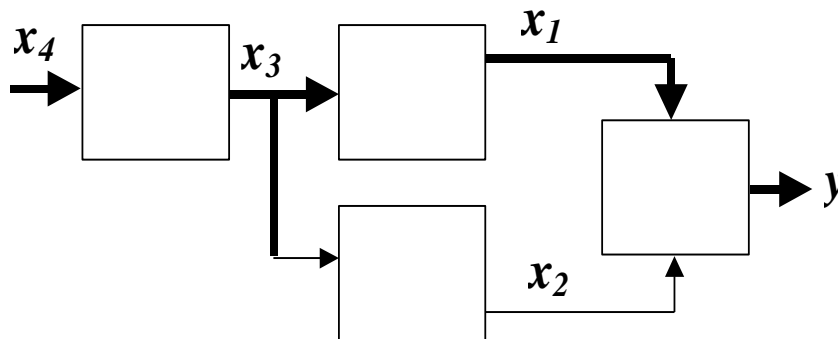

Overview about Applications of BDs

- **Fault simulation**

- Calculate the value of: $\frac{\partial F(X)}{\partial x_i}$

- **Test generation**

- Single faults: Find the solution for: $\frac{\partial F(X)}{\partial x_i} = 1$

- Multiple faults: Find the solution for: $\frac{\partial F(X)}{\partial(x_i, x_j)} = 1$

- Decompositional approach (complex functions):

$$\frac{\partial F_k(F_j(X), X)}{\partial x_i} = \frac{\partial F_k}{\partial F_j} \frac{\partial F_j}{\partial x_i}$$

- **Fault masking analysis:** $\frac{\partial y}{\partial x_i} = 1; \frac{\partial^2 y}{\partial x_j \partial x_i} = \frac{\partial}{\partial x_j} \left(\frac{\partial y}{\partial x_i} \right) = 0$

2. Teoreetilised alused

2.1. Boole'i differentsiaalalgebra

- Boole'i funktsioonide differentseerimine
- Boole'i differentsiaalvõrrandid

2.2. Binaarsed otsustusdiagrammid (BDD)

2.3. Kõrgtasandi otsustusdiagrammid

Boolean Differentials and Fault Diagnosis

dx - fault variable, $dx \in (0, 1)$

$dx = 1$, if the value of X has changed because of a fault

Partial Boolean differential (for fault **simulation**):

$$d_{x_i} F = F(x_1, \dots, x_i, \dots, x_n) \oplus F(x_1, \dots, x_i \oplus dx_i, \dots, x_n) = \frac{\partial F}{\partial x_i} dx_i$$

Full Boolean differential (for fault **diagnosis**):

$$dF = F(x_1, \dots, x_i, \dots, x_n) \oplus F(x_1 \oplus dx_1, \dots, x_i \oplus dx_i, \dots, x_n \oplus dx_n)$$



$$dF = F(X) \oplus F(X \oplus dX)$$

Fault diagnosis: $dX = g^{-1}(dY, X)$

Boolean Differentials and Fault Diagnosis

$$y = \bar{x}_1(\bar{x}_2 \vee x_3) \quad dy = y \oplus (\bar{x}_1 \oplus dx_1)((\bar{x}_2 \oplus dx_2) \vee (x_3 \oplus dx_3))$$

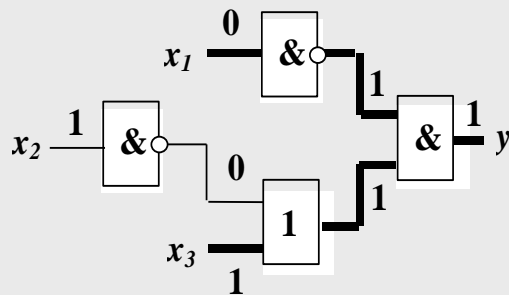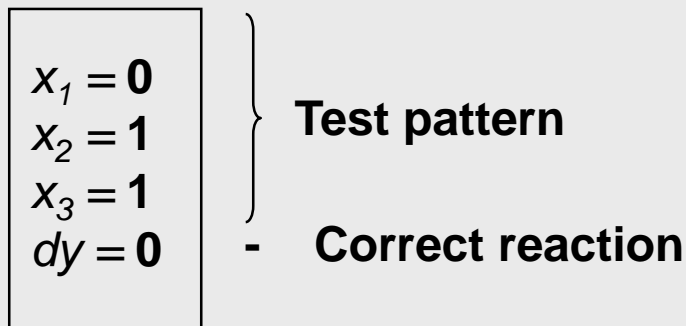Diagnostic experiment \Rightarrow **Fault diagnosis:** $dX = g^{-1}(dY, X)$



Substitution of values:

$$dy = 1 \oplus \bar{dx}_1(dx_2 \vee \bar{dx}_3) = 0$$

$$dy = \bar{dx}_1(dx_2 \vee \bar{dx}_3) = 1$$

Adjusting for SAF faults:


$$\bar{dx}_1^0(dx_2^1 \vee \bar{dx}_3^1) = 1$$

Partial diagnosis: $\bar{dx}_1^0 = 1$


Boolean Differentials and Fault Diagnosis

$$y = \bar{x}_1(\bar{x}_2 \vee x_3) \quad dy = y \oplus (\bar{x}_1 \oplus dx_1)((\bar{x}_2 \oplus dx_2) \vee (x_3 \oplus dx_3))$$

Two diagnostic experiments

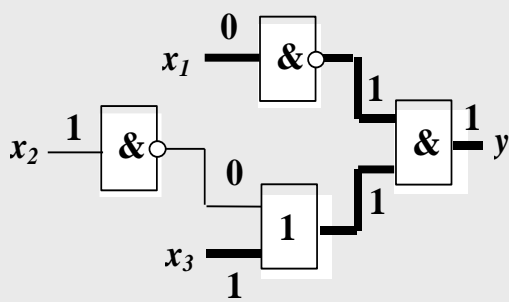
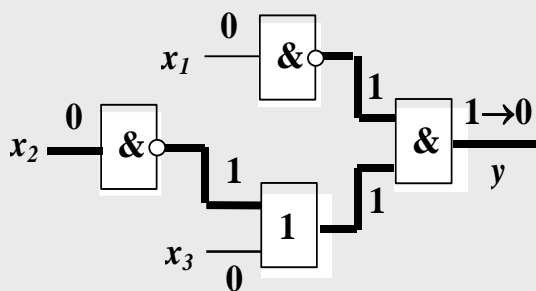
$$\begin{aligned} x_1 &= 0 \\ x_2 &= 1 \\ x_3 &= 1 \\ dy &= 0 \end{aligned}$$



$$\begin{aligned} x_1 &= 0 \\ x_2 &= 0 \\ x_3 &= 0 \\ dy &= 1 \end{aligned}$$

1) Correct output signal:

$$\bar{dx}_1^0(dx_2^1 \vee \bar{dx}_3^1) = 1 \rightarrow \boxed{\bar{dx}_1^0 = 1}$$

2) Erroneous output signal:

$$dy = 1 \oplus \bar{dx}_1(\bar{dx}_2 \vee dx_3) = 1$$

$$dx_1^0 \vee dx_2^0 \bar{dx}_3^0 = 1$$

Diagnosis from two experiments

$$\bar{dx}_1^0(dx_2^1 \vee \bar{dx}_3^1)(dx_1^0 \vee dx_2^0 \bar{dx}_3^0) = 1$$

Boolean Differentials and Fault Diagnosis

Diagnosis from two experiments:

$$\overline{dx_1^0} (dx_2^1 \vee \overline{dx_3^1}) (dx_1^0 \vee dx_2^0 \overline{dx_3^0}) = 1$$

Rule: $\overline{dx_k^0} dx_k^0 = 0$

$$\overline{dx_1^0} (dx_2^1 dx_2^0 \overline{dx_3^0} \vee dx_2^0 \overline{dx_3^0} \overline{dx_3^1}) = 1$$

$$= 0$$

Rule: $dx_k^0 dx_k^1 = 0$

Final diagnosis:

$$\overline{dx_1^0} dx_2^0 \overline{dx_3^0} \overline{dx_3^1} = 1$$

The line x_3 works correctly
 There is a fault: $x_2 \equiv 1$
 The fault $x_1 \equiv 1$ is missing

Question:

1) Which question regarding the possible present faults is still open?

Correctness Proof with Test Pairs

$$y = x_1 x_2 \vee x_3$$

$$dy = y \oplus (x_1 \oplus dx_1)(x_2 \oplus dx_2) \vee (x_3 \oplus dx_3)$$

We will test the fault $x_1 \equiv 1$


The test is successful

So, we conclude that x_1 is correct

Let us use now mathematics:

$$dy = dx_1 \overline{dx_2} \vee dx_3 = 0$$
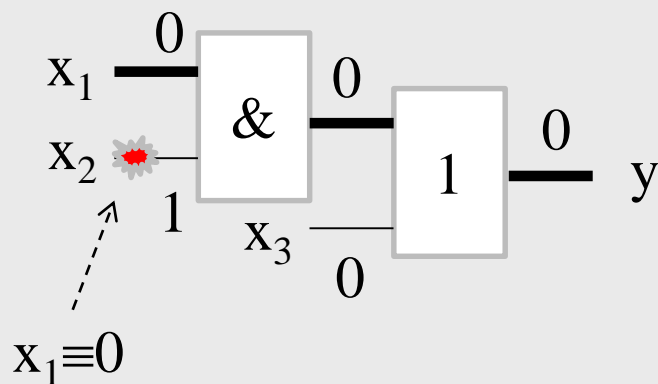
$$(\overline{dx_1} \vee \overline{dx_2}) \overline{dx_3} = 1$$





Now we are not any more very sure about x_1

Correctness Proof with Test Pairs

$$y = x_1 x_2 \vee x_3$$
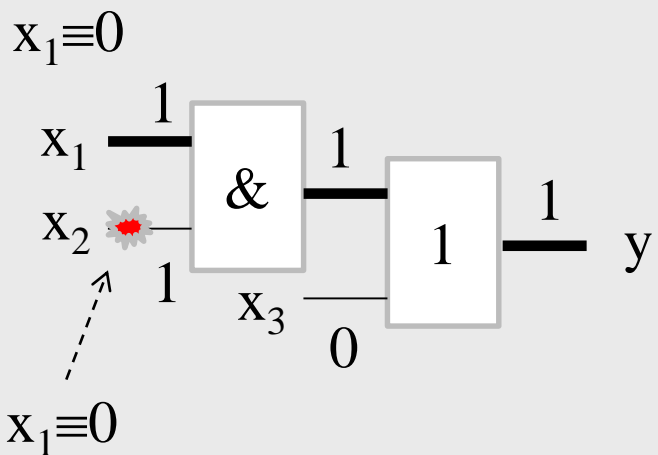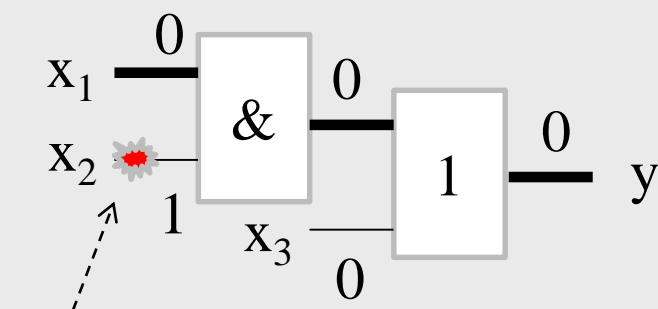
$$dy = y \oplus (x_1 \oplus dx_1)(x_2 \oplus dx_2) \vee (x_3 \oplus dx_3)$$



We have: $dy = dx_1 \overline{dx_2} \vee dx_3 = 0$

$$(\overline{dx_1} \vee dx_2) \overline{dx_3} = 1$$

2. test: we change the value of x_1 to have a test pair

$$dy = 1 \oplus (\overline{dx_1} \overline{dx_2} \vee dx_3) = 0$$

$$(\overline{dx_1} \overline{dx_2} \vee dx_3) = 1$$

Both experiments together:

$$\begin{aligned} & (\overline{dx_1^1} \overline{dx_2} \vee dx_3) (\overline{dx_1^0} \vee dx_2) \overline{dx_3} = \\ & = \overline{dx_1^1} \overline{dx_1^0} \overline{dx_2} \overline{dx_3} = 1 \end{aligned}$$

Diagnostic Equation


Digital circuit:

$$X \Rightarrow y = F(X) \quad y = \bar{x}_1 (\bar{x}_2 \vee x_3) \Rightarrow y$$

Diagnostic model: Full differential equation

$$X, dX \Rightarrow dy = F(X, dX)$$
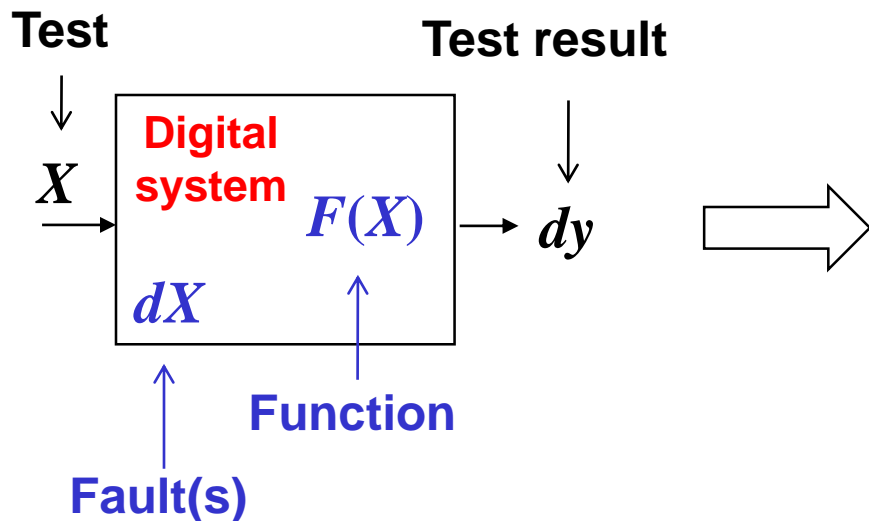
$$dy = y \oplus (\bar{x}_1 \oplus dx_1) ((\bar{x}_2 \oplus dx_2) \vee (x_3 \oplus dx_3)) \Rightarrow dy$$




Diagnostic equation:

$$F(X, dX) = dy$$

\uparrow \uparrow \uparrow
 Test Test result
 Fault(s)

How the Test Tasks are Related

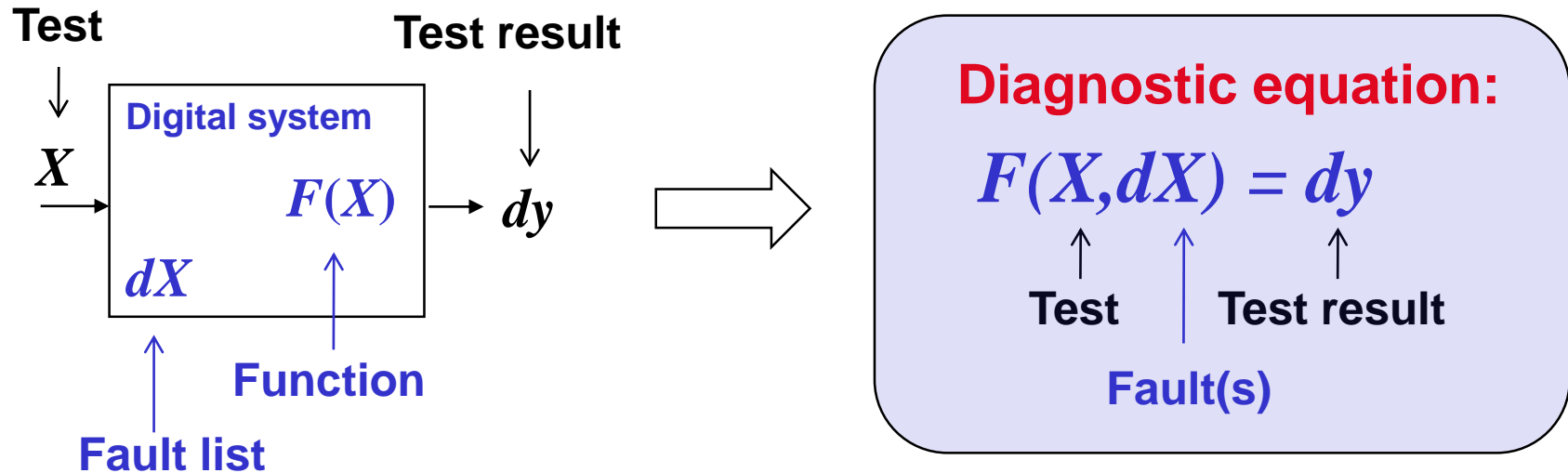

Task	Given		Find
Test generation	dx	dy = 1	X
Fault diagnosis	X	dy	{dx}
Fault simulation	X	dy = 1	{dx}

Special case of fault diagnosis

Both equations can be presented as SAT tasks