

Süsteemide diagnostika

2. Teoreetilised alused

2.1. Boole'i differentsiaalalgebra


2.2. Binaarsed otsustusdiagrammid (BDD)

2.3. Kõrgtasandi otsustusdiagrammid


How to Go Beyond the Boolean World?

Two basic tasks:

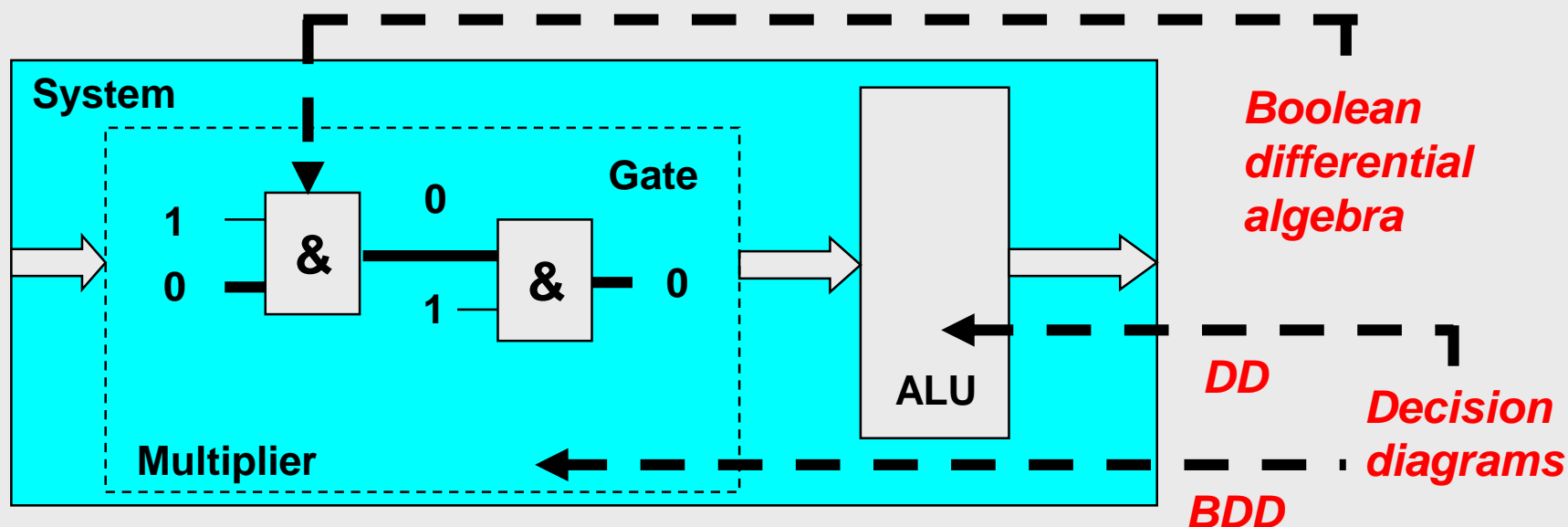1. Which test patterns are needed to detect a fault (or all faults)
2. Which faults are detected by a given test (or by all tests)



Logic Level BDDs

 

Functional BDD

$$y = x_1 \vee x_2 (x_3 \vee x_4 x_5) \vee x_6 x_7$$

Simulation:

$$\begin{array}{ccccccccc} x_1 & x_2 & x_3 & x_4 & x_5 & x_6 & x_7 & & y \\ 0 & 1 & 1 & 0 & 1 & 0 & 0 & \longrightarrow & 1 \end{array}$$


Boolean derivative:

$$\frac{\partial y}{\partial x_3} = \overline{x_1} \vee \overline{x_6 x_7 x_2 x_4 x_5} = 1$$

Generalization of BDDs


Binary DD

 2 terminal nodes and
2 edges from each node



General case of DD

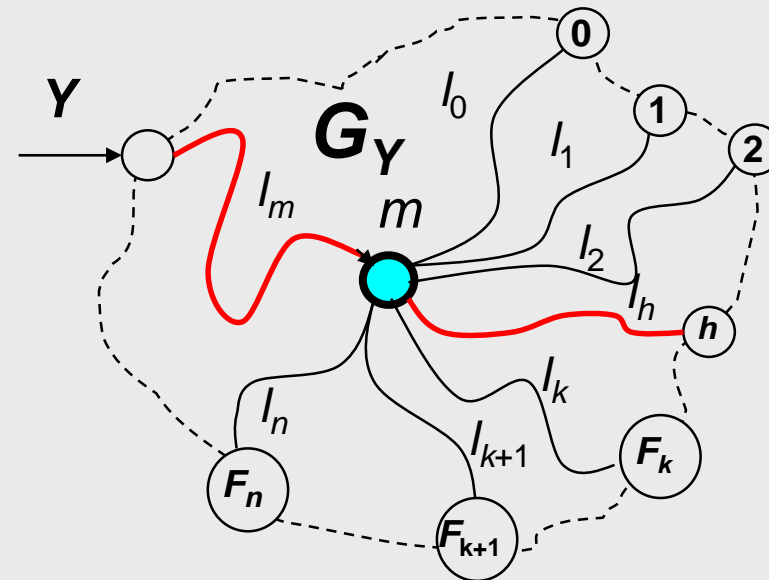$n \geq 2$ terminal nodes and
 $n \geq 2$ edges from each node



Novelty: Boolean methods can be generalized in a straightforward way to higher functional levels

HLDDs and Faults


Each path in a DD represents a **working mode** of the system
 The **faults** having effect on the behaviour can be associated with nodes **along the path**

D1: node output is **always activated (SAF-1)**

D2: node output is **broken (SAF-0)**

D3: instead of the given output **another output set is activated**

 Instead of the 14 fault classes, the HLDD based fault model includes only 3 fault classes



based

HLDDs and Faults

RTL-statement:

$$K: (If T,C) R_D \leftarrow F(R_{S1}, R_{S2}, \dots, R_{Sm}), \rightarrow N$$

Nonterminal nodes



RTL-statement faults:

label,
timing condition,
logical condition,
register decoding,
operation decoding,
control faults

Terminal nodes

RTL-statement faults:

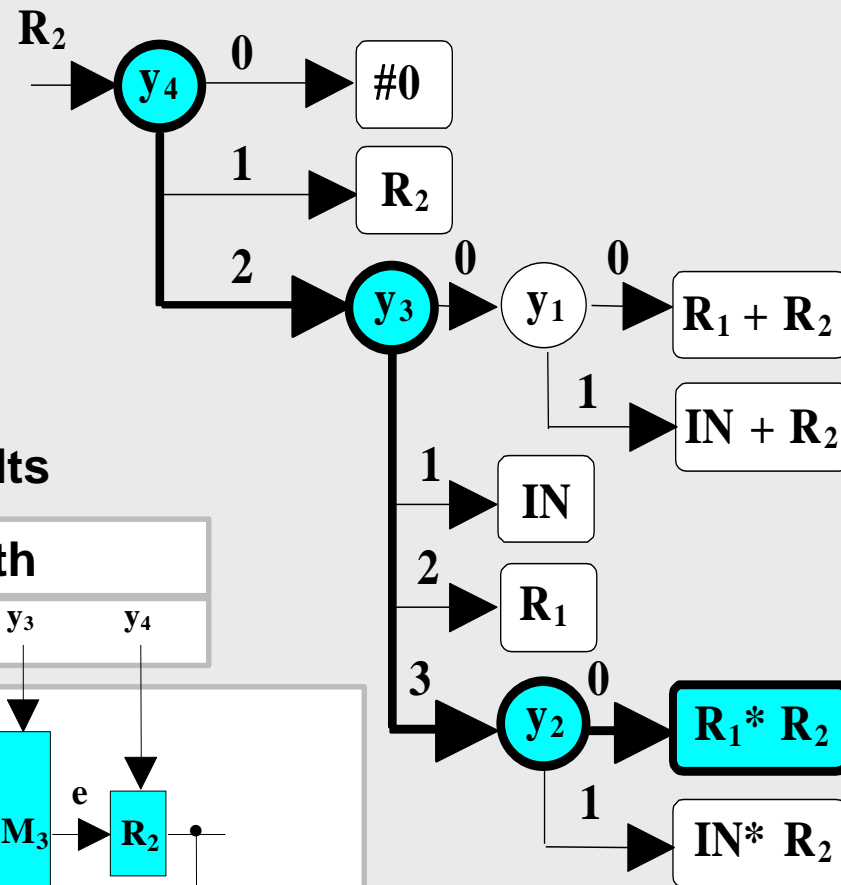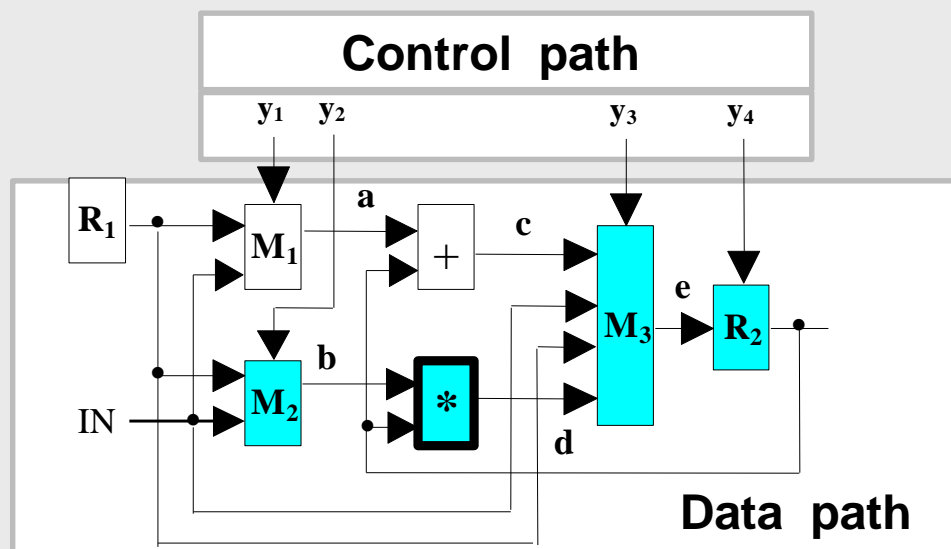
data storage,
data transfer,
data manipulation faults




Test Generation in Digital Systems

Multiple paths activation in a DD

Control function y_3 is tested

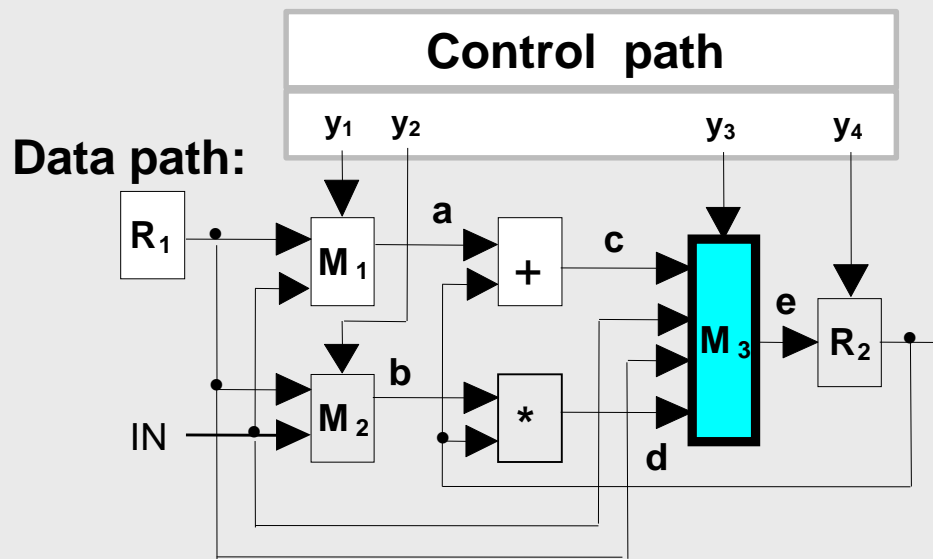

Decision Diagram

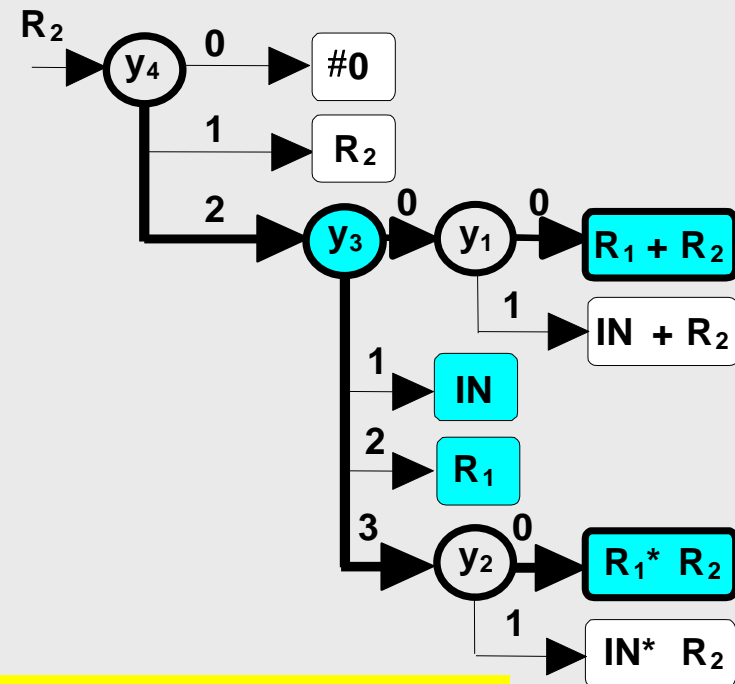

Test cycle:

Control: For $D = 0, 1, 2, 3$: $y_1 y_2 y_3 y_4 = 00D2$


Data: Solution of $R_1 + R_2 \neq IN \neq R_1 \neq R_1 * R_2$

Decision Diagrams for Microprocessors

Instruction set:


I_1 :	MVI A,D	$A \leftarrow IN$
I_2 :	MOV R,A	$R \leftarrow A$
I_3 :	MOV M,R	OUT $\leftarrow R$
I_4 :	MOV M,A	OUT $\leftarrow A$
I_5 :	MOV R,M	$R \leftarrow IN$
I_6 :	MOV A,M	$A \leftarrow IN$
I_7 :	ADD R	$A \leftarrow A + R$
I_8 :	ORA R	$A \leftarrow A \vee R$
I_9 :	ANA R	$A \leftarrow A \wedge R$
I_{10} :	CMA A,D	$A \leftarrow \neg A$

DD-model of the microprocessor:

 


Decision Diagrams for Microprocessors

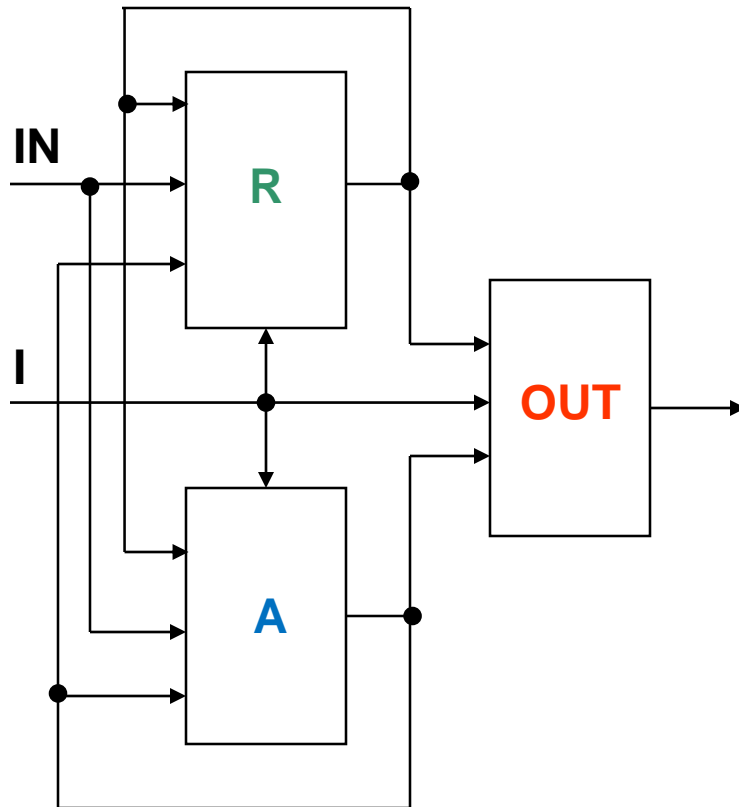High-Level DD-based structure of the microprocessor (example):



DD-model of the microprocessor:

 

From MP Instruction Set to HLDDs


OP	B	Semantic	RT level operations	
0	0	READ memory	$R(A1) = M(A)$	$PC = PC + 2$
	1	WRITE memory	$M(A) = R(A2)$	$PC = PC + 2$
1	0	Transfer	$R(A1) = R(A2)$	$PC = PC + 1$
	1	Complement	$R(A1) = \neg R(A2)$	$PC = PC + 1$
2	0	Addition	$R(A1) = R(A1) + R(A2)$	$PC = PC + 1$
	1	Subtraction	$R(A1) = R(A1) - R(A2)$	$PC = PC + 1$
3	0	Jump	$PC = A$	
	1	Conditional jump	IF C=1, THEN PC = A, ELSE PC = PC + 2	

Instruction code:


ADD A1 A2

OP=2. B=0. A1=3. A2=2

$R_3 = R_3 + R_2$
 $PC = PC + 1$

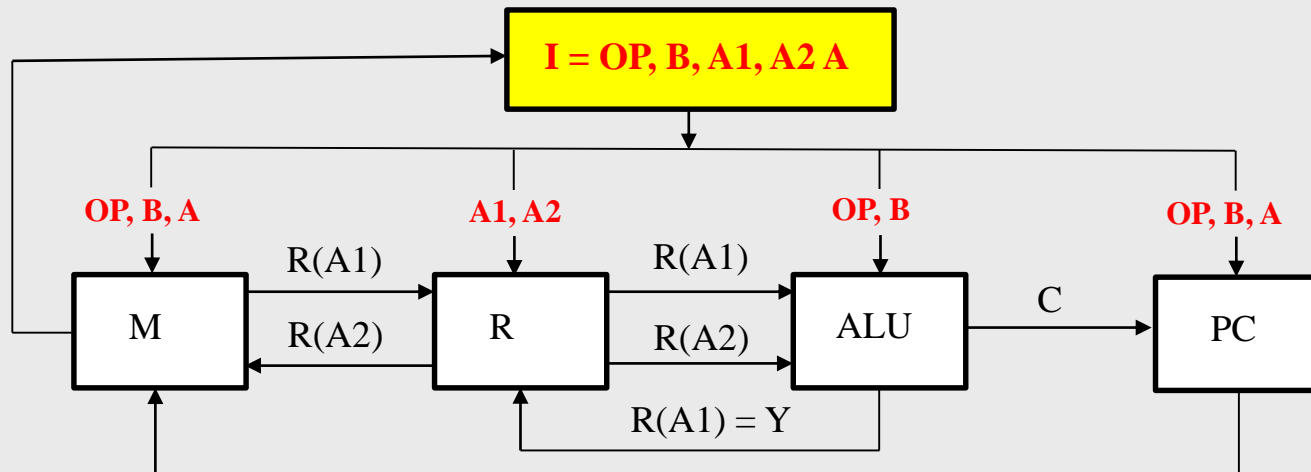





From MP Instruction Set to HLDDs

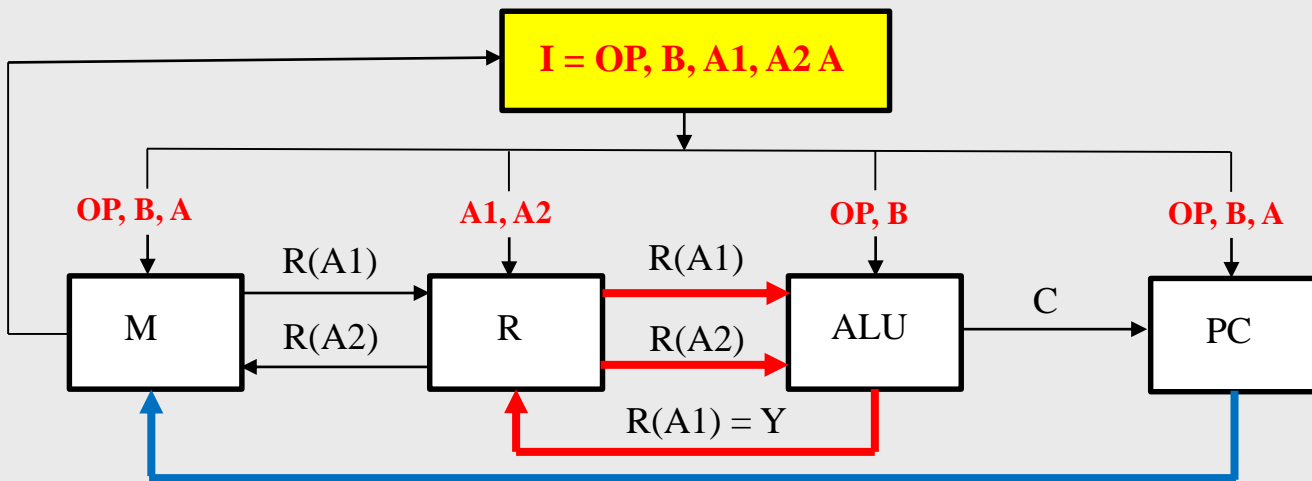

Instruction code:
ADD A1 A2

OP=2. B=0. A1=3. A2=2

$R_3 = R_3 + R_2$
 $PC = PC + 1$

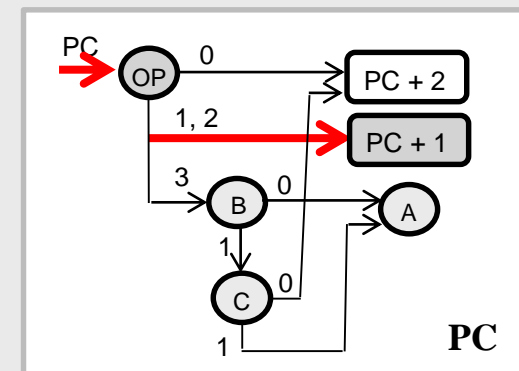 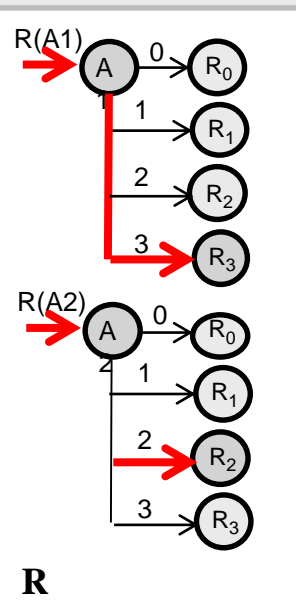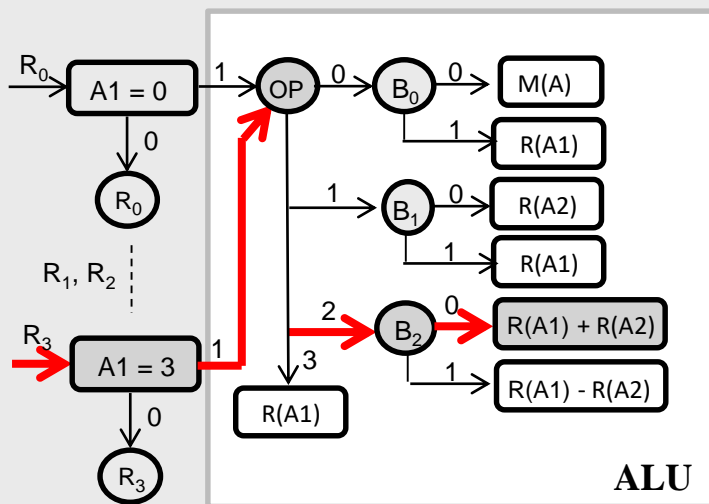

From MP Instruction Set to HLDDs




OP	B	Semantic	RT level operations	
0	0	READ memory	$R(A1) = M(A)$	$PC = PC + 2$
	1	WRITE memory	$M(A) = R(A2)$	$PC = PC + 2$
1	0	Transfer	$R(A1) = R(A2)$	$PC = PC + 1$
	1	Complement	$R(A1) = \neg R(A2)$	$PC = PC + 1$
2	0	Addition	$R(A1) = R(A1) + R(A2)$	$PC = PC + 1$
	1	Subtraction	$R(A1) = R(A1) - R(A2)$	$PC = PC + 1$
3	0	Jump	$PC = A$	
	1	Conditional jump	IF C=1, THEN PC = A, ELSE PC = PC + 2	

Instruction code:

ADD A1 A2


OP=2. B=0. A1=3. A2=2

$R_3 = R_3 + R_2$
 $PC = PC + 1$

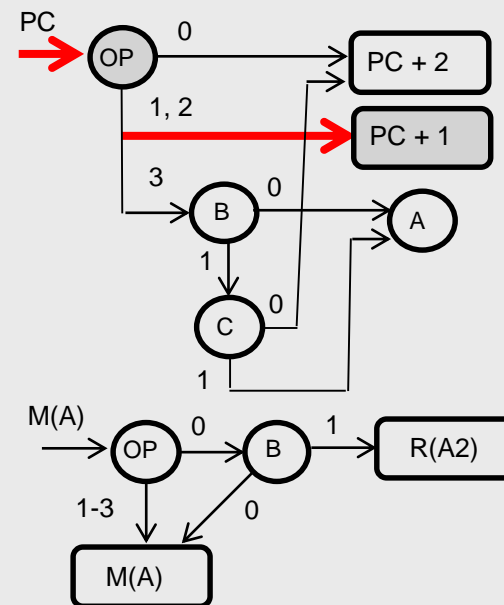 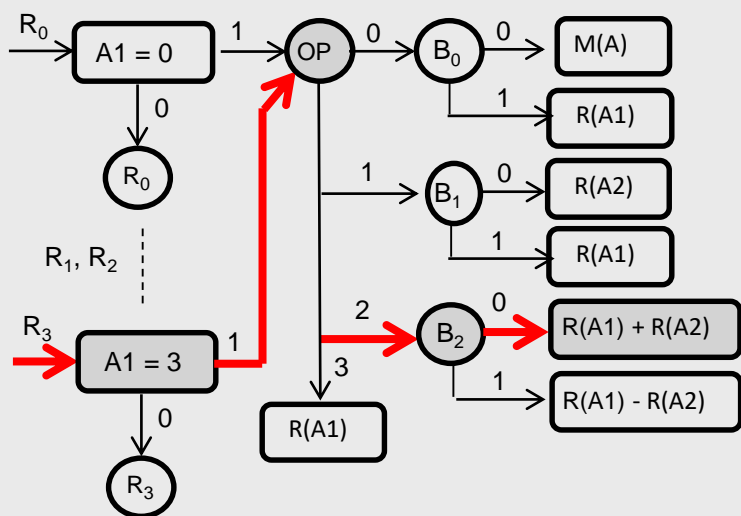


Data Path: Structural Synthesis of HLDDs

Structural description of the Data Path

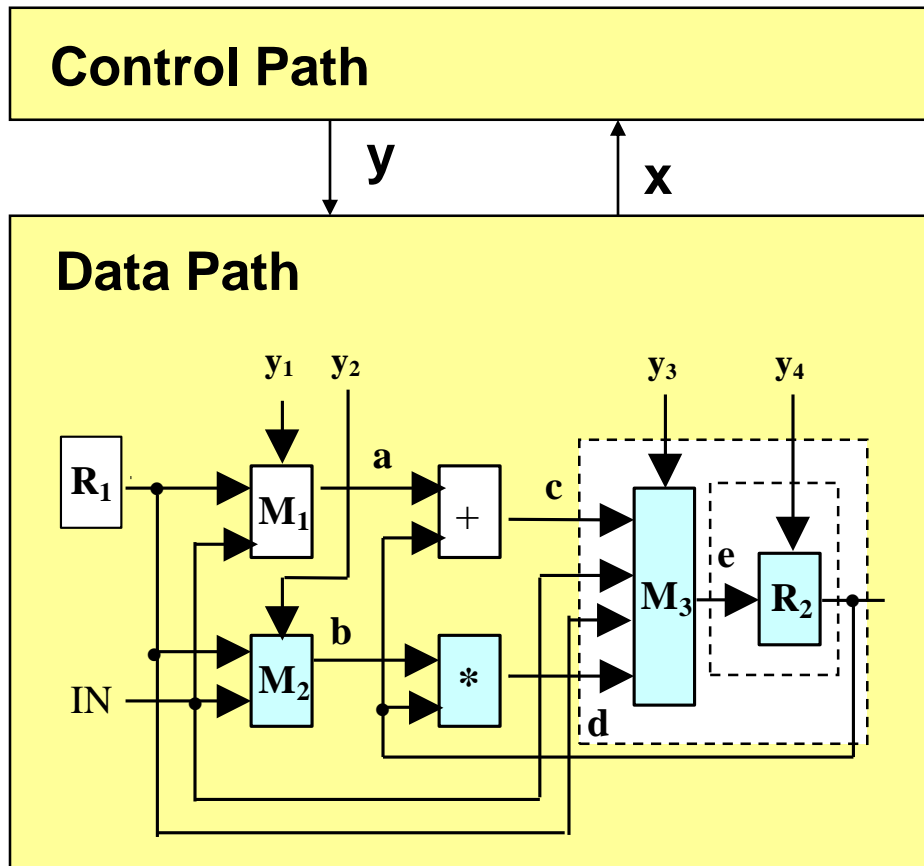

$c(M_1)$		
y_1	Function	
0	$M_1 = R$	
1	$M_1 = IN$	
$d(M_2)$		
y_2	Function	
0	$M_2 = R$	
1	$M_2 = IN$	
$e(M_3)$		
y_3	Function	
0	$M_3 = M_1 + R$	
1	$M_3 = IN$	
2	$M_3 = R$	
3	$M_3 = M_2 * R$	
R		
y_4	Operation	Function
0	Reset	$R_2 = 0$
1	Hold	$R_2 = R_2$
2	Load	$R_2 = M_3$


Data Path: Structural Synthesis of HLDDs

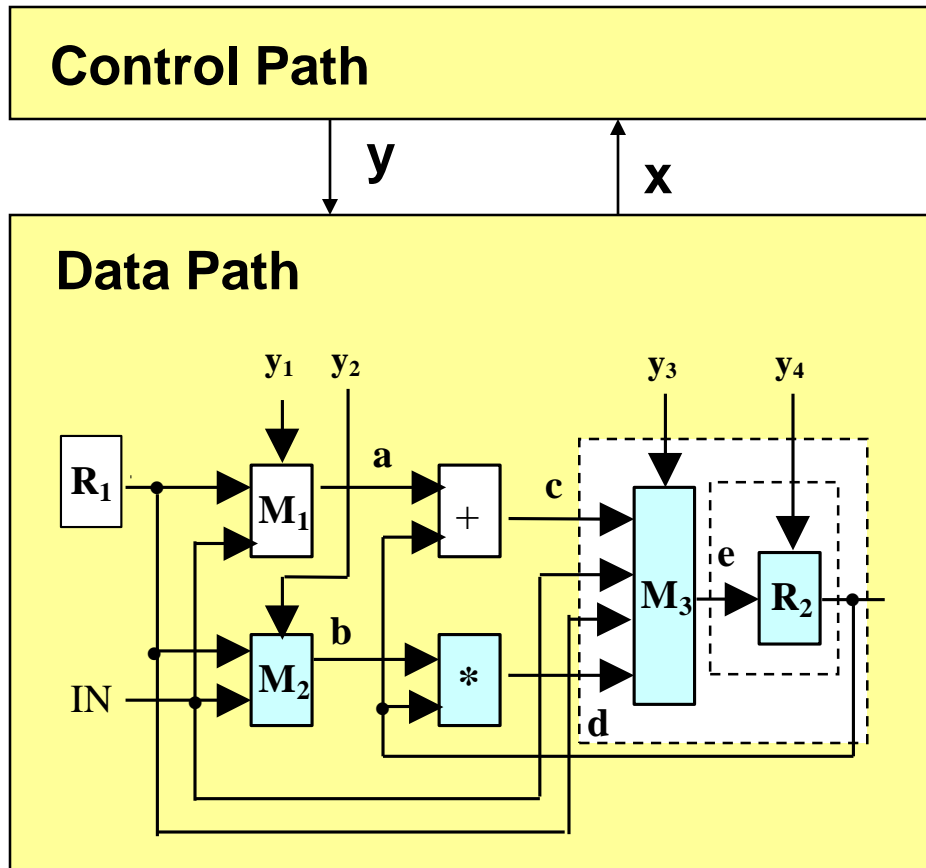


R_2		
y_4	Operator	Function
0	Reset	$R_2 = 0$
1	Hold	$R_2 = R_2$
2	Load	$R_2 = M_3$

Start of the synthesis:

 
Creation of the HLDD for the output subcircuit




Data Path: Structural Synthesis of HLDDs

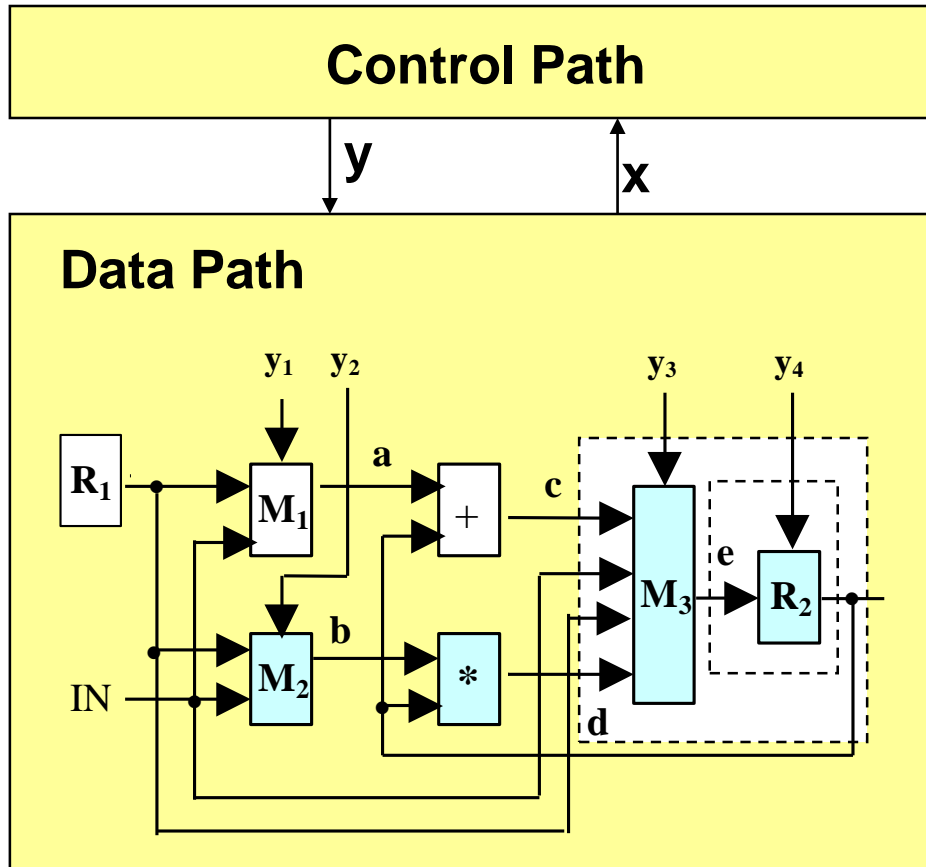


Superposition of the HLDDs

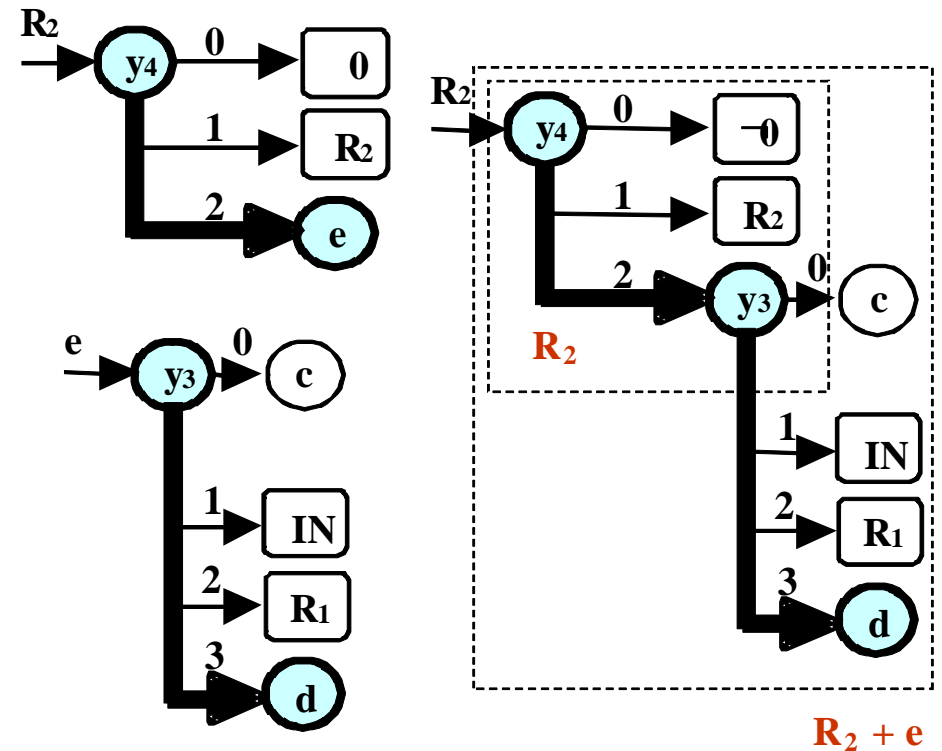

Data Path: Structural Synthesis of HLDDs

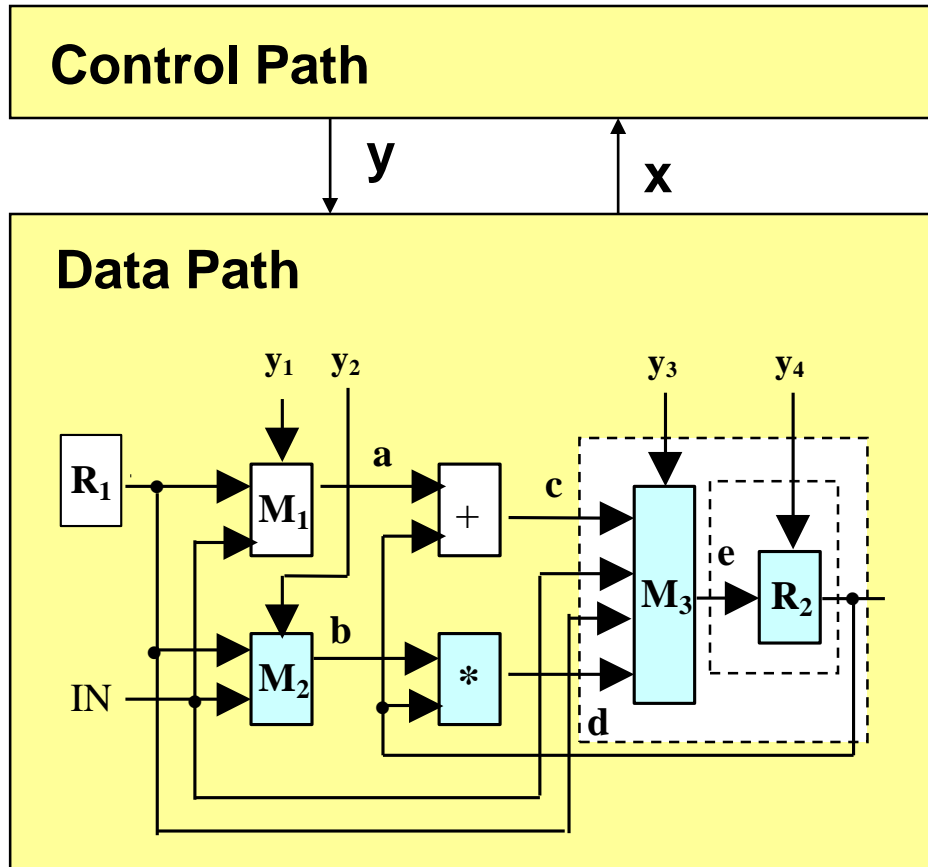

Superposition of the HLDDs


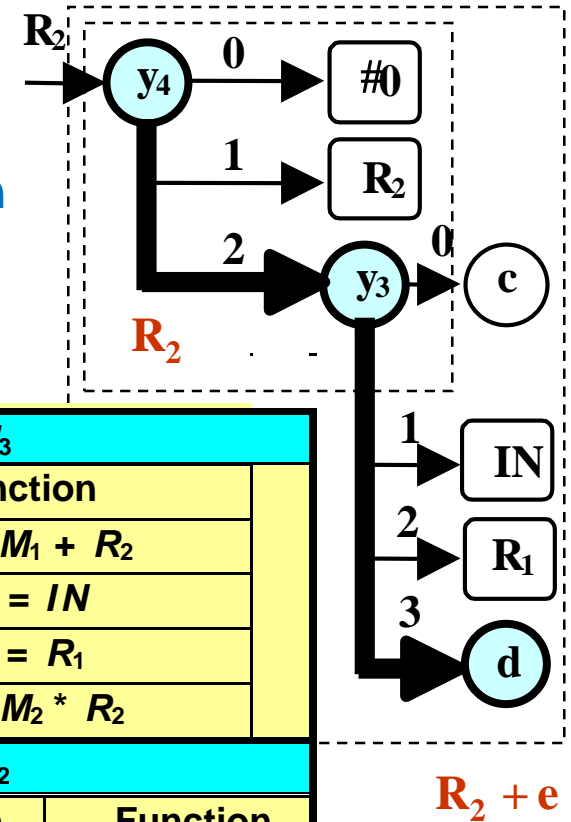


M_3		
y_3	Function	
0	$M_3 = M_1 + R_2$	
1	$M_3 = IN$	
2	$M_3 = R_1$	
3	$M_3 = M_2 * R_2$	
R_2		
y_4	Operation	Function
0	Reset	$R_2 = 0$
1	Hold	$R_2 = R'_2$
2	Load	$R_2 = M_3$

Mapping Between a Circuit and HLDDs

Superposition of the High-Level DDs:

A single DD for a subcircuit

 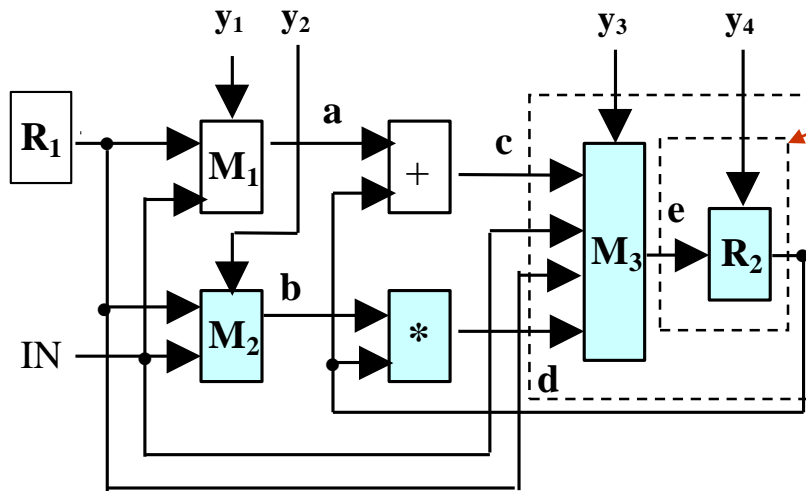


Instead of simulating of all the components in the circuit, **only a single path** in the DD should be traced

Functional Synthesis of High-Level DDs

Data-Flow Diagram

```
IF F0 THEN AC = AC + 1
ELSE
IF F1 THEN
  IF AC = 0
  THEN PC = PC + 1
ELSE
IF F2 THEN
AC = AX, AX = AC
```




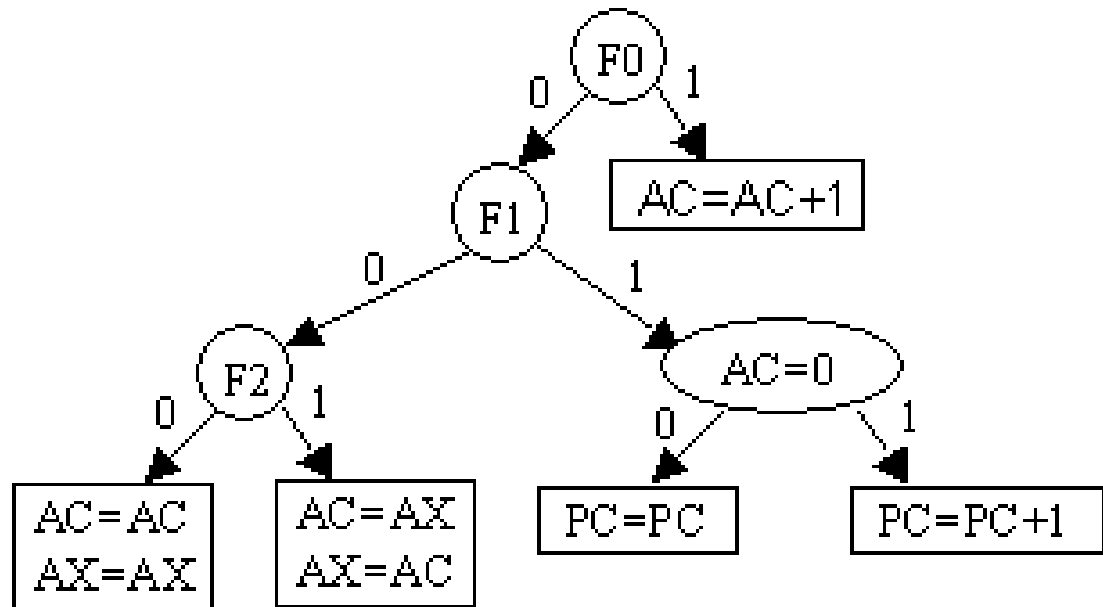
Symbolic execution of the Data-Flow Diagram



Functional Synthesis of High-Level DDs

High-Level DDs can be synthesized by **symbolic execution** of the Data-Flow Diagram:


Decision Diagrams:

  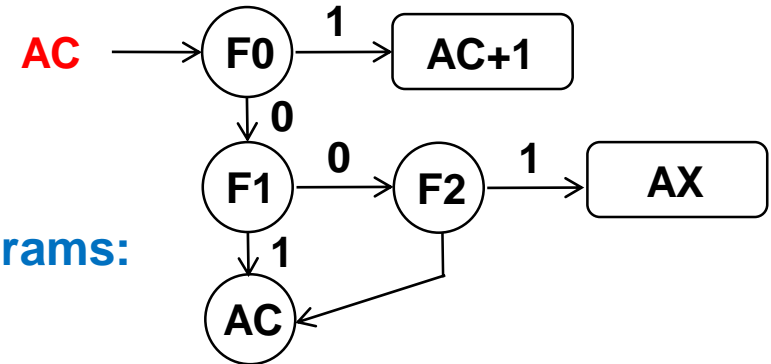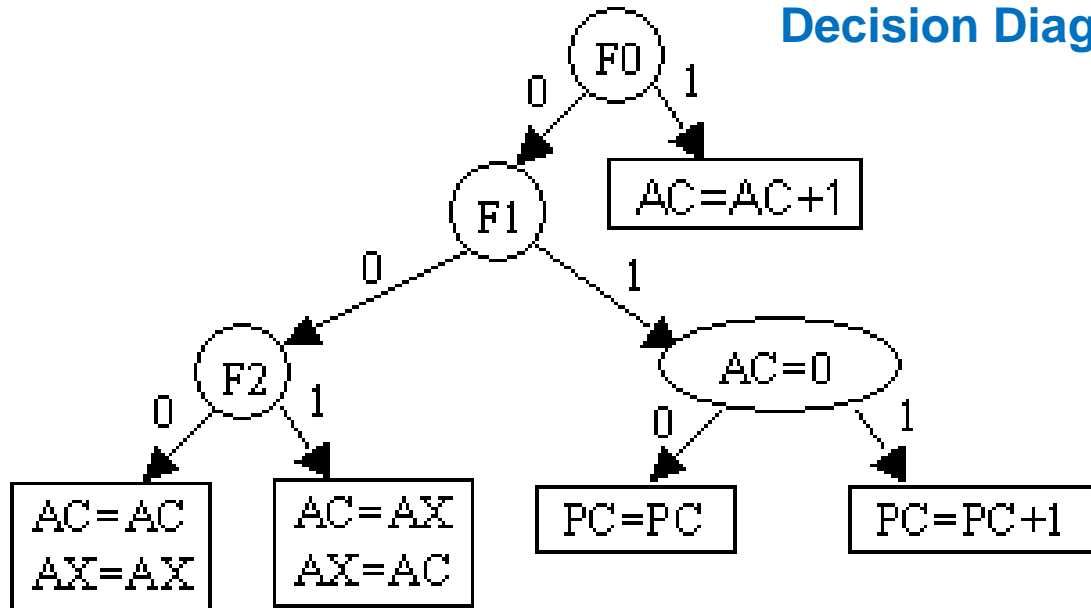


HLDD can be designed for a program written in any language describing either SW or HW

Digital System and Data Flow Diagram

Digital system

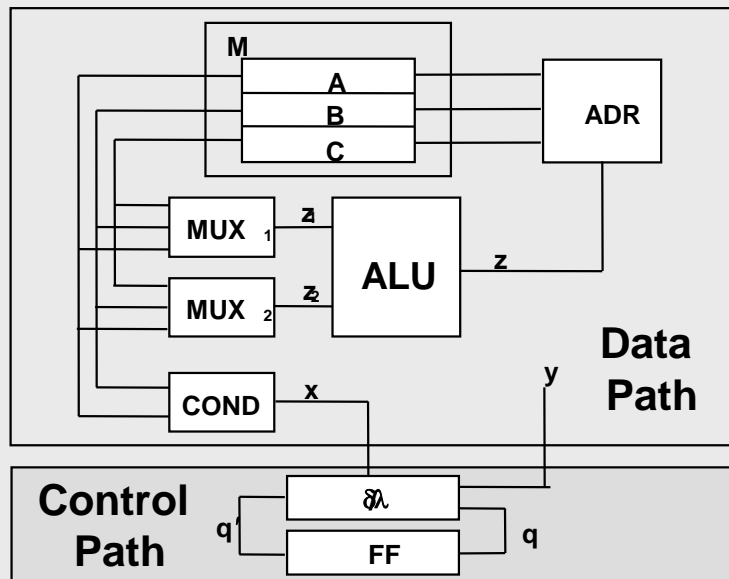


Data Flow Diagram

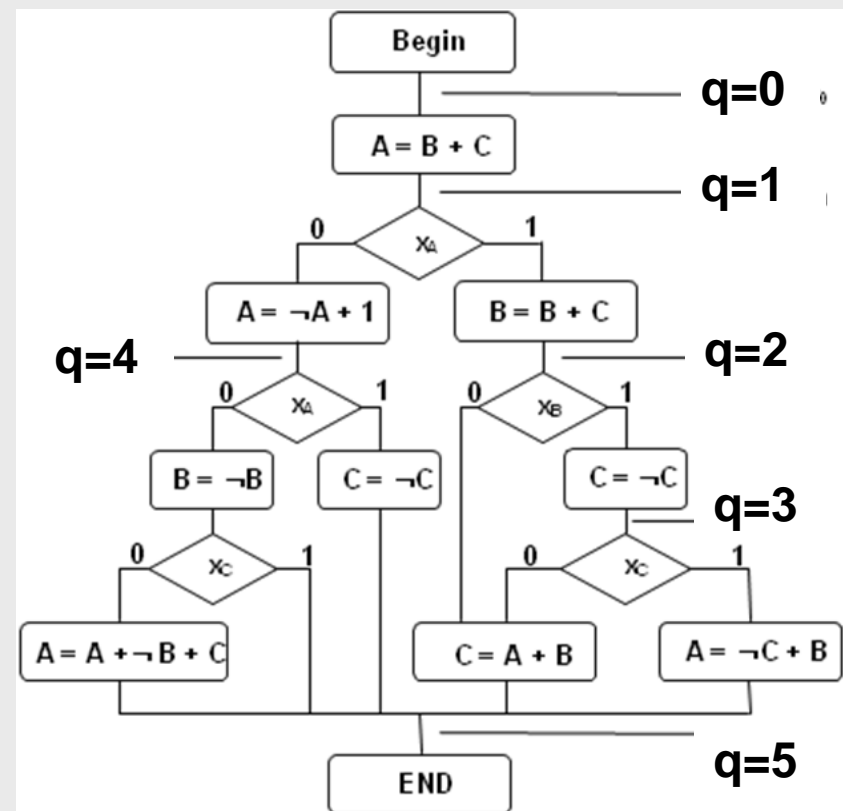

Synthesis of Functional HLDDs

Data Flow Diagram/FSMD

Insertion of states into the diagram

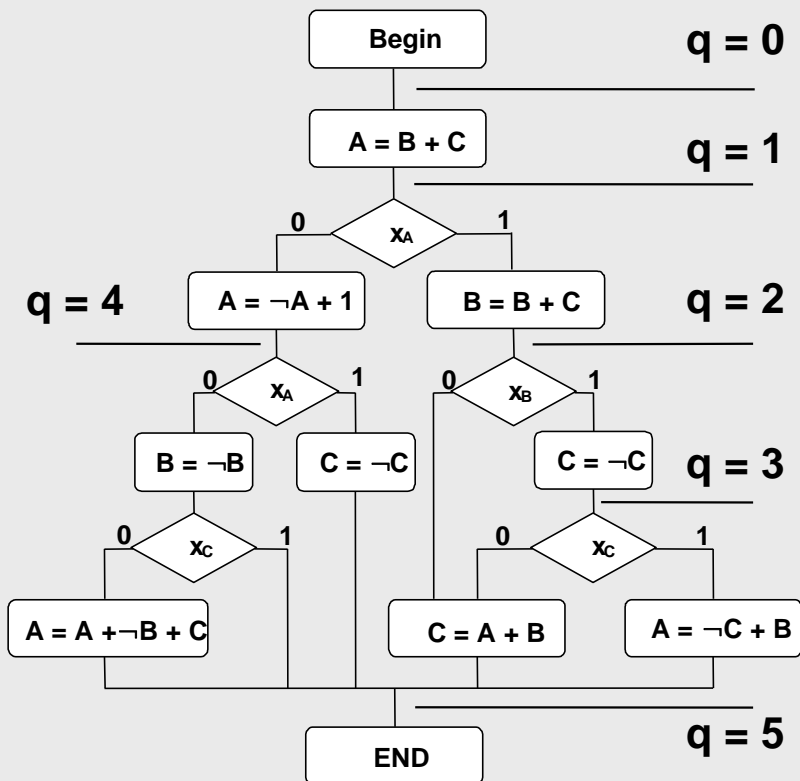

Results of the cycle based symbolic simulation:

Constraints				Assignment statements
q	x_A	x_B	x_C	
0				$A = B + C; q = 1$
1	0			$A = \neg A + 1; q = 4$
1	1			$B = B + C; q = 2$
2		0		$C = A + B; q = 5$
2		1		$C = \neg C; q = 3$
3			0	$C = A + B; q = 5$
3			1	$A = \neg C + B; q = 5$
4	0			$B = \neg B$
4	0		0	$A = A + \neg B + C; q = 5$
4	0		1	$q = 5$
4	1			$C = \neg C; q = 5$

Synthesis of HLDDs

Extraction of the behaviour for A:

Results of symbolic simulation:

Constraints				Assignment statements
q	x _A	x _B	x _C	
0				A = B + C; q = 1
1	0			A = ¬A + 1; q = 4
1	1			B = B + C; q = 2
2		0		C = A + B; q = 5
2		1		C = ¬C; q = 3
3			0	C = A + B; q = 5
3			1	A = ¬C + B; q = 5
4	0			B = ¬B
4	0		0	A = A + ¬B + C; q = 5
4	0		1	q = 5
4	1			C = ¬C; q = 5

q	x _A	x _B	x _C	A
0				B + C
1	0			¬A + 1
3			1	¬C + B
4	0		0	A + ¬B + C

Predicate equation for A:

$$A = f(q, A, B, C, x_A, x_C) =$$

$$= (q=0)(B+C) \vee$$

$$(q=1)(x_A=0)(\neg A + 1) \vee$$

$$(q=3)(x_C=1)(\neg C+B) \vee$$

$$(q=4)(x_A=0)(x_C=0)(A + \neg B + C + 1)$$

Synthesis of HLDDs

Extraction of the behaviour for A:

q	x_A	x_B	x_C	A
0				$B + C$
1	0			$\neg A + 1$
3			1	$\neg C + B$
4	0		0	$A + \neg B + C$


Predicate equation for A:

$$A = (q=0)(B+C) \vee (q=1)(x_A=0)(\neg A + 1) \vee$$

$$(q=3)(x_C=1)(\neg C+B) \vee$$

$$(q=4)(x_A=0)(x_C=0)(A + \neg B + C + 1)$$

Decision diagram for A:

 


Synthesis method: similar to Shannon's expansion theorem:

$$y = F(X) = x_k F(X) \Big|_{x_k=1} \vee \overline{x_k} F(X) \Big|_{x_k=0}$$




Functional HLDDs

Data Flow Diagram

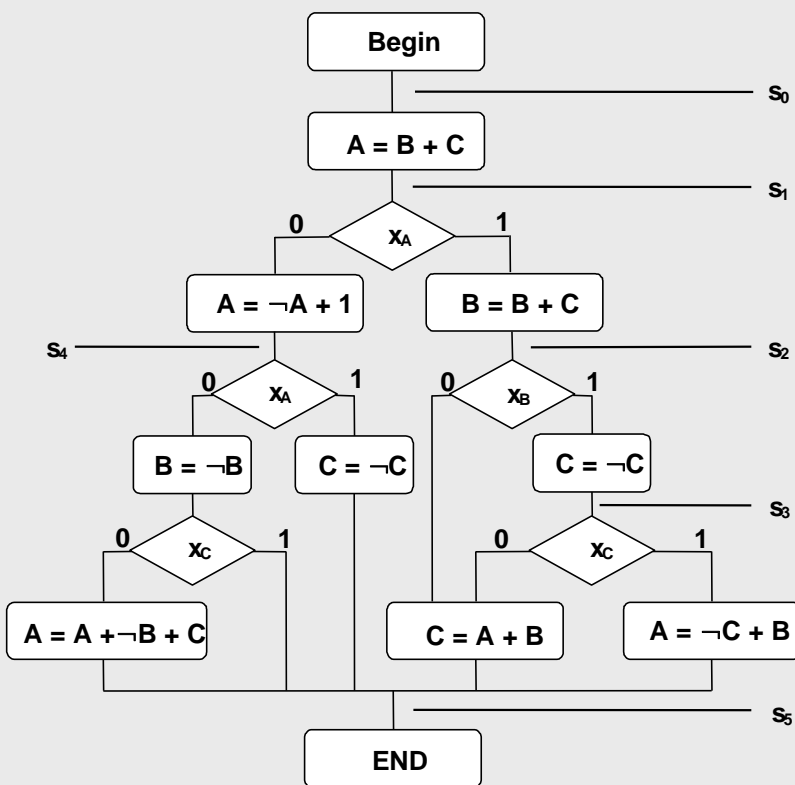


Decision Diagrams

Register variables

  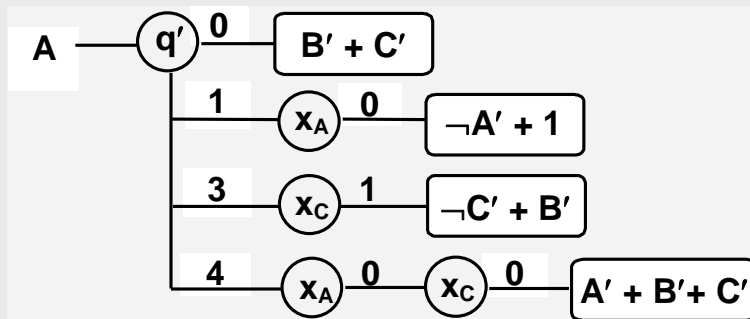


State variable

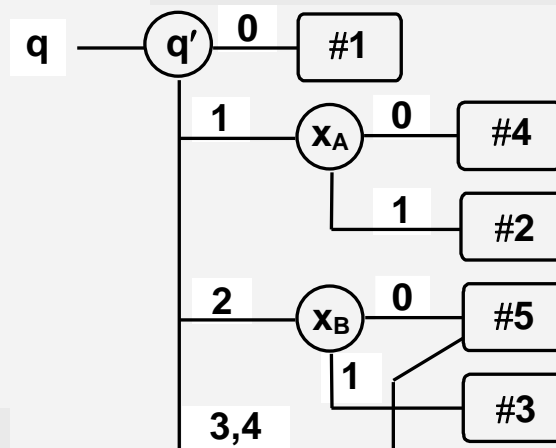


High-Level Vector Decision Diagrams

System with 4 HLDDs

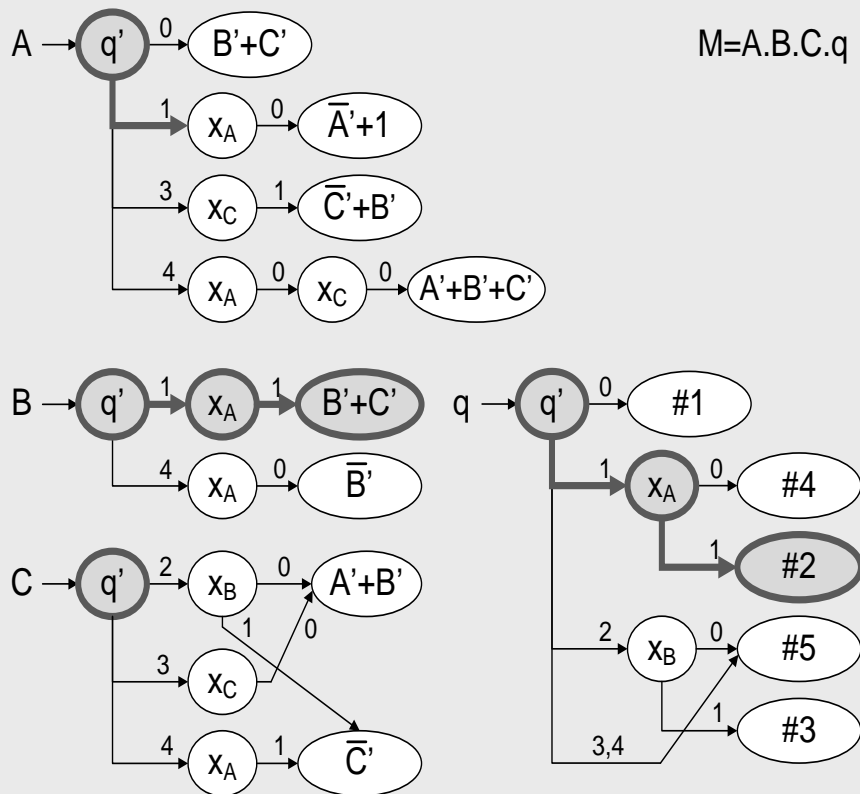


Vector HLDD

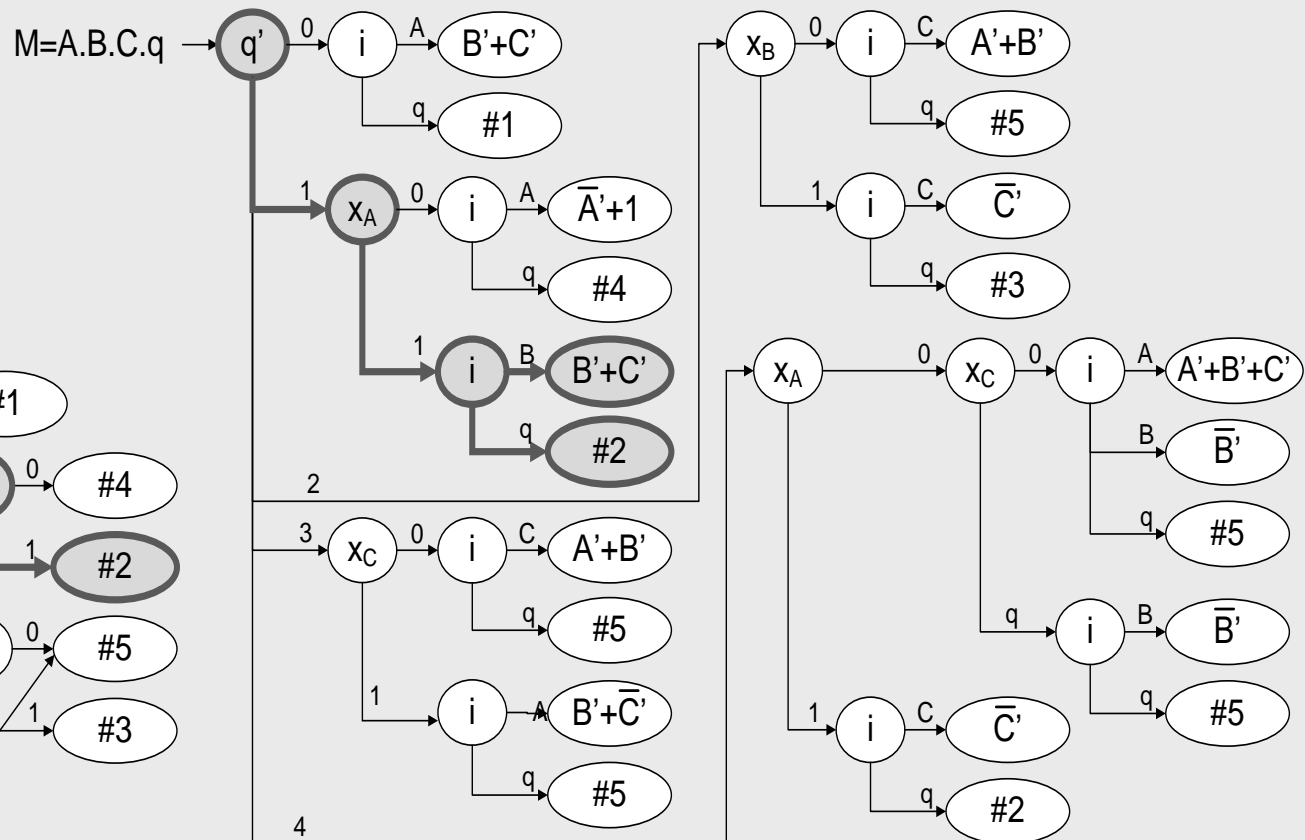


Hierarchical Test Generation with DDs

System:
High-level decision diagram

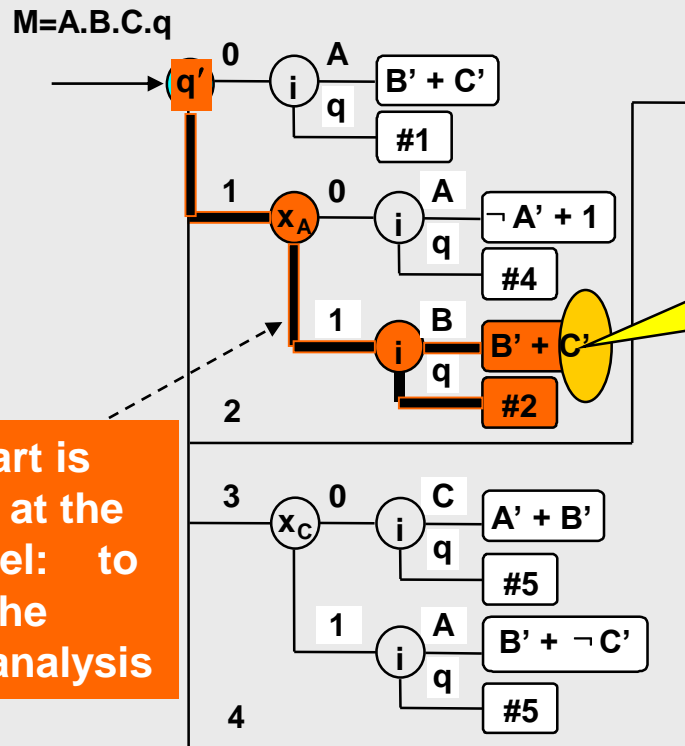

A small part is simulated at the higher level: to increase the speed of analysis

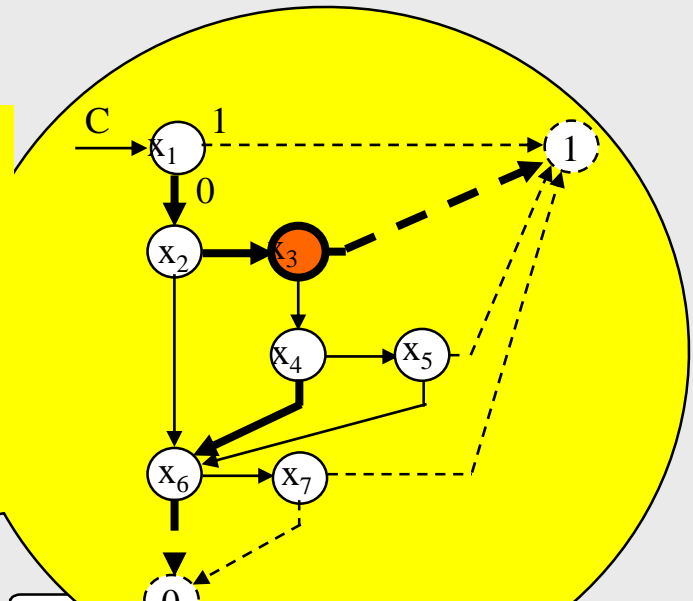
A small part is simulated at the lower level




Cause-effect analysis well formalized

Managing of the Complexity of HL Reasoning

Program data flow

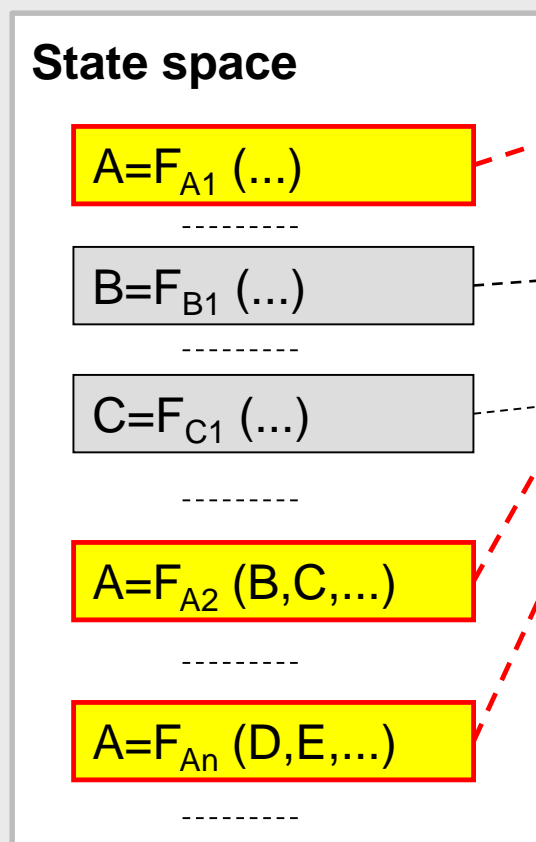

High-Level Decision Diagrams

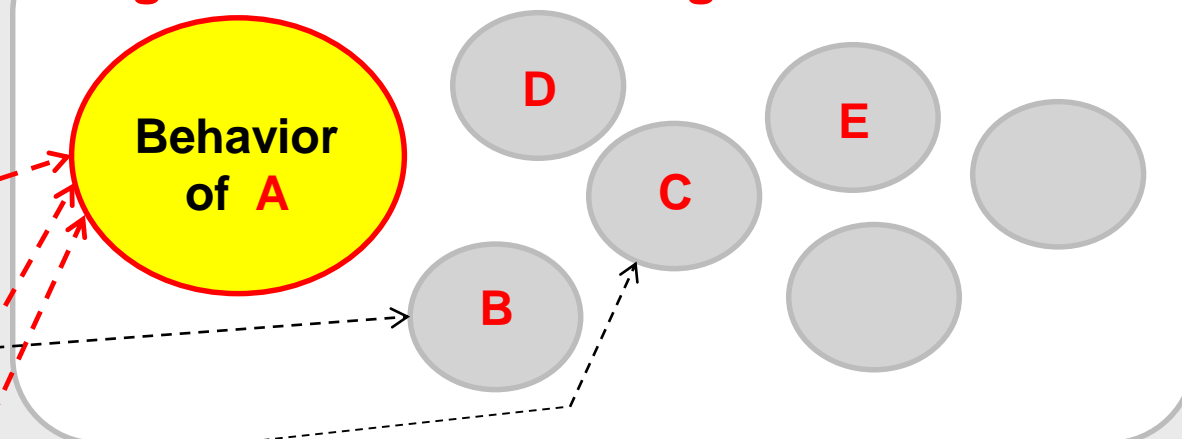

Impact of the HLDDs: Instead of reasoning the design as a whole, it will be partitioned into the behavioral sub-models of functional variables (HLDDs)

DD Synthesis from VHDL Descriptions

VHDL description of 4 processes which represent a simple control unit

```

entity rd_pc is
  port
    ( clk, rst : in bit; rb0 : in bit; enable : in bit; reg_cp : out bit ;
      reg : out bit ; outreg : out bit ; fin : out bit ) ;
end rd_pc ;
architecture archi_rd_pc of rd_pc is type STATETYPE is
  (state1, state2);
  signal state, nstate: STATETYPE ; signal enable_in : bit ;
  signal reg_cp_comb : bit ;
begin
  seq: process(clk, rst)
  begin
    if rst='1' then state <= state1 ;
    elsif (clk'event and clk='1') then state <= nstate ;
    end if ;
  end process ;
  process(clk, enable)
  begin
    if clk='1' then enable_in <= enable ;
    end if ;
  end process ;

```

```

process(clk, reg_cp_comb)
begin
  if clk='0' then reg_cp <= reg_cp_comb ;
  end if ;
end process ;
comb: process (state, rb0, enable_in)
begin
  case state is
    when state1 => outreg <= '0' ; fin <= '0' ;
      if (enable_in='0') then nstate <= state1 ;
        reg <= '1' ; reg_cp_comb <= '0' ;
      else nstate <= state2 ; reg <= '1' ;
        reg_cp_comb <= '1' ;
      end if ;
    when state2 =>
      if (rb0='1') then nstate <= state2 ; reg <= '0' ;
        reg_cp_comb <= '1' ; outreg <= '0' ; fin <= '0' ;
      elsif (enable_in='0') then nstate <= state1 ; reg <= '0' ;
        reg_cp_comb <= '0' ; outreg <= '1' ; fin <= '1' ;
      else nstate <= state2 ; reg <= '0' ;
        reg_cp_comb <= '0' ; outreg <= '0' ; fin <= '1' ;
      end if ;
    end case ;
  end process ;
end archi_rd_pc ;

```

Synthesis of HLDDs from VHDL

```

entity rd_pc is
  port
    ( clk, rst : in bit; rb0 : in bit; enable : in bit; reg_cp : out bit ;
      reg : out bit ; outreg : out bit ; fin : out bit ) ;
end rd_pc ;
architecture archi_rd_pc of rd_pc is type STATETYPE is
  (state1, state2);
  signal state, nstate: STATETYPE ; signal enable_in : bit ;
  signal reg_cp_comb : bit ;

```

```

begin
  seq: process(clk, rst)
  begin
    if rst='1' then state <= state1 ;
    elsif (clk'event and clk='1') then state <= nstate ;
    end if ;
  end process ;



```

```

process(clk, enable)
begin
  if clk='1' then enable_in <= enable ;
  end if ;
end process ;

```

DDs for state, enable_in and nstate

 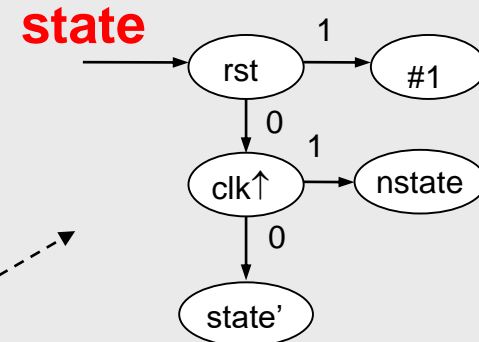


Synthesis of HLDDs from VHDL

```

process(clk, reg_cp_comb)
begin
  if clk='0' then reg_cp <= reg_cp_comb ;
  end if ;
end process ;
comb: process (state, rb0, enable_in)
begin
  case state is
    when state1 => outreg <= '0' ; fin <= '0' ;
      if (enable_in='0') then nstate <= state1 ;
        reg <= '1' ; reg_cp_comb <= '0' ;
      else nstate <= state2 ; reg <= '1' ;
        reg_cp_comb <= '1' ;
      end if ;
    when state2 =>
      if (rb0='1') then nstate <= state2 ; reg <= '0' ;
        reg_cp_comb <= '1' ; outreg <= '0' ; fin <= '0' ;
      elsif (enable_in='0') then nstate <= state1 ; reg <= '0' ;
        reg_cp_comb <= '0' ; outreg <= '1' ; fin <= '1' ;
      else nstate <= state2 ; reg <= '0' ;
        reg_cp_comb <= '0' ; outreg <= '0' ; fin <= '1' ;
      end if ;
  end case ;
end process ;
end archi_rd_pc ;

```

 

Synthesis of HLDDs from VHDL

```

entity rd_pc is
  port
    ( clk, rst : in bit; rb0 : in bit; enable : in bit; reg_cp : out bit ;
      reg : out bit ; outreg : out bit ; fin : out bit ) ;
end rd_pc ;
architecture archi_rd_pc of rd_pc is type STATETYPE is
  (state1, state2);
  signal state, nstate: STATETYPE ; signal enable_in : bit ;
  signal reg_cp_comb : bit ;

```

```

begin
  seq: process(clk, rst)
  begin
    if rst='1' then state <= state1 ;
    elsif (clk'event and clk='1') then state <= nstate ;
    end if ;
  end process ;




```

```

process(clk, enable)
begin
  if clk='1' then enable_in <= enable ;
  end if ;
end process ;

```

DDs for state, enable_in and nstate

  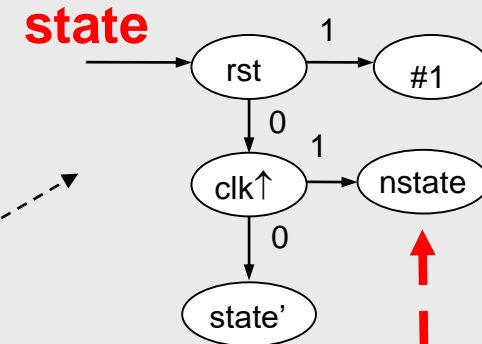


Synthesis of HLDDs from VHDL


```

process(clk, reg_cp_comb)
begin
  if clk='0' then reg_cp <= reg_cp_comb ;
  end if ;
end process ;
comb: process (state, rb0, enable_in)
begin
  case state is
    when state1 => outreg <= '0' ; fin <= '0' ;
      if (enable_in='0') then nstate <= state1 ;
        reg <= '1' ; reg_cp_comb <= '0' ;
      else nstate <= state2 ; reg <= '1' ;
        reg_cp_comb <= '1' ;
      end if ;
    when state2 =>
      if (rb0='1') then nstate <= state2 ; reg <= '0' ;
        reg_cp_comb <= '1' ; outreg <= '0' ; fin <= '0' ;
      elsif (enable_in='0') then nstate <= state1 ; reg <= '0' ;
        reg_cp_comb <= '0' ; outreg <= '1' ; fin <= '1' ;
      else nstate <= state2 ; reg <= '0' ;
        reg_cp_comb <= '0' ; outreg <= '0' ; fin <= '1' ;
      end if ;
  end case ;
end process ;
end archi_rd_pc ;
  
```

HLDD model for the **Control Unit**

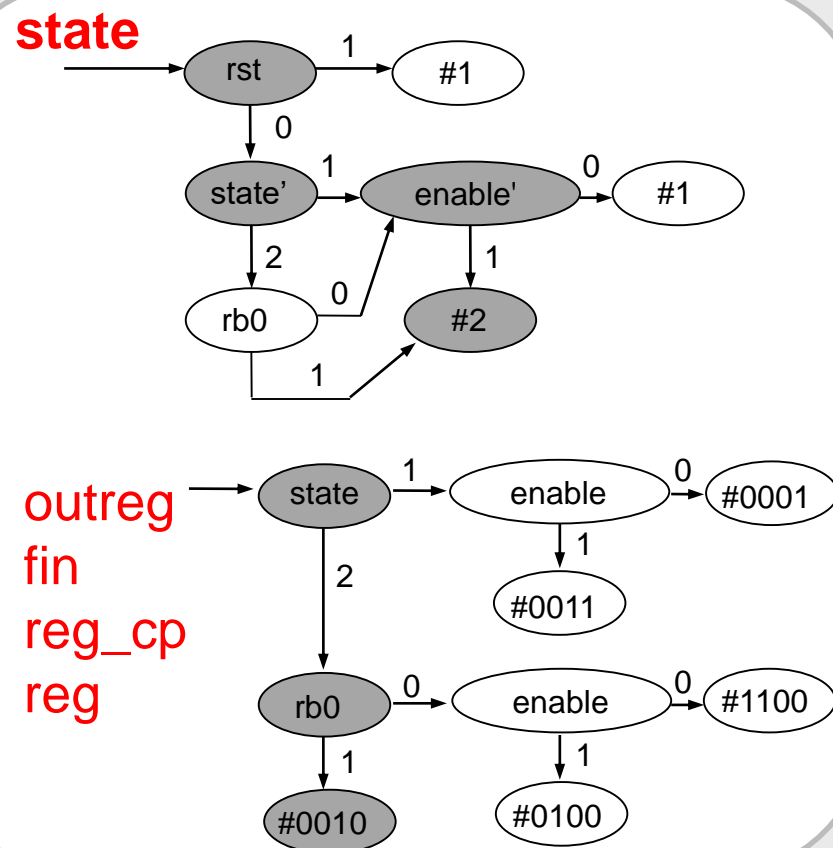

Simulation & Fault Backtracing with HLDD

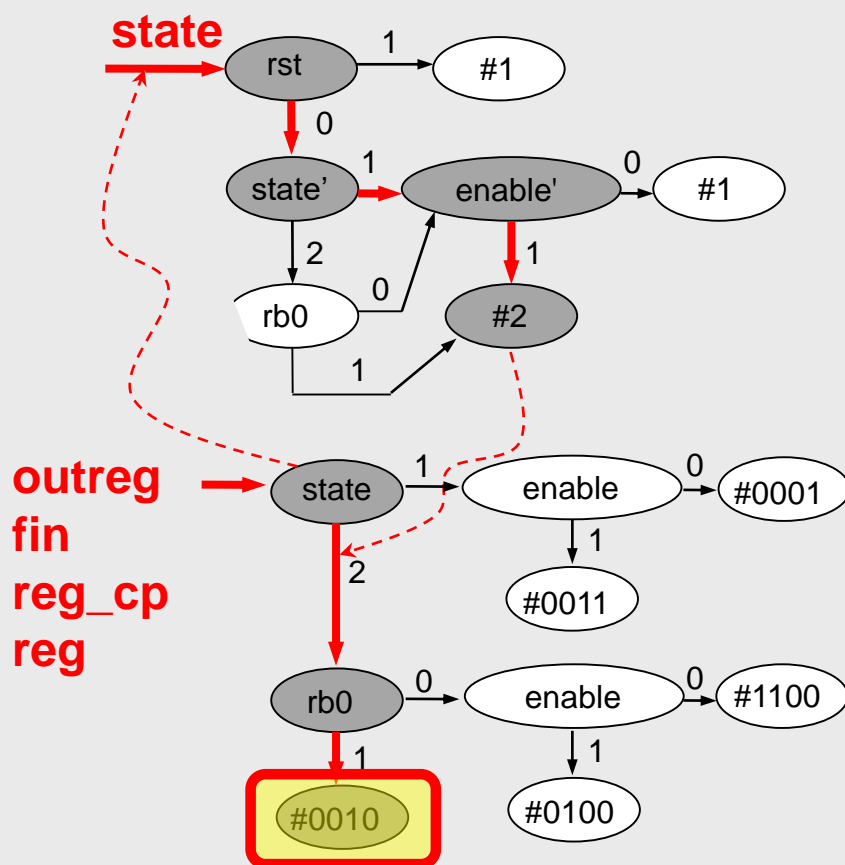

Inputs

time	1	2	3	4	5	6
rst	1	0	0	0	0	0
enable	0	1	1	1	0	0
rb0	x	x	1	0	0	0
state	1	1	2	2	2	1
outreg	0	0	0	0	1	0
fin	0	0	0	1	1	0
reg_cp	0	1	1	0	0	0
reg	1	1	0	0	0	1

Outputs

Simulated vector

Motivations for High-Level Fault Models

Current State-of-the-Art:

- The efficiency of test generation (quality, speed) is highly depending on
 - the description method (level, language), and
 - fault models
- Because of the growing complexity of systems, gate level methods have become obsolete
- High-Level methods for diagnostic modeling are today emerging, however they are not still mature

Main disadvantages:

- The known methods for fault modeling are
 - dedicated to special classes (i.e. for microprocessors, for RTL, VHDL etc. languages...), not general
 - not well defined and formalized

State of Art: Microprocessor Fault Model

Source decoding (MUX):

- F1: no source is selected
- F2: wrong source is selected;
- F3: more than one source is selected and the multiplexer output is either a wired-AND or a wired-OR function of the sources, depending on the technology.

Destination decoding (DMUX)

- F4: no destination is selected
- F5: instead of, or in addition to the selected correct destination, one or more other destinations selected

Instruction exec. faults

- F6: one or more microorders not activated
- F7: microorders are erroneously activated
- F8: a different set of micro-instructions is activated instead of, or in addition to

Data storage/bus/ALU faults:

- F9: one or more cells SAF0 /1;
- F10: one or more cells fail 0→1/1→0
- F11: two or more cells coupled;
- F12: one or more lines SAF0 /1;
- F13: one or more lines wired-OR/AND
- F14: data manipulation faults

Register Level Fault Models

RTL statement:

$$K: (If\ T, C) \ R_D \leftarrow F(R_{S1}, R_{S2}, \dots R_{Sm}), \rightarrow N$$

Components (variables)
of the statement:

K	- label
T	- timing condition
C	- logical condition
R_D	- destination register
R_S	- source register
F	- operation (microoperation)
\leftarrow	- data transfer
$\rightarrow N$	- jump to the next statement



RT level faults:

$K \rightarrow K'$	- label faults
$T \rightarrow T'$	- timing faults
$C \rightarrow C'$	- logical condition faults
$R_D \rightarrow R_D$	- register decoding faults
$R_S \rightarrow R_S$	- data storage faults
$F \rightarrow F'$	- operation decoding faults
\leftarrow	- data transfer faults
$\rightarrow N$	- control faults
$(F) \rightarrow (F)'$	- data manipulation faults

Universal Functional Fault Models

Exhaustive combinational fault model:

  - exhaustive test patterns
- pseudoexhaustive test patterns
 - exhaustive output line oriented test patterns
 - exhaustive module oriented test patterns



Hierarchical test generation:

Fault Models for High-Level Components

Decoder:

- instead of correct line, incorrect is activated
- in addition to correct line, additional line is activated
- no lines are activated

Multiplexer (n inputs $\log_2 n$ control lines):

- stuck-at - 0 (1) on inputs
- another input (instead of, additional)
- value, followed by its complement
- **value, followed by its complement on a line whose address differs in 1 bit**

Memory fault models:

- one or more cells stuck-at - 0 (1)
- two or more cells coupled


Fault Model vs. Test Description

Dedicated functional fault model for multiplexer:

- stuck-at-0 (1) on inputs,
 - another input (instead of, additional)
 - value, followed by its complement
- value, followed by its complement on a line whose address differs in one bit


Functional fault model

Test description

 

This functional model corresponds to two SAF models for all bit-slices in the MUX-circuit

Hierarchical Test Generation

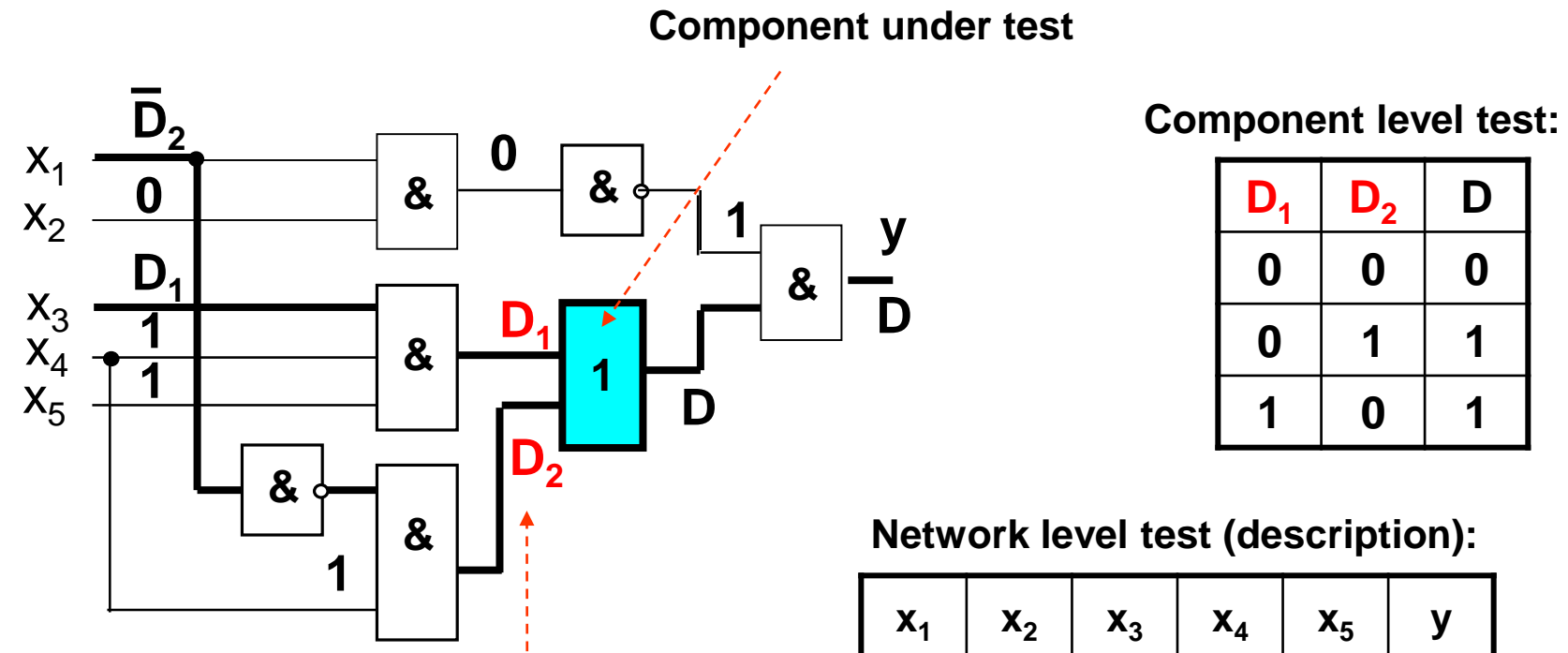

Input pattern – as a fault model

Symbolic test: contains 3 patterns

Network level test (description):


x_1	x_2	x_3	x_4	x_5	y
$\overline{D_2}$	0	D_1	1	1	D

Fault model (embedded in the test description)

Generalization of BDDs


Binary DD

 2 terminal nodes and
2 edges from each node



General case of DD

 $n \geq 2$ terminal nodes and
 $n \geq 2$ edges from each node



Novelty: Boolean methods can be generalized in a straightforward way to higher functional levels

HLDDs and Faults

RTL-statement:

$$K: (If T,C) R_D \leftarrow F(R_{S1}, R_{S2}, \dots, R_{Sm}), \rightarrow N$$

Nonterminal nodes



RTL-statement faults:

label,
timing condition,
logical condition,
register decoding,
operation decoding,
control faults

Terminal nodes

RTL-statement faults:

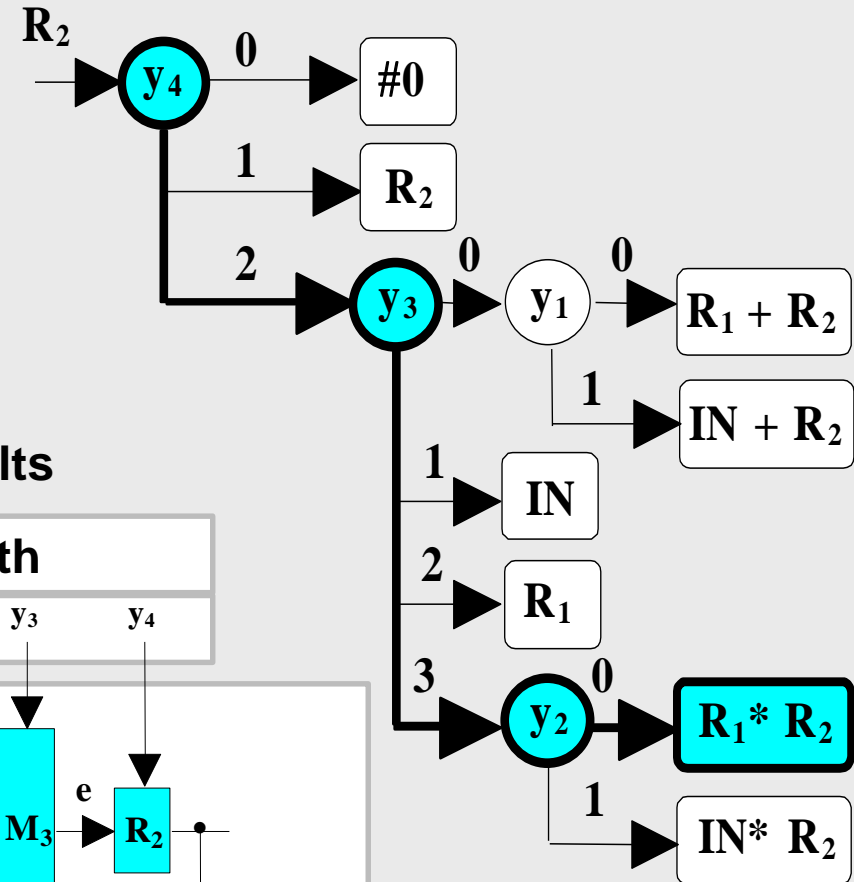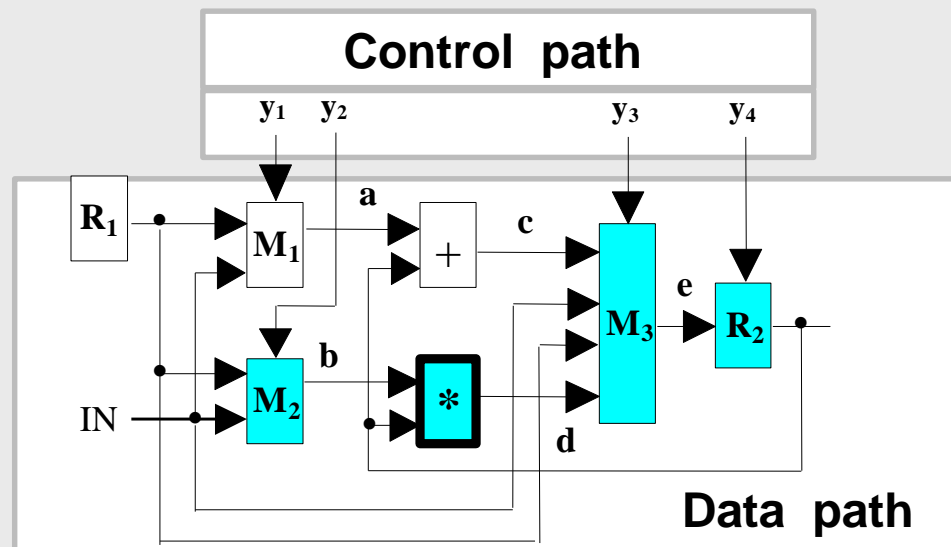data storage,
data transfer,
data manipulation faults



From Trad. MP Fault Model to HLDD Faults


Each path in a DD represents a **working mode** of the system
 The **faults** having effect on the behaviour can be associated with nodes **along the path**

D1: node output is **always activated (SAF-1)**

D2: node output is **broken (SAF-0)**

D3: instead of the given output **another output set is activated**


 
Instead of the 14 fault classes, the HLDD based fault model includes only 3 fault classes



based

Fault Collapsing with SSBDDs

  Each node in SSBDD represents a signal path:




Two SSBDD faults $x_{11} \equiv 1$, $x_{11} \equiv 0$ represent a set of six faults in the circuit:

$$\{x_{11} \equiv 1, x_6 \equiv 1, y \equiv 1; x_{11} \equiv 0, x_6 \equiv 0, y \equiv 0\}$$


Fault Collapsing with Structural HLDDs

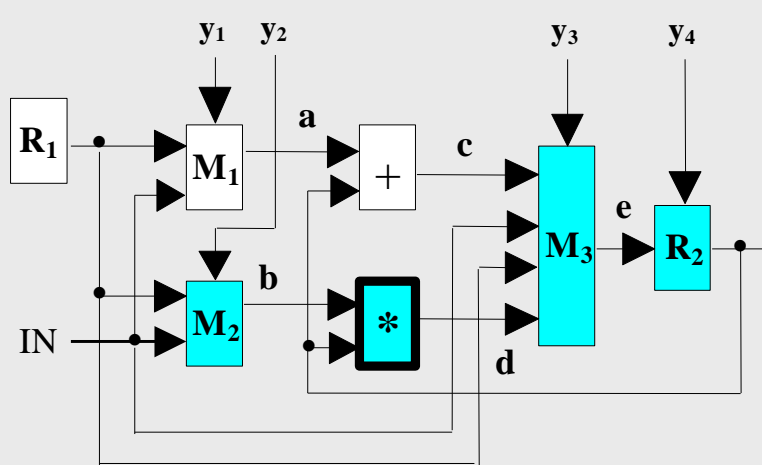Each node in SSBDD represents a signal path:



The faults at y_3 in HLDD represent the faults in the control circuitry and in the multiplexer M3 of the RTL circuit

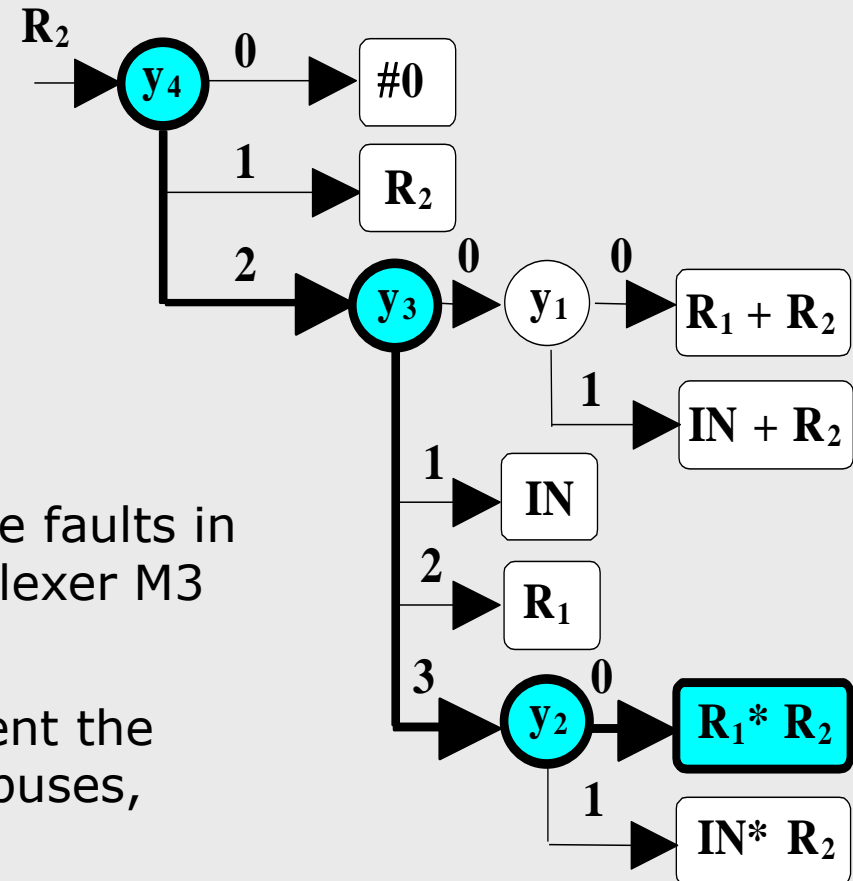The faults at $R1 * R2$ in HLDD represent the faults in multiplier, input and output buses, and in the registers




Fault collapsing – not investigated at high-level


Fault Activation in Digital Systems

Multiple paths activation in a DD

Control function y_3 is tested

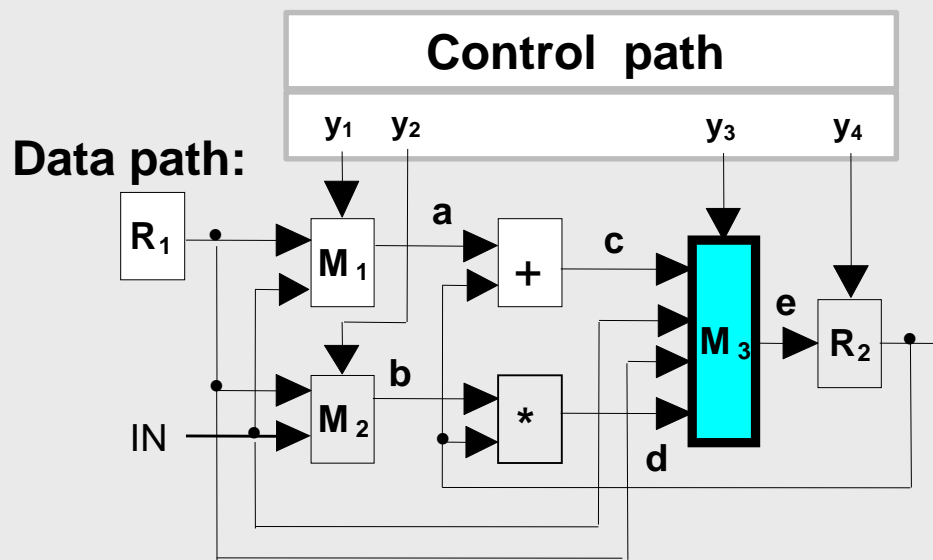

Decision Diagram

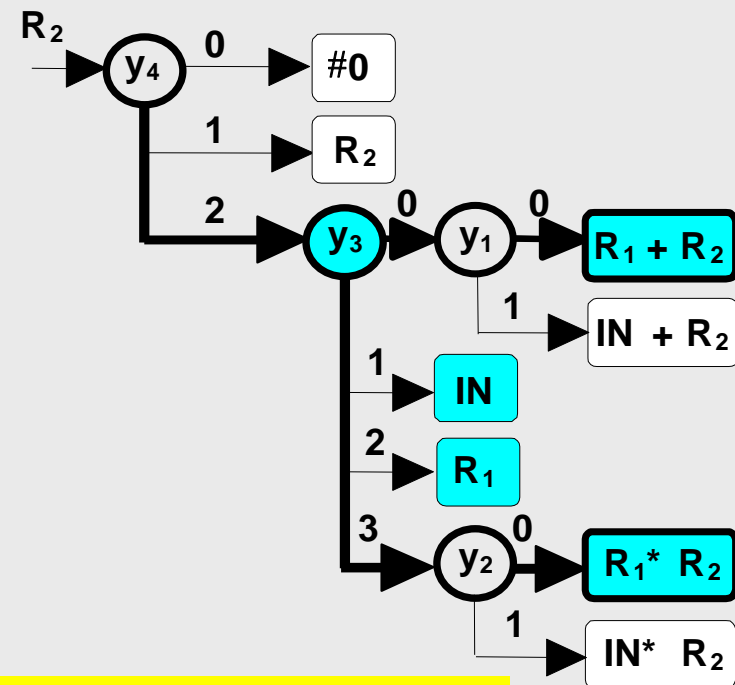


Test cycle:

Control: For $D = 0, 1, 2, 3$: $y_1 y_2 y_3 y_4 = 00D2$

Data: Solution of $R_1 + R_2 \neq IN \neq R_1 \neq R_1 * R_2$

Uniform Conditional Node Fault Model

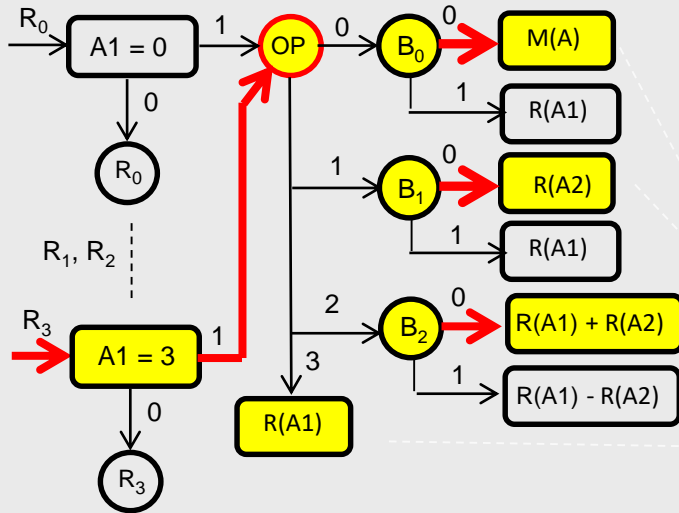

Test data calculation rules:


$$\forall m^T \in M^T(OP): [f(m^T) \neq \text{ZERO}]$$

$$\forall m_i, m_j \in M^T(OP): [(f(m_i) < f(m_j))]$$

Terminal nodes:

$$M^T(OP) = \{M(A), R(A2), R(A1)+R(A2), R(A1)\}$$

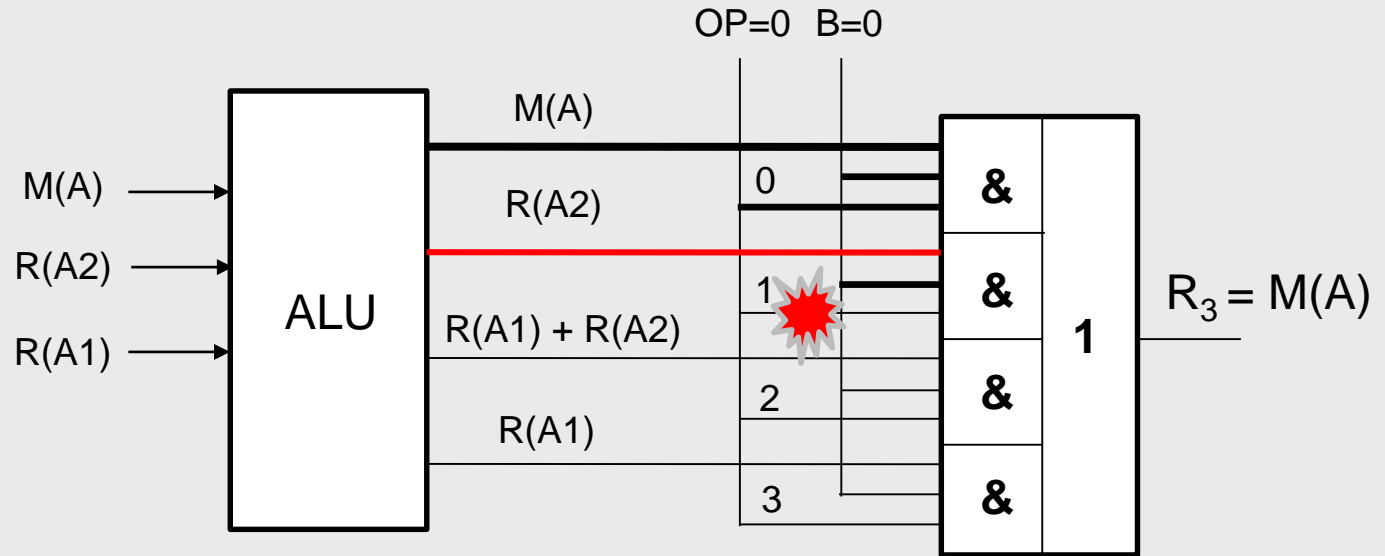Explanation of the meaning of constraints (rules):




To detect the fault: $R_3 = M(A) \vee R(A2) \longrightarrow M(A) < R(A2)$ is needed


Uniform Conditional Node Fault Model

Logic level analog:
Conditional SAF model

Condition
(constraint)

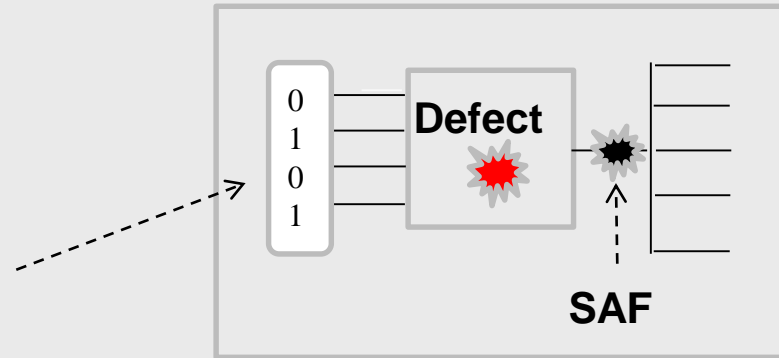

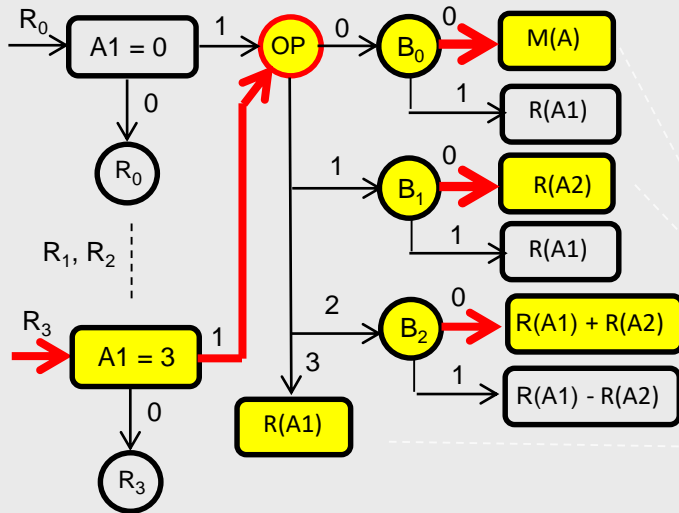High level analog: Constraints for testing a node *OP* in HLDD:



High-level fault model:

Test data calculation rules:

$$\forall m^T \in M^T(OP): [f(m^T) \neq \text{ZERO}]$$


$$\forall m_i, m_j \in M^T(OP): [(f(m_i) < f(m_j))]$$

Terminal nodes:

$$M^T(OP) = \{M(A), R(A2), R(A1)+R(A2), R(A1)\}$$

Multi-Terminal BDDs

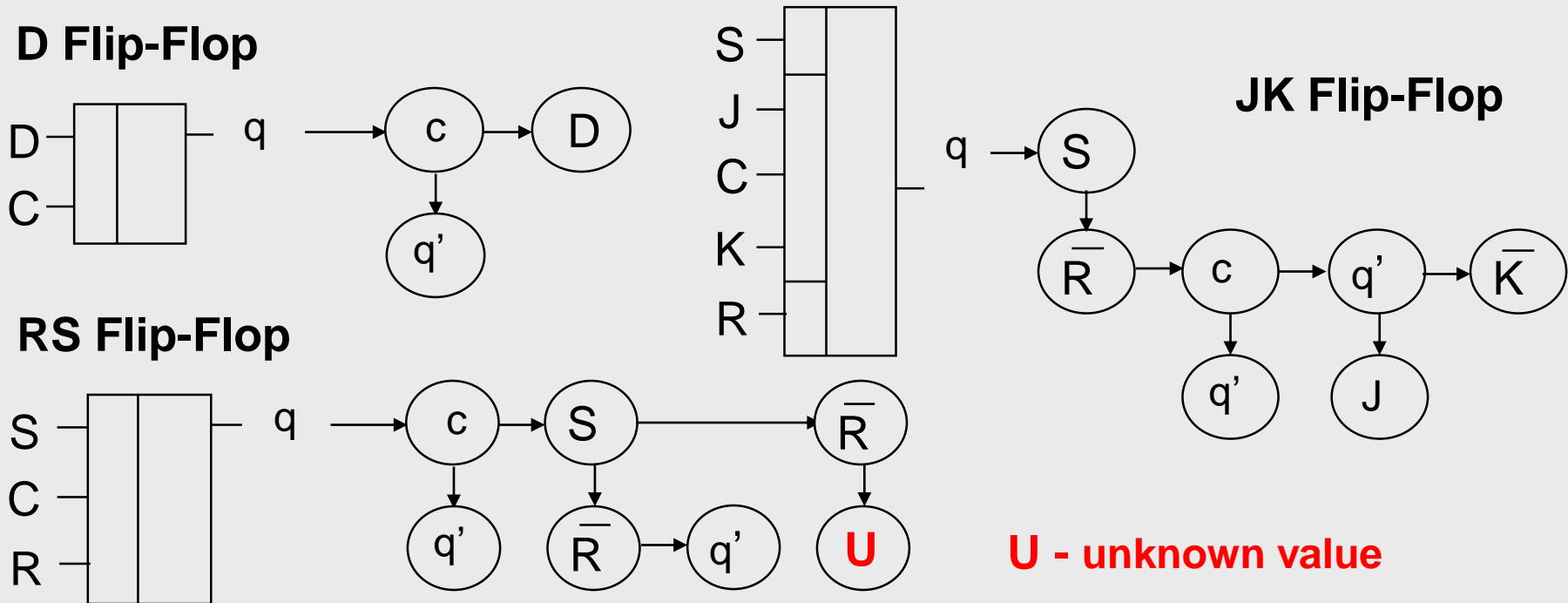Multi-Terminal BDDs for representing uncertainties:





$$q = c(S \vee q' \bar{R}) \vee \bar{c} q'$$

$$SR = 0$$

Generalization of MTBDDs for FSMs

State Transition Diagram:

  


New features:

- ✓ representing vectors (vector DD)
- ✓ multi-output internal nodes
- ✓ multi-terminal DDs

HLDDs for MP InstrSet

Behavioral level variables of MP

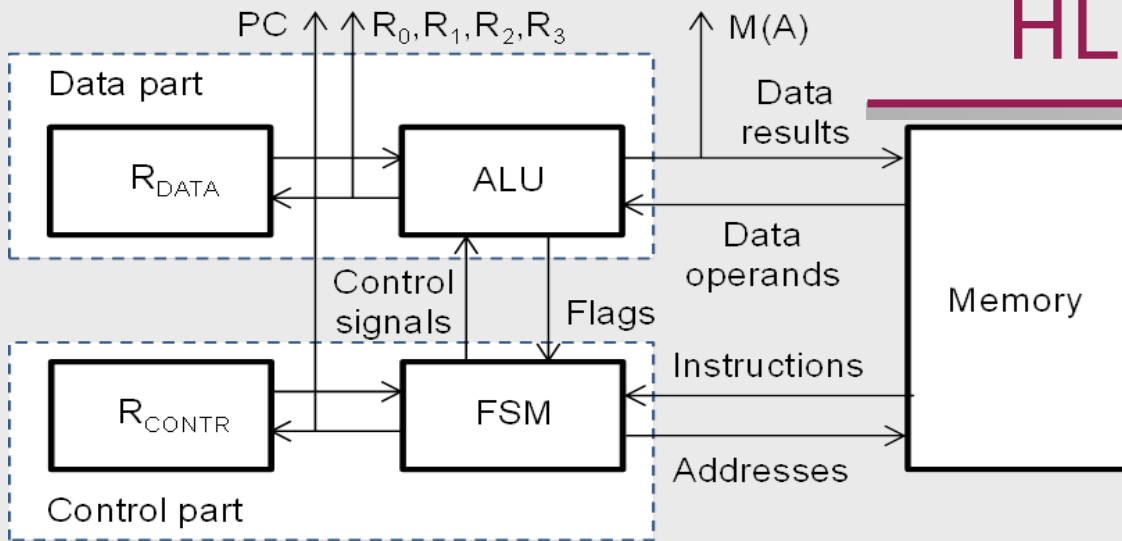


Instruction code:
 ADD A1 A2
 OP=2. B=0. A1=3. A2=2


$$R_3 = R_3 + R_2$$

$$PC = PC + 1$$


Program Counter

 

Registers and ALU

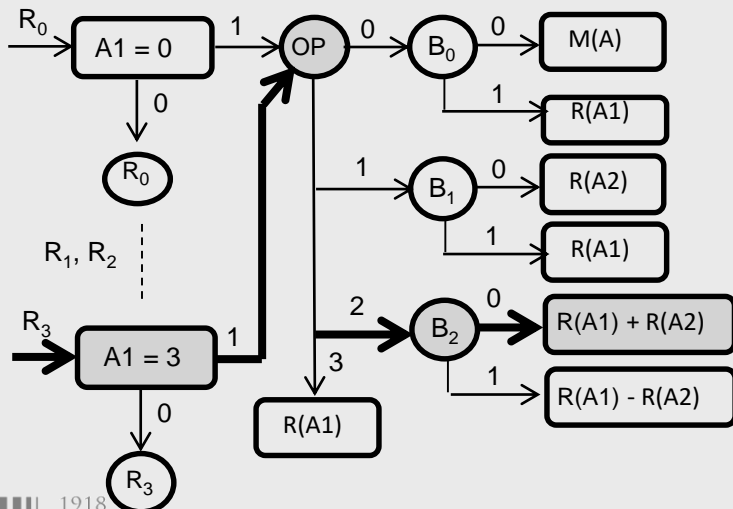

Register Decoding

 

Memory Access

