

# Süsteemide diagnostika

---

## **3. Rikete modelleerimine**


### **3.1. Rikete klassifikatsioon**

### **3.2. Loogikatasandi konstantrikked**

### **3.3. Tingimuslikud rikked**

### **3.4. Kõrgtasandi rikked**
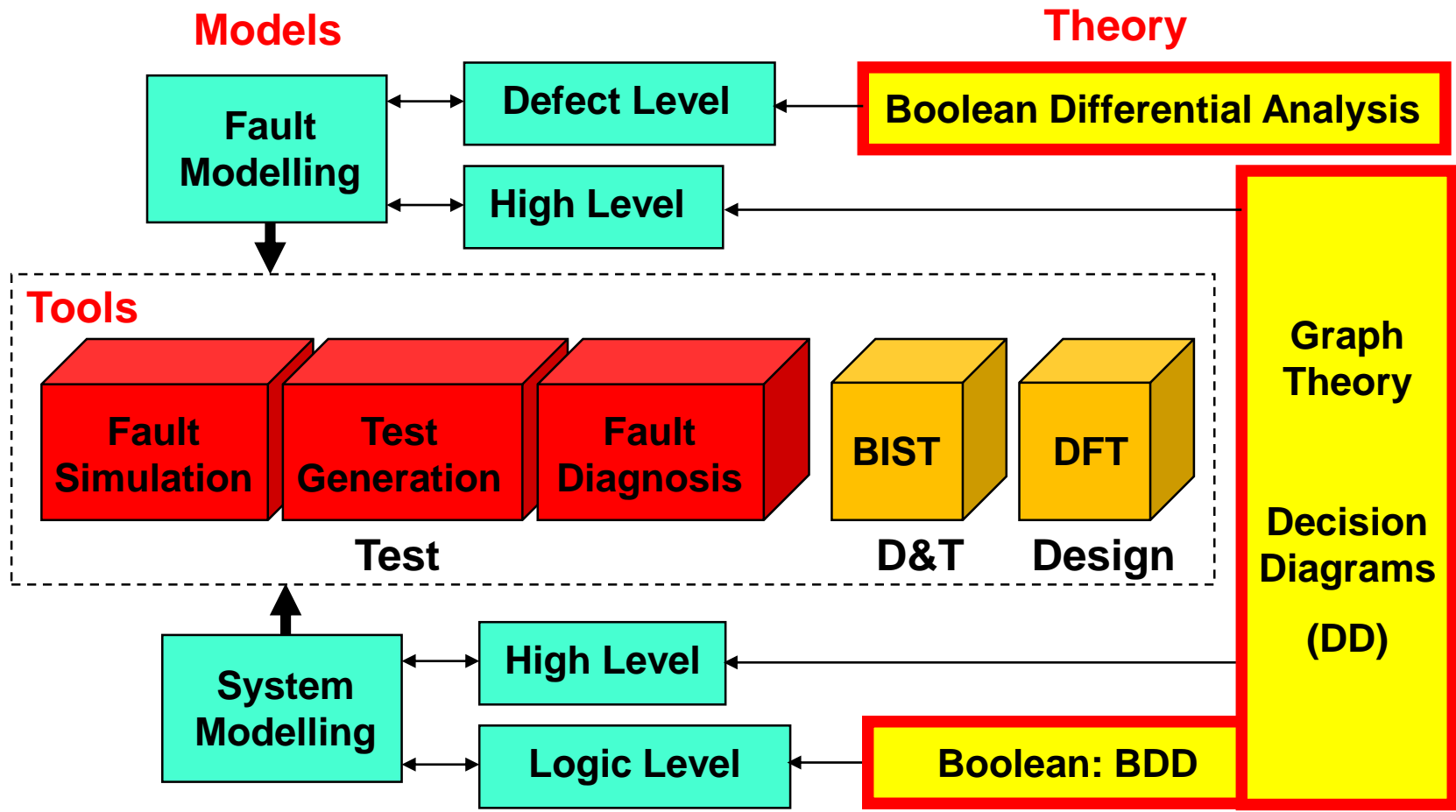
# Introduction to Theories: The Course Map



# Test Related Basic Problems

Fault table (Solutions of Diagnostic equations)

Test experiment data

**Fault modeling**

	F <sub>1</sub>	F <sub>2</sub>	F <sub>3</sub>	F <sub>4</sub>	F <sub>5</sub>	F <sub>6</sub>	F <sub>7</sub>
T <sub>1</sub>	0	1	1	0	0	0	0
T <sub>2</sub>	1	0	0	1	0	0	0
T <sub>3</sub>	1	1	0	1	0	1	0
T <sub>4</sub>	0	1	0	0	1	0	0
T <sub>5</sub>	0	0	1	0	1	1	0
T <sub>6</sub>	0	0	1	0	0	1	1

E <sub>1</sub>	E <sub>2</sub>	E <sub>3</sub>
0	0	1
0	1	0
0	1	0
1	0	1
1	0	1
0	0	0

How many rows and columns should be in the Fault Table?

**Fault simulation**

**Fault F<sub>5</sub> located**

**Fault diagnosis**

**Test generation**

**VIRTUAL WORLD**

**REAL WORLD**

# Why We Need Fault Models?

---

- **Fault models are needed for**
  - test generation,
  - test quality evaluation and
  - fault diagnosis
- **To handle real physical defects is too difficult**
- **The fault model should**
  - reflect accurately the behaviour of defects, and
  - be **computationally efficient**
- **Usually combination of different fault models is used**
- **Fault model free approaches (!)**

# Classification of Fault Models

---

- **Fault modeling levels**

- Transistor level defects

- stuck-open, stuck-off

- Logic level faults

- stuck-at fault model
- bridging fault model
- delay fault model

- Register transfer level faults

- ISA level faults (MP faults)

- SW level faults

**Low-Level** models

**High-Level** models


- Hierarchical fault modeling and mapping

- Functional fault modeling

# Fault modeling terminology

- **Defect:** a **physical imperfection**, which can manifest itself as an erroneous logic signal
- Defect does not allow easy and direct mathematical treatment for diagnostic purposes
- **Fault:** a **logic fault model** as a manifestation of an error in a logic signal
- **Error:** an instance of an **incorrect operation** of the system being tested
- The causes of the observed errors may be **design errors** or **physical faults (defects)**
- **Failure:** an error which causes a **system failing** to perform in a required manner

## Defects, faults and errors

 

# Physical Defects as Fault Causes

---

Physical defects may occur:

- **Manufacturing process:** missing contacts , parasitic transistors, gate oxide shorts, oxide break-down, metal-to silicon shorts, missing or wrong components, broken or shorted tracks (board design), etc.
- **Process fabrication marginalities:** line width variation, etc.
- **Material and age defects:** bulk defects (cracks, crystal imperfections), surface impurities, dielectric breakdown, electromigration, etc.
- **Packaging:** contact degradation, seal leaks, etc.
- **Environmental influence:** temperature related defects, high humidity, vibration, electrical stress, crosstalk, radiation, etc.

# Soft and Hard Defects

---

Defects can be divided roughly into two basic groups :

- **Soft defects**

- defects which cause speed fault
- show up at high speed or produce some temperature
- they need two or more test patterns for their activation and error observation (require carefully constructed transitions for defect activation);
- require tests to be applied at speed.
- examples: “high resistance” bridges, x-coupling, “tunneling break”

- **Hard defects**

- defects observed at all frequencies
- a test can be applied at slow speed
- they need only one-pattern test set
- example: “low resistance” bridge



# Defect Manifestation and Test Methods

---

Defects have to be measured and modeled into the faults

They are manifested in different measurable manners:


- by changing a logical value on a circuit node (**Boolean testing**, or testing at the logical level)
- by changing time specifications (**At-speed testing**)
- by increasing the steady state supply current (**IDDQ testing**)
- by variation in one or a set of parameters such that their specific distribution in a circuit makes it fall out of specifications

The test methods listed are not replacable

They all have to be used for achieving high quality of testing

# Transistor Level Faults

## Logic level interpretations:

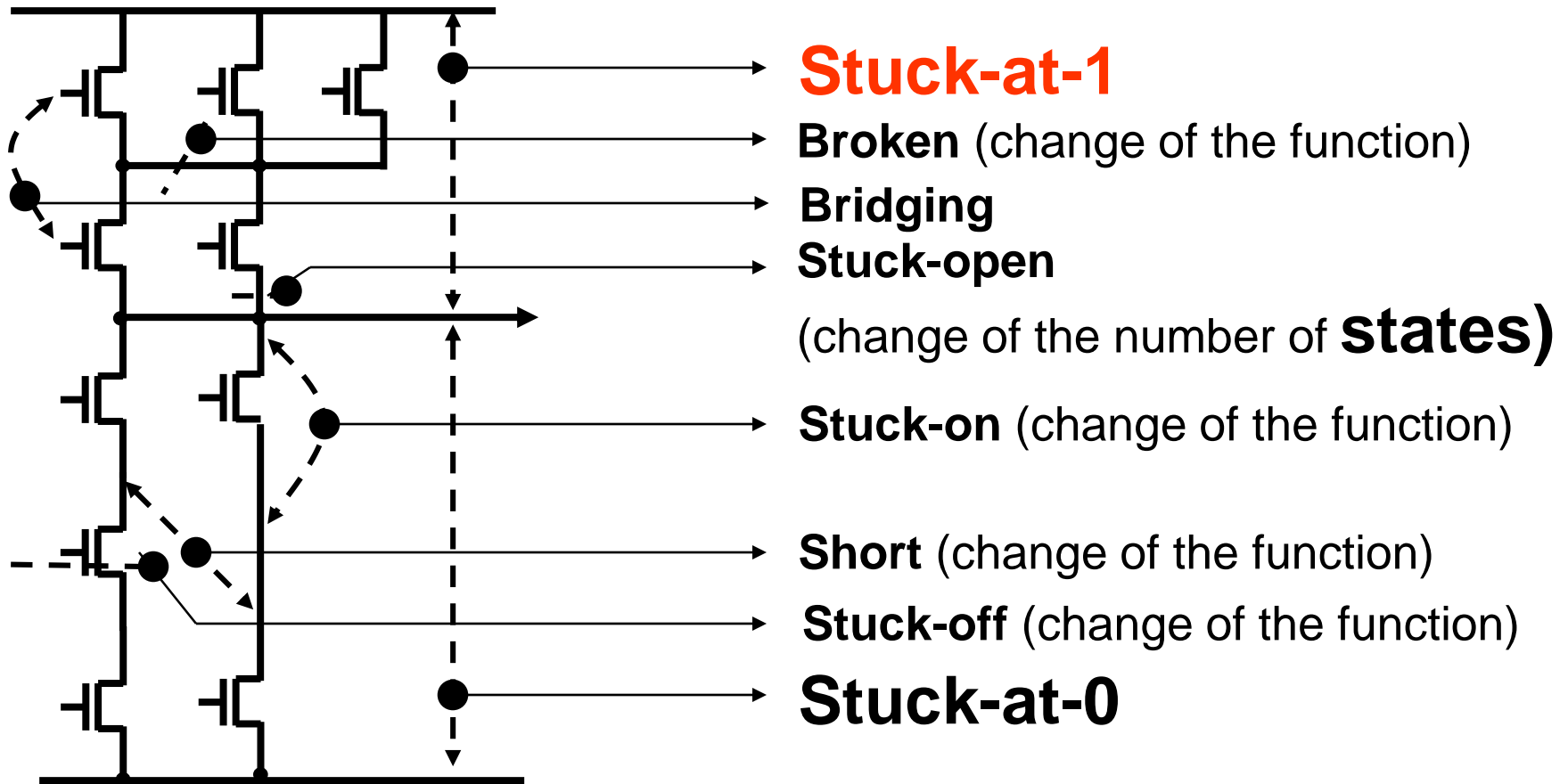

# Süsteemide diagnostika

---

## **3. Rikete modelleerimine**

**3.1. Rikete klassifikatsioon**

**3.2. Loogikatasandi konstantrikked**

**3.3. Tingimuslikud rikked**

**3.4. Kõrgtasandi rikked**

# Structural and Functional Fault Modeling


## Classification of fault models

Fault models are: **explicit** and **implicit**

- **explicit** faults may be enumerated
- **implicit** faults are given by some characterizing properties

Fault models are: **structural** and **functional**:

 - **structural** faults are related to structural models, they modify interconnections between components
- **functional** faults are related to functional models, they modify functions of components



## Structural faults:

- line  $a$  is broken
- short between  $x_2$  and  $x_3$

## Functional fault:

Instead of  $y = x_1x_2 \vee x_2x_3$   
 $y = x_2x_3$

# Fault and defect modeling

---

## Structural faults

- Structural fault models assume that components are fault-free and only their interconnections are affected:
  - a **short** is formed by connecting points not intended to be connected
  - an **open** results from the breaking of a connection
- Structural fault models are:
  - a line is **stuck at** a *fixed logic value*  $v$  ( $v \in \{0,1\}$ ), examples:
    - a short between ground or power and a signal line
    - an open on a unidirectional signal line
    - any internal fault in the component driving its output that it keeps a constant value
  - **bridging faults** (shorts between signal lines) with two types: AND and OR bridging faults (depending on the technology).


# Structural Logic Level Fault Modeling

## Why logic fault models?

- complexity of simulation reduces (many physical faults may be modeled by the same logic fault)
- one logic fault model is applicable to many technologies
- logic fault tests may be used for physical faults whose effect is not completely understood
- **they give a possibility to move from the lower physical level to the higher logic level**

## Stuck-at fault model:

### Two defects:

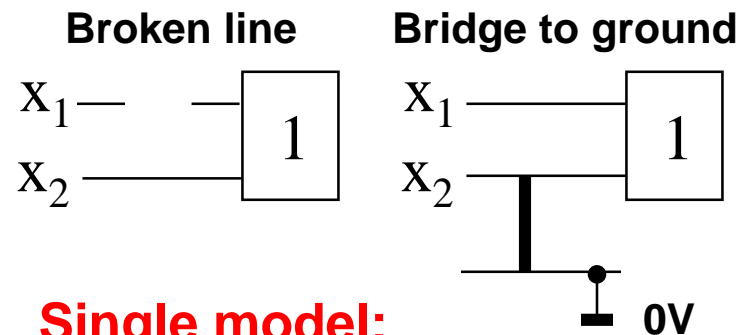

### Single model: Stuck-at-0


# Gate-Level Faults: SAF Model

---

- SAF is modeled by assigning a fixed (0,1) value to a signal line: stuck\_at 0 (SAF0) or stuck\_at 1 (SAF1)
- SAF model is the **industrial standard since 1959**
- The death of the SAF model has been predicted, but several reasons and SAF properties have been persuaded that the **SAF model continues living:**
  - **simplicity:** SAF is easy to apply to a CUT
  - **tractability:** can be applied to millions of gates at once
  - **logic behavior:** fault behavior can be determined logically, so simulation is straightforward and deterministic
  - **measurability:** detection/non detection are easy
  - **adaptability:** can apply on gates, systems, transistors, RTL, etc.

# Gate-Level Faults: SAF Model

## Stuck-At Fault Model

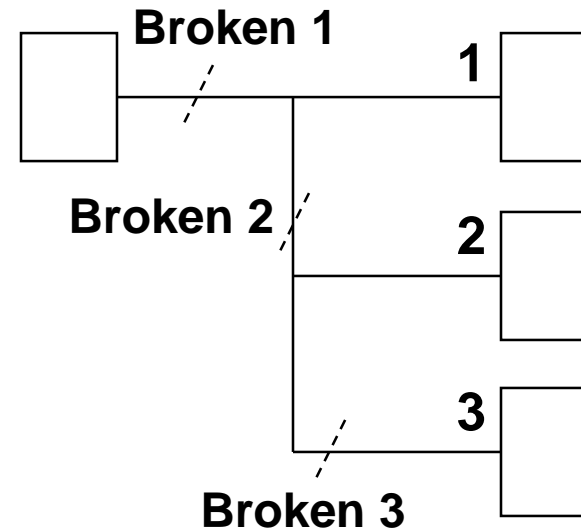

**Broken 1** → stuck branches: 1,2,3 (or stuck stem)


**Broken 2** → stuck branches: 2,3

**Broken 3** → stuck branches: 3



# Stuck-at Fault Properties


 
## Fault equivalence and fault dominance:



A	B	C	D	Fault class
1	1	1	0	A/0, B/0, C/0, D/1 → <b>Equivalence class</b>
0	1	1	1	A/1, D/0
1	0	1	1	B/1, D/0
1	1	0	1	C/1, D/0

→ **Dominance classes**

## Fault collapsing:

 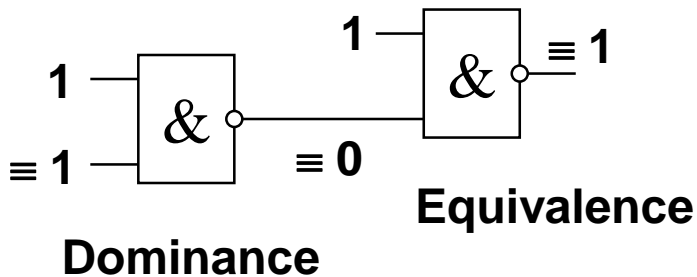

# Rikete dominants

## Kuidas seletada dominantsi suhet:

A	B	C	D	Rikete vahelised suhted
1	1	1	0	A/0, B/0, C/0, D/1 <b>Ekvivalents</b>
0	1	1	1	A/1, <b>D/0</b>
1	0	1	1	B/1, <b>D/0</b>
1	1	0	1	C/1, <b>D/0</b>

→ **D/0 domineerib**


- Viin ja **jää** hävitavad su neerud
- Rumm ja **jää** hävitavad su maksa
- Viski ja **jää** hävitavad su südame
- Džinn ja **jää** hävitavad su aju
- Pepsi ja **jää** hävitavad su hambad

**Ilmselt domineerib kõikjal jää  
ja on seega surmav**

# Impact of Fault Collapsing
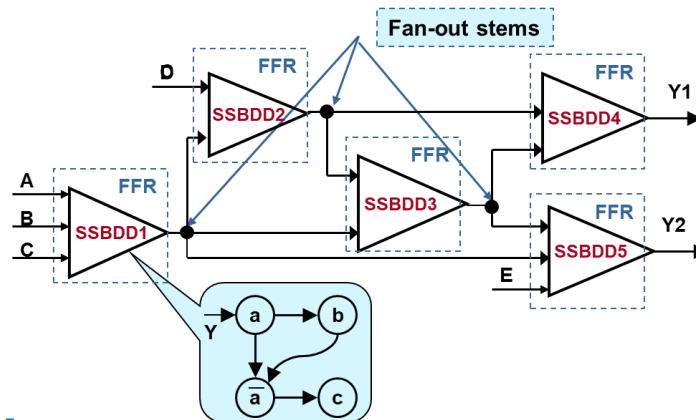
## Theorem 1:

A test that detects all single SAF on **all inputs** of **tree like circuit** detects all single SAF in that circuit



**FFR** – Fan-out-free circuit



## Theorem 2:

A test that detects all single SAF on all inputs **and all fan-out branches** of a circuit will detect all single SAFs in that circuit

The idea of **N-detect** single SAF test vectors was proposed to detect more defects not covered by the SAF model
  
# Fault Collapsing with SSBDDs

Each node in SSBDD represents a signal path:




## Theorem 2:


A set of test vectors that detects all single SAFs on all primary inputs and all fanout branches of a combinational logic circuit will detect all single SAFs in that circuit

# Fault Redundancy

Redundant gates (bad design):

 

Internal signal dependencies:

 

Impossible pattern,  
OR → XOR  
not testable

$$y = \overline{x_1} \vee (\overline{x_1} \vee \overline{x_2})x_4 \vee \overline{x_3}x_4$$


Faults at  $x_2$  not testable

$$\frac{\partial y}{\partial x_2} \equiv 0$$

Optimized function:  $y = \overline{x_1} \vee x_4 \vee x_3$


# Fault Redundancy

Hazard control circuitry:

 

Redundant AND-gate  
Fault  $\equiv 0$  is not testable

Error control circuitry:

 

$E \equiv 1$  if decoder is fault-free  
Fault  $\equiv 0$  is not testable

# Fault Redundancy

- **Why this phenomenon is important and troublesome**
  - **It makes test generation (search for a proper test pattern for the given fault extremely time consuming)**
    - $n$  – number of inputs of the circuit
    - If fault is redundant,  **$2^n$  backtracks** in search are needed
    - If 64 inputs, then  $2^{64} = 10^{19}$  backtracks
  - **It does not allow evaluate the test quality trustworthy – the problem of test efficiency and fault coverage**
    - $F$  – number of all faults
    - $F_R$  – number of redundant faults
    - $F_D$  – number of detected faults
    - $FC$  – fault coverage
    - $TE$  – test efficiency
  - **Fault coverage:  $FC = F_D / F$**
  - **Test efficiency:  $TE = F_D / (F - F_R)$**

Example:

Faults:  $F = 1000$

Redundant faults:  $FR = 100$

Detected faults:  $FD = 880$

**Fault coverage:  $FC = 880/1000 = 88\%$**

**Test efficiency:  $TE = 880/900 = 98\%$**

**Contradiction: between fault tolerance and fault coverage**

# Problems with Testing: Multiple Faults

- Multiple stuck-fault (MSF) model is an extension of the single stuck-fault (SSF) where several lines can be simultaneously stuck
- If  $n$  - is the number of possible SSF sites, there are  $2n$  possible SSFs, but there are

**$3^n - 1$  possible MSFs**

Wire a 0,1,x  
 Wire b 0,1,x

- If we assume that the multiplicity of faults is no greater than  $k$ , then the **number of possible MSFs** is

$$N = \sum_{i=1}^k \{C_n^i\} 2^i \ll 3^n - 1 \quad C_n^i = \frac{n!}{i!(n-i)!}$$


- $C_n^i$  - number of sets of  $i$  lines,  $2^i$  - number of faults on the set



# Multiple Fault Problem

We have three wires,  
each of them may be  
in three states:

0, 1, OK

 

$$N = 3^n - 1 = 26$$

$$N = \sum_{i=1}^k \{C_n^i\} 2^i \ll 3^n - 1$$

$$C_n^i = \frac{n!}{i!(n-i)!}$$

Number of assumed faults	Number of combinations of faulty wires $C_n^i$	Number of faults on this combination of wires $2^i$	Number of faults for each case $i$	Total number of multiple faults $N$
Single fault	1, 2, 3 → 3	$2^1 = 2$	6	<b>6</b>
2 faults	1,2; 1,3; 2,3 → 3	$2^2 = 4$	12	<b>18</b>
3 faults	1,2,3 → 1	$2^3 = 8$	8	<b>26</b>

**The number of multiple faults is very big.** However, their consideration is needed because of possible

***fault masking***

# Multiple Fault Testing

---

- ✓ **2n** single faults (SSAF) vs.  **$3^n - 1$**  multiple faults (MSAF)

Two approaches to testing:


## Devil's advocate

- ✓ **Goal:** to test and identify **faults**
- ✓ Does not work because of huge number of multiple fault combinations

## Angel's advocate

- ✓ **Goal:** to identify **fault-free lines**
- ✓ **State of the Art:** Test generation using **test pairs**

# Test Related Basic Problems

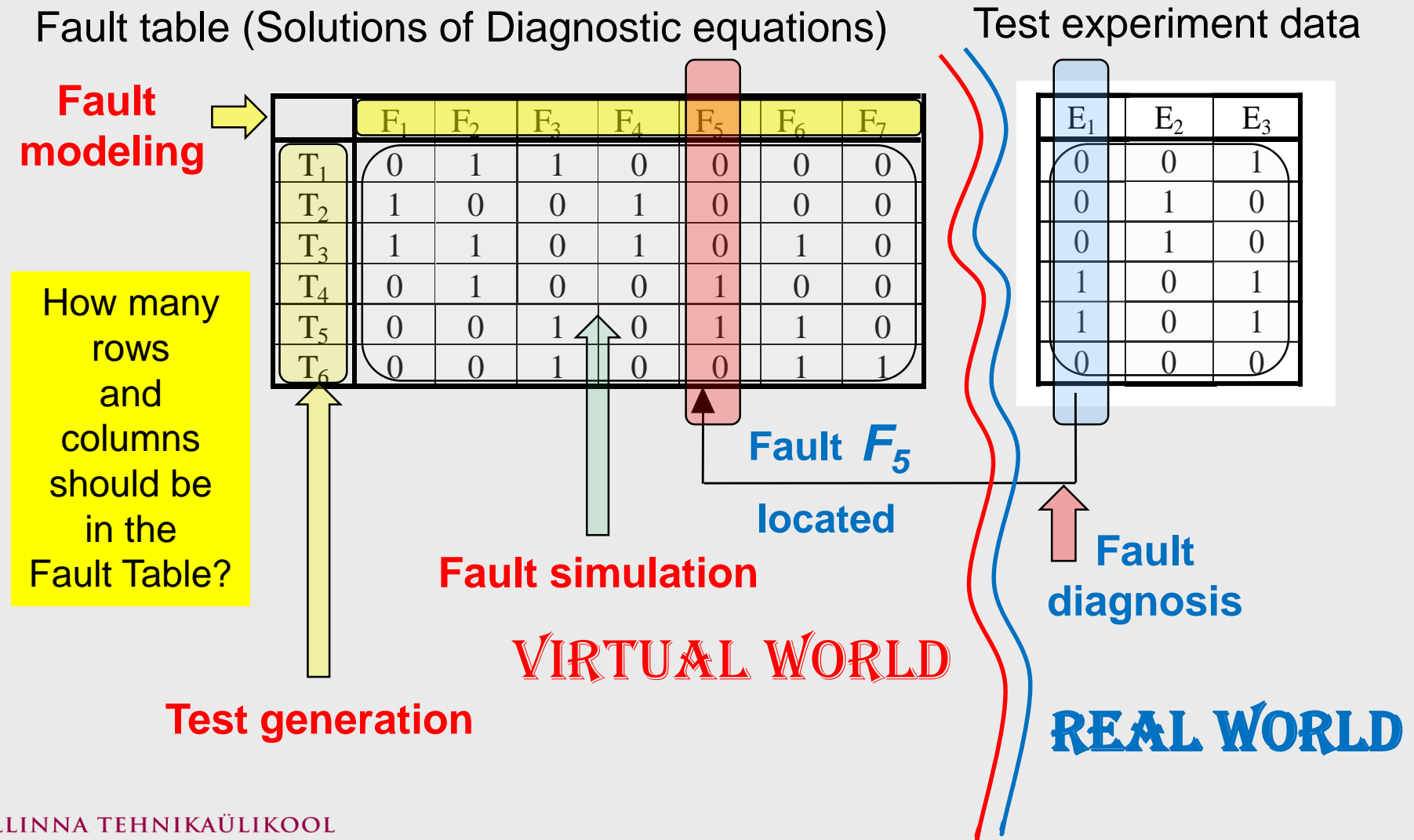

# Fault Diagnosis Dilemmas

Diagnosis method	Fault table				Test result
Devil's advocate approach		Tested faults			Passed
				Tested faults	Failed
			Tested faults		Failed
Single fault assumption				Fault candidates	Diagnosis
Multiple faults allowed		?	Fault candidates		
Angel's advocate		Proved OK		Fault candidates	

# Süsteemide diagnostika

---

## **3. Rikete modelleerimine**

**3.1. Rikete klassifikatsioon**

**3.2. Loogikatasandi konstantrikked**

**3.3. Tingimuslikud rikked**

**3.4. Kõrgtasandi rikked**


# Bridging Faults

---


- **Bridging faults model all defects that cause unintended electrical connections across two or more circuit nodes**
- **Physical causes of the shorts:**
  - **extra conducting material:** e.g. photolithographic printing error, conductive particle contamination, etc.
  - **missing insulating material:** printing error, gate-oxide defect causing pinhole, insulating particle contamination, etc.
- **Bridges have non-linear or linear properties with resistance from zero to  $> 1 \text{ M}\Omega$ . The typical values for resistance:**
  - logical critical resistance is  $100 \text{ }\Omega$  to  $2 \text{ k}\Omega$
  - timing critical resistance is  $5 \text{ k}\Omega$  to  $10 \text{ k}\Omega$
- **Bridging faults can be classified:**
  - **inter-gate shorts** (can produce sequential behavior if short creates feedback)
  - **intra-gate shorts**

# Bridging Faults


## Wired AND/OR model

 

### W-AND:

 

### W-OR:

 

Fault-free		W-AND		W-OR	
$x_1$	$x_2$	$x'_1$	$x'_2$	$x'_1$	$x'_2$
0	0	0	0	0	0
0	1	0	0	1	1
1	0	0	0	1	1
1	1	1	1	1	1

# Simulating of Bridging Faults

---

- In absence of any physical layout information, a fault list may be created by **exhaustively enumerating** every two nets in the design
- This method, however, is only feasible for very small circuits, because the number of all net pairs in the design grows exponentially
- For larger circuits, fault sampling may be used, where a set of net pairs is chosen **randomly**
- An alternative method of creating a bridging fault list without layout information is to enumerate all possible input-to-input and input-to-output shorts for each gate (or cell) in the design
- This method would require physical **layout information**



# Advanced Bridging Fault Models


## Constrained Multiple Line SAF Model

**Bridge** between a and b

The two branches of a and three branches of b could be interpreted by the driven gates to be any one of the 32 combinations

One corresponds to fault free situation, 31 correspond to faulty situations – **31 MLSFs**

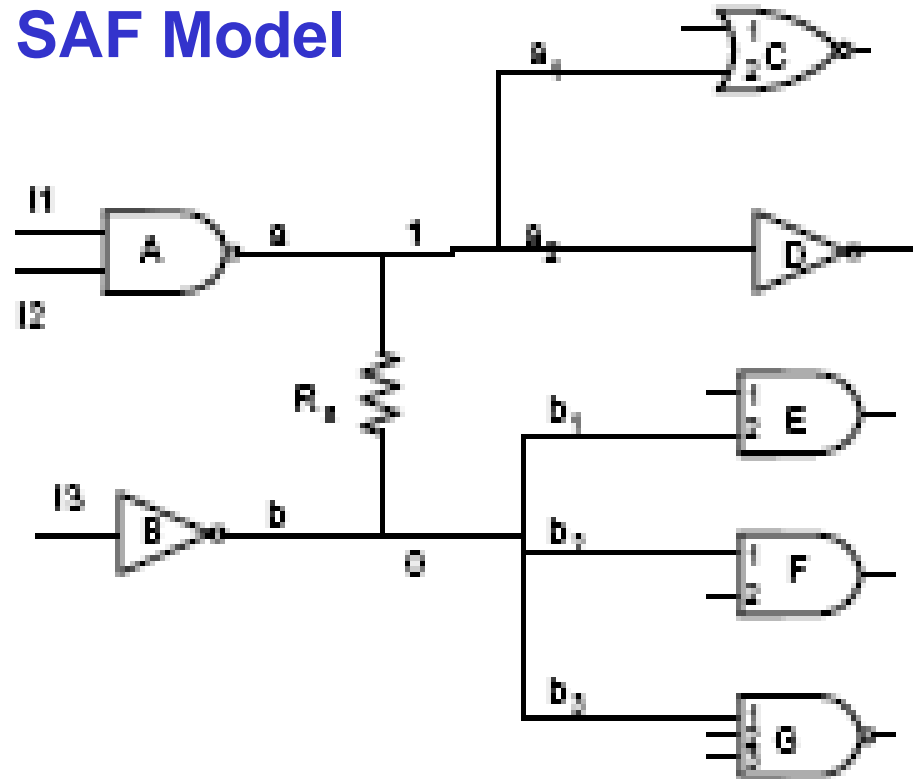Method of **implicit fault simulation**: assign one branch with faulty value, and let other branches with unknown values



Copyright © G.Chen, S.Reddy, I.Pomeranz, J.Rajski, P.Engelke, B.Becker 2005

# Advanced Bridging Fault Models

---

## Constrained Multiple Line SAF Model

### Advantages:

- Method is uniform to consider opens and bridges
- Method does not need circuit level information such as relative strengths and threshold voltages of transistors associated with bridge
- Method allows different levels of model complexity and accuracy (e.g. using implicit simulation with different number of unknown values)
- Method is based on constrained SAF model, hence, traditional gate level tools can be used

# Delay Faults


---

- **Studies of the electrical properties of defects have shown that most of the random CMOS defects cause a timing (delay) effect rather than a other catastrophic defects (e.g. resistive bridges above a critical resistance cause delay)**
- **Delay fault means that a good CUT may perform correctly its function in a system, but it fails in designed timing specifications**
- **Delay faults could be caused by:**
  - **subtle manufacturing process defects,**
  - **transistor threshold voltage shifts,**
  - **increased parasitic capacitance,**
  - **improper timing design, etc.**

# Delay Fault Models

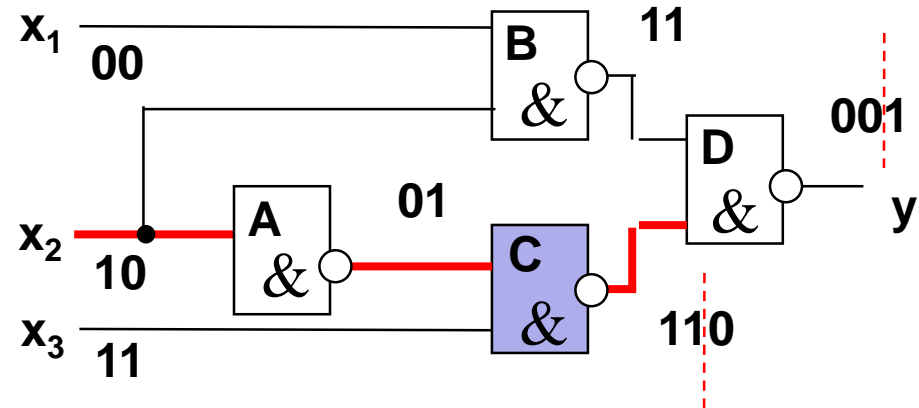**Delay faults are tested by test pattern pairs:**

- the first test pattern initializes the circuit, and
- the second pattern sensitizes the fault



**Delay fault models:**


- **Gate delay fault** (delay fault is lumped at a single gate, quantitative model)
- **Transition fault** (qualitative model, gross delay fault model, independent of the activated path)
- **Path delay fault** (sum of the delays of gates along a given path)
- **Line delay fault** (is propagated through the longest sensitizable path)
- **Segment delay fault** (tradeoff between the transition and the path delay fault models)

# Comparison of Delay Faults

Fault models	Advantages	Limitations
Gate delay	All gates can be modeled	<ul style="list-style-type: none"> <li>• Distributed failures not considered</li> <li>• Exact defect size not possible</li> </ul>
Transition fault	Easy to model all gates	Distributed failures not considered
Path delay	Distributed failures considered	Impossible to enumerate all paths
Line delay	<ul style="list-style-type: none"> <li>• All gates are modeled</li> <li>• Distributed failures considered</li> <li>• Better coverage metric</li> <li>• Additional fault coverage by using multi-path technique</li> </ul>	<ul style="list-style-type: none"> <li>• Existence of nonrobust test</li> <li>• May fail for some shorter paths</li> </ul>
Segment delay	Considers general delay defect from spot to distributed failures	Longest delay path may not be tested

Copyright © A.K.Majhi, V.D.Agrawal 1997

# Extended Fault Models

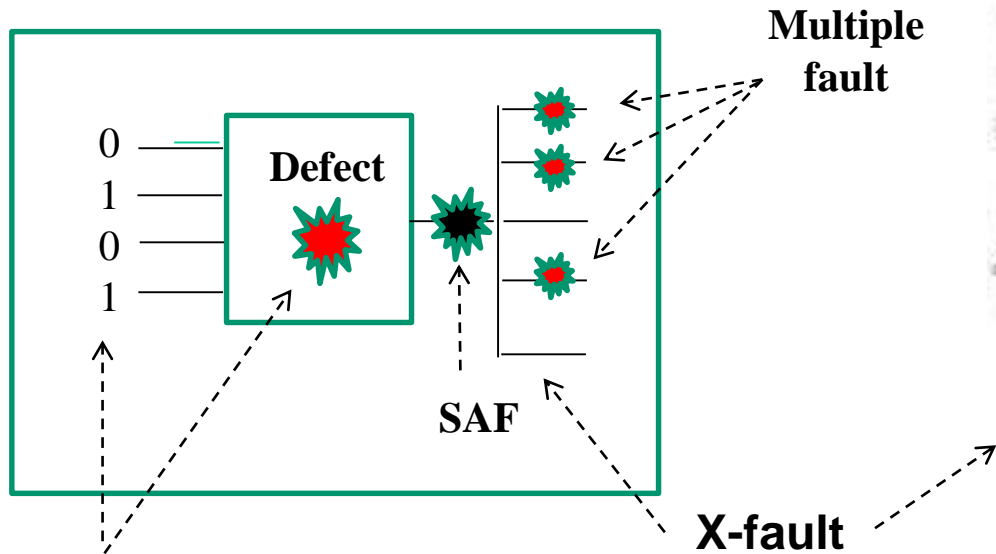


**Conditional fault**  
 Pattern fault  
 Constrained SAF  
**Single faulty signal**

**X-fault**  
 Byzantine fault  
 Bridges  
 Stuck-opens  
**Multiple faulty signal**




**Resistive bridge fault**

 
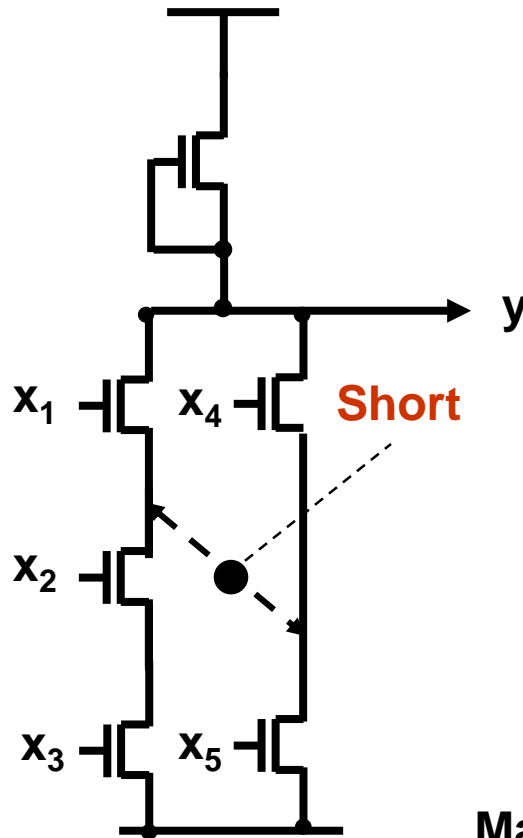
# Mapping Transistor Faults to Logic Level

A transistor fault causes a change in a logic function not representable by SAF model



Function:  $y = x_1 x_2 x_3 \vee x_4 x_5$

Faulty function:  $y^d = (x_1 \vee x_4)(x_2 x_3 \vee x_5)$

Defect variable:  $d = \begin{cases} 0 - \text{defect } d \text{ is missing} \\ 1 - \text{defect } d \text{ is present} \end{cases}$


Generic function with defect:

$$y^* = (y \wedge \bar{d}) \vee (y^d \wedge d)$$

Mapping the physical defect onto the logic level by solving the equation:

$$\frac{\partial y^*}{\partial d} = 1$$
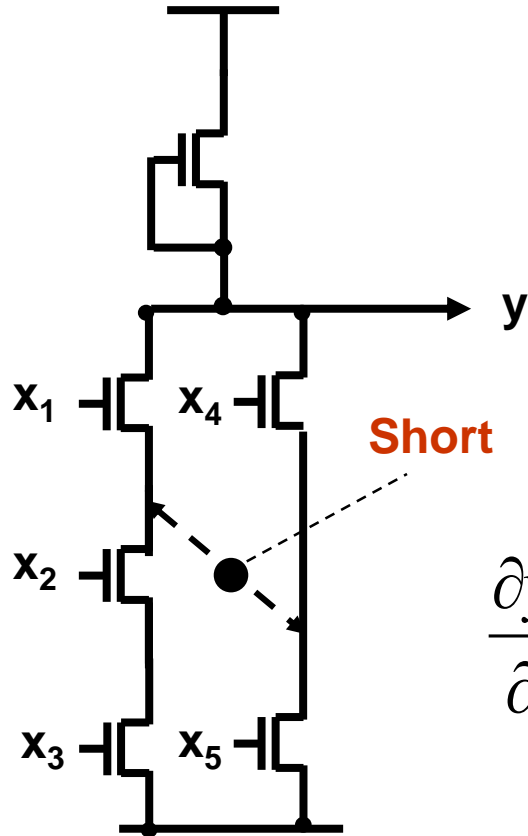
# Mapping Transistor Faults to Logic Level



Function:  $y = x_1 x_2 x_3 \vee x_4 x_5$

Faulty function:  $y^d = (x_1 \vee x_4)(x_2 x_3 \vee x_5)$

**Generic function with defect:**

$$y^* = (y \wedge \bar{d}) \vee (y^d \wedge d)$$


**Test calculation by Boolean derivative:**

$$\begin{aligned} \frac{\partial y^*}{\partial d} &= \frac{\partial \left( (x_1 x_2 x_3 \vee x_4 x_5) \bar{d} \vee (x_1 \vee x_4)(x_2 x_3 \vee x_5) d \right)}{\partial d} = \\ &= \overline{x_1 x_2 x_4 x_5} \vee \overline{x_1 x_3 x_4 x_5} \vee \overline{x_1 x_2 x_3 x_4 x_5} = 1 \end{aligned}$$



# Fault Table: Mapping Defects to Faults

$i$	Fault $d_i$	Erroneous function $f^{di}$	$p_i$	Input patterns $t_j$															
				0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
1	B/C	$\text{not}((B*C)*(A+D))$	0.010307065				1								1	1	1		
2	B/D	$\text{not}((B*D)*(A+C))$	0.000858922				1								1	1		1	
3	B/N9	$B*(\text{not}(A))$	0.043375564	1	1	1						1	1	1	1				
4	B/Q	$B*(\text{not}(C*D))$	0.007515568	1	1	1						1	1	1		1	1	1	
5	B/VDD	$\text{not}(A+(C*D))$	0.001717844									1	1	1					
6	B/VSS	$\text{not}(C*D)$	0.035645265													1	1	1	
7	A/C	$\text{not}((A*C)*(B+D))$	0.098990767				1					1				1	1		
8	A/D	$\text{not}((A*D)*(B+C))$	0.013098561				1					1				1		1	
9	A/N9	$A*(\text{not}(B))$	0.038651492	1	1	1													
10	A/Q	$A*(\text{not}(C*D))$	0.025982392	1	1	1													
11	A/VDD	$\text{not}(B+(C*D))$	0.000214731																
12	C/N9	$\text{not}(A+B+D)+(C*(\text{not}((A*B)+D)))$	0.020399399		1														
13	C/Q	$C*(\text{not}(A*B))$	0.033927421	1	1														
14	C/VSS	$\text{not}(A*B)$	0.005153532																
15	D/N9	$\text{not}(A+B+C)+(D*(\text{not}((A*B)+C)))$	0.007730298			1													
16	D/Q	$D*(\text{not}(A*B))$	0.149452437	1		1													
17	N9/Q	$\text{not}((A*B)+(B*C*D)+(A*C*D))$	0.143654713																
18	N9/VDD	$\text{not}((C*D)+(A*B*D)+(A*B*C))$	0.253382006																
19	Q/VDD	SA1 at Q	0.014386944																1
20	Q/VSS	SA0 at Q	0.095555078	1	1	1													

 

# Generalization: Functional Fault Model


Constraints calculation:

$$y^* = F^*(x_1, x_2, \dots, x_n, d) = \overline{d}F \vee dF^d$$

Fault-free    Faulty

$d = 1$ , if the defect is present

Component with defect:

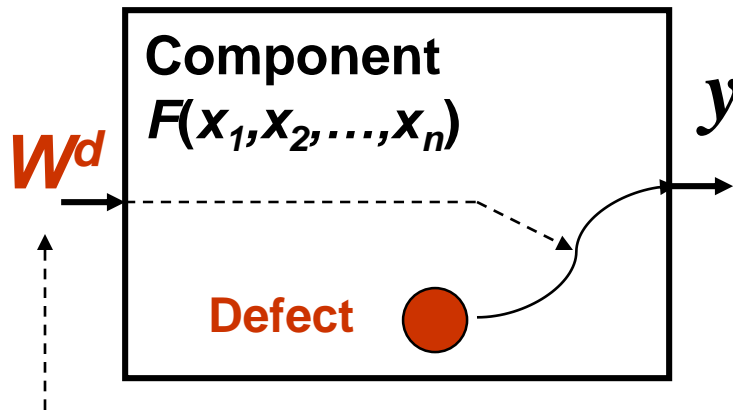

Logical constraints

Constraints:


$$W^d = \frac{\partial y^*}{\partial d} = 1$$

Fault model:

$$(dy, W^d), (dy, \{W_k^{ch}\})$$

# Functional Fault Model Examples

Component with defect:

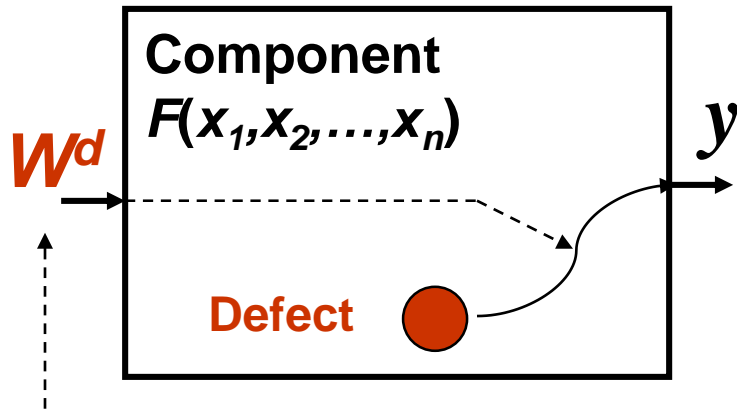

Logical constraints

FF model:

$(dy, W^d), (dy, \{W_k^{ch}\})$

Constraints:

$$W^d = \frac{\partial y^*}{\partial d} = 1$$


Constraints examples:

N	Fault (defect)	Constraints
1	SAF $x \equiv 0$	$x = 1$
2	SAF $x \equiv 1$	$x = 0$
3	Short between x and z	$x = 1, z = 0$
4	Exchange of x and z	$x = 1, z = 0$
5	Delay fault on x	$x = 1, x' = 0$

# Synthesis of a Functional Fault Model

 Example:

**Bridging fault** between leads  $x_k$  and  $x_l$



$$x_k^* = \bar{d}x_k \vee dx_k^d = \bar{d}x_k \vee dx_k x_l = x_k (\bar{d} \vee x_l)$$

$$x_k^* = f(x_k, x_l, d)$$

$$W^d = \frac{\partial x_k^*}{\partial d} = x_k \bar{x}_l$$

**Wired-AND  
model**

The condition  $W^d = x_k \bar{x}_l = 1$  means that

in order to detect the short between leads  $x_k$  and  $x_l$   
on the lead  $x_k$

we have to assign to  $x_k$  the value 1 and to  $x_l$  the value 0.

# Synthesis of a Functional Fault Model

## Example:

A short between leads  $x_k$  and  $x_l$  changes the combinational circuit into sequential one


$$y^* = \bar{d}(x_1 x_2 \vee \bar{x}_3) \vee d(x_1 x_2 y \vee \bar{x}_3) = x_1 x_2 (\bar{d} \vee y') \bar{x}_3$$

$$W^d = \partial y^* / \partial d = x_1 x_2 x_3 \bar{y}' = 1$$


Sequential constraints:

$t$	$x_1$	$x_2$	$x_3$	$y$
<b>1</b>	<b>0</b>		<b>1</b>	<b>0</b>
<b>2</b>	<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>

Bridging fault causes a feedback loop:

 

Equivalent faulty circuit:

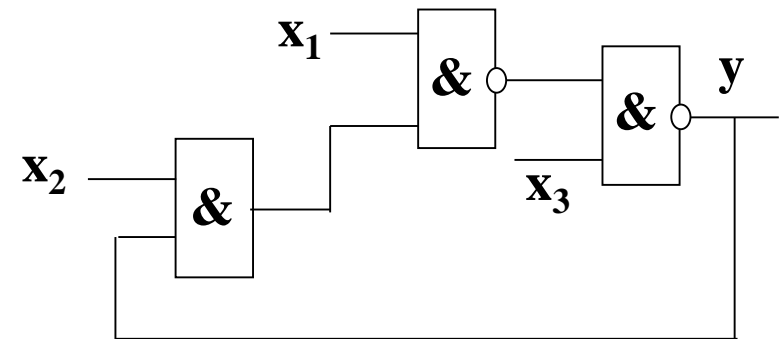

# Süsteemide diagnostika

---

## **3. Rikete modelleerimine**

**3.1. Rikete klassifikatsioon**

**3.2. Loogikatasandi konstantrikked**


**3.3. Tingimuslikud rikked**

**3.4. Kõrgtasandi rikked**

 
# Hierarchical Fault Modeling

$$y^* = F^*(x_1, \dots, x_n, d) = \bar{d}F \vee dF^d$$

$$W^d = \frac{\partial y^*}{\partial d} = 1$$


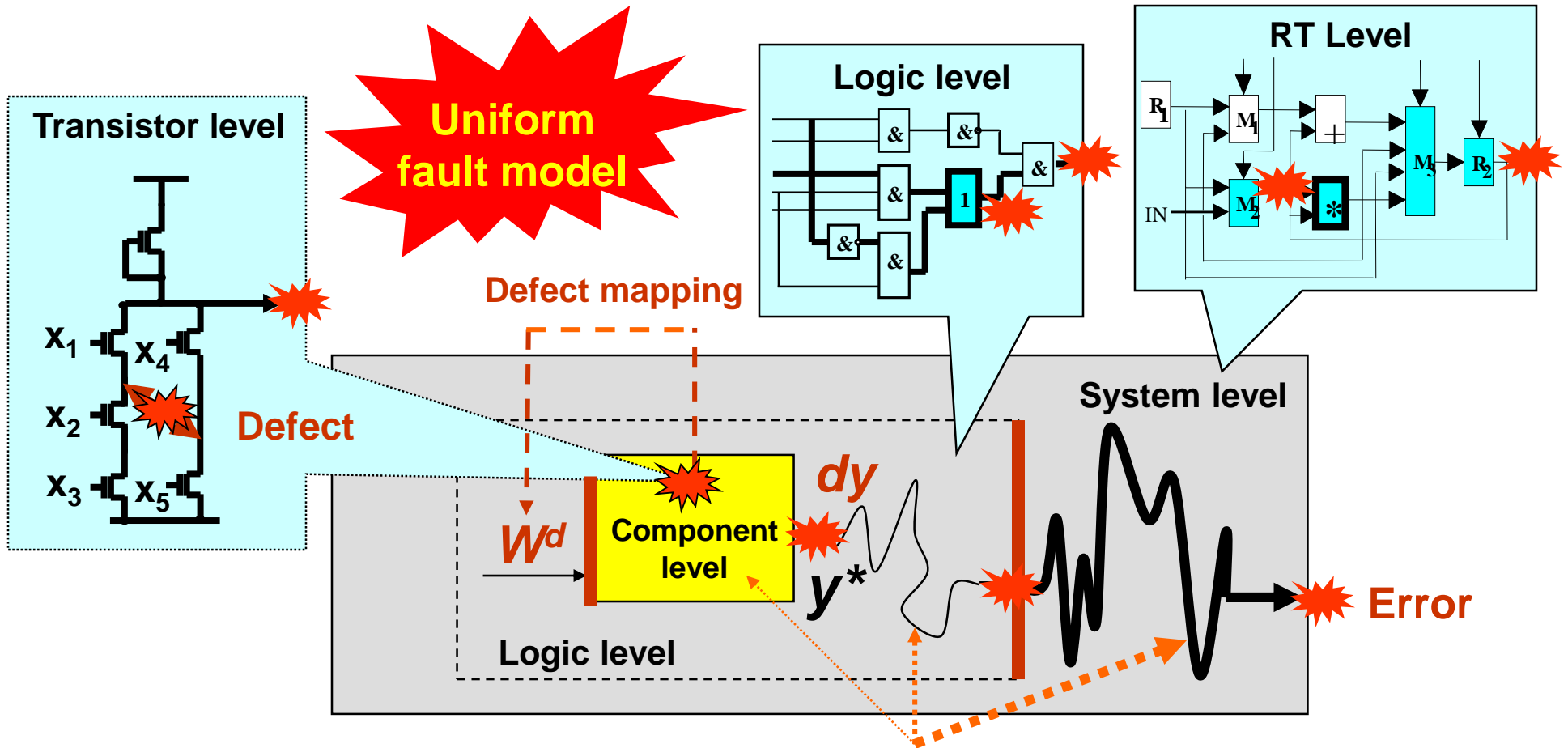
# Hierarchical Diagnostic Modeling of Systems



**Hierarchical fault propagation**



# Motivations for High-Level Fault Models

---

## Current situation:

- The efficiency of test generation (quality, speed) is highly depending on
  - the description method (level, language), and
  - fault models
- Because of the growing complexity of systems, gate level methods have become obsolete
- High-Level methods for diagnostic modeling are today emerging, however they are not still mature

## Main disadvantages:






- The known methods for fault modeling are
  - dedicated to special classes (i.e. for microprocessors, for RTL, VHDL etc. languages...), not general
  - not well defined and formalized

# Fault Models for Combinational Circuits

---
     
## Exhaustive combinational fault model:

- exhaustive test patterns
- pseudoexhaustive test patterns
  - exhaustive output line oriented test patterns
  - exhaustive module oriented test patterns



# Fault Models for High-Level Components

---

## Decoder:

- instead of correct line, incorrect is activated
- in addition to correct line, additional line is activated
- no lines are activated

## Multiplexer ( $n$ inputs $\log_2 n$ control lines):

- stuck-at - 0 (1) on inputs
- another input (instead of, additional)
- value, followed by its complement
- **value, followed by its complement on a line whose address differs in 1 bit**

## Memory fault models:

- one or more cells stuck-at - 0 (1)
- two or more cells coupled

# Fault models and Tests

---

*Dedicated functional fault model for multiplexer:*

- stuck-at-0 (1) on inputs,
  - another input (instead of, additional)
  - value, followed by its complement
- value, followed by its complement on a line whose address differs in one bit



Functional  
fault model



Test  
description

# Register Level Fault Models

---

RTL statement:

**$K: (If\ T, C)\ R_D \leftarrow F(R_{S1}, R_{S2}, \dots R_{Sm}), \rightarrow N$**

Components (variables)  
of the statement:

**K** - label  
**T** - timing condition  
**C** - logical condition  
**R<sub>D</sub>** - destination register  
**R<sub>S</sub>** - source register  
**F** - operation (microoperation)  
**←** - data transfer  
**→ N** - jump to the next statement

RT level faults:

**K → K'** - label faults  
**T → T'** - timing faults  
**C → C'** - logical condition faults  
**R<sub>D</sub> → R<sub>D</sub>** - register decoding faults  
**R<sub>S</sub> → R<sub>S</sub>** - data storage faults  
**F → F'** - operation decoding faults  
**←** - data transfer faults  
**→ N** - control faults  
**(F) → (F)'** - data manipulation faults

# Microprocessor Fault Model


---

Faults affecting the operation of microprocessor can be divided into the following classes:

- addressing faults affecting register decoding
- addressing faults affecting the instruction decoding and – sequencing functions;
- faults in the data-storage function;
- faults in the data-transfer function;
- faults in the data-manipulation function.

# Binary Decision Diagrams and Faults
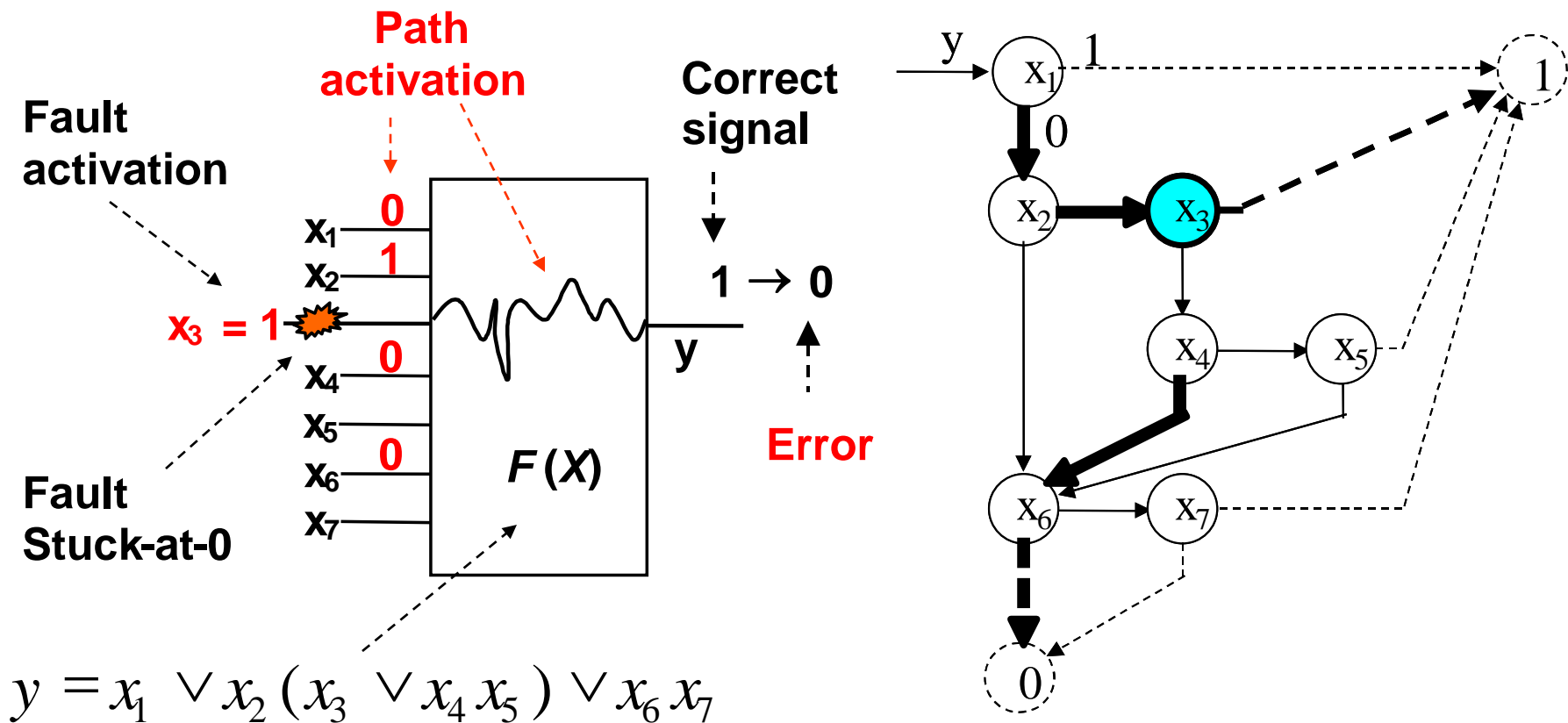
## Fault modeling on Structurally Synthesized BDDs:



# High-Level Decision Diagrams and Faults

RTL-statement:


$$K: (\text{If } T, C) R_D \leftarrow F(R_{S1}, R_{S2}, \dots, R_{Sm}), \rightarrow N$$

**Nonterminal nodes**

RTL-statement faults:  
label,  
timing condition,  
logical condition,  
register decoding,  
operation decoding,  
control faults

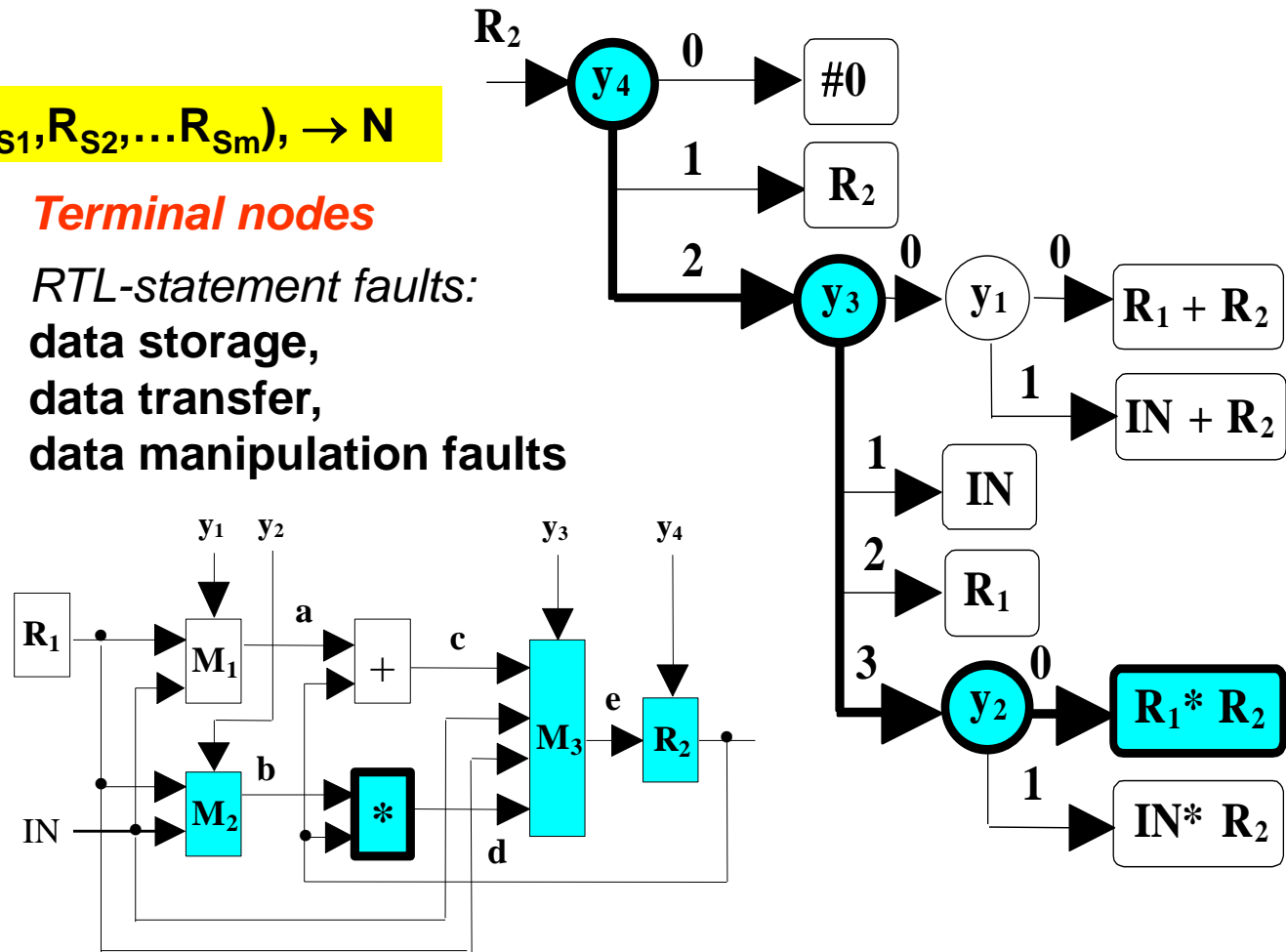**Terminal nodes**

RTL-statement faults:  
data storage,  
data transfer,  
data manipulation faults






# Fault Modeling on DDs

 
## Binary DD

with 2 terminal nodes and  
2 outputs  
from each node



 
## General case of DD

with  $n \geq 2$  terminal nodes and  
 $n \geq 2$  outputs  
from each node


 
# Fault Modeling on DDs

- Each path in a DD describes the behavior of the system in a specific **mode** of operation
- **The faults** having effect on the behaviour can be associated with nodes **along the path**
- A fault causes **incorrect leaving** the path activated by a test




# Uniform Formal Fault Model on DDs

**D1:** the output edge for  $x(m) = i$  of a node  $m$  is **always activated**

**D2:** the output edge for  $x(m) = i$  of a node  $m$  is **broken**

 **D3:** instead of the given edge, **another edge** or a set of edges is **activated**




# Modeling Microprocessors with DDs

## High-Level DDs for a microprocessor (example):

Instruction set:


$I_1$ :	MVI A,D	$A \leftarrow IN$
$I_2$ :	MOV R,A	$R \leftarrow A$
$I_3$ :	MOV M,R	$OUT \leftarrow R$
$I_4$ :	MOV M,A	$OUT \leftarrow A$
$I_5$ :	MOV R,M	$R \leftarrow IN$
$I_6$ :	MOV A,M	$A \leftarrow IN$
$I_7$ :	ADD R	$A \leftarrow A + R$
$I_8$ :	ORA R	$A \leftarrow A \vee R$
$I_9$ :	ANA R	$A \leftarrow A \wedge R$
$I_{10}$ :	CMA A,D	$A \leftarrow \neg A$

DD-model of the  
microprocessor:

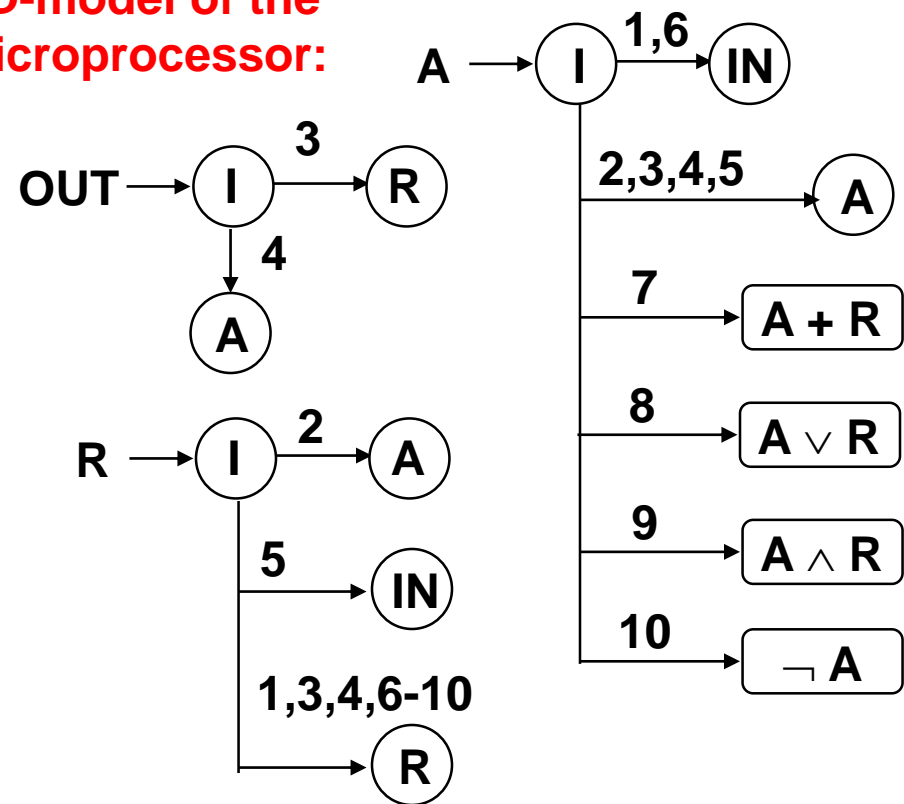

 
# Decision Diagrams for Microprocessors

High-Level DD-based structure of the microprocessor (example):



DD-model of the microprocessor:

 

# From MP Instruction Set to HLDDs




OP	B	Semantic	RT level operations	
0	0	READ memory	$R(A1) = M(A)$	$PC = PC + 2$
	1	WRITE memory	$M(A) = R(A2)$	$PC = PC + 2$
1	0	Transfer	$R(A1) = R(A2)$	$PC = PC + 1$
	1	Complement	$R(A1) = \neg R(A2)$	$PC = PC + 1$
2	0	Addition	$R(A1) = R(A1) + R(A2)$	$PC = PC + 1$
	1	Subtraction	$R(A1) = R(A1) - R(A2)$	$PC = PC + 1$
3	0	Jump	$PC = A$	
	1	Conditional jump	IF C=1, THEN PC = A, ELSE PC = PC + 2	

Instruction code:

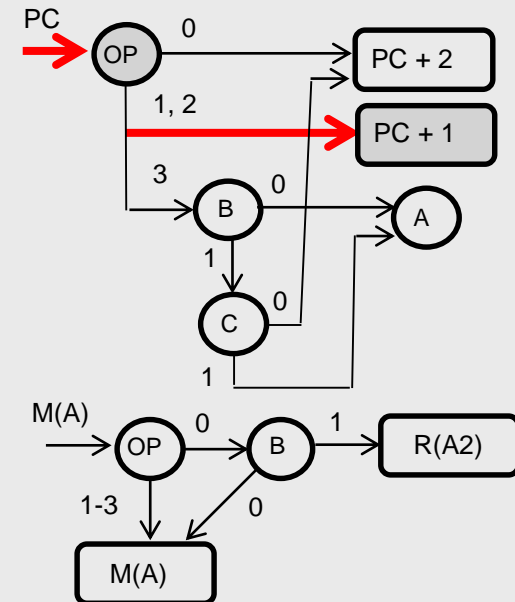 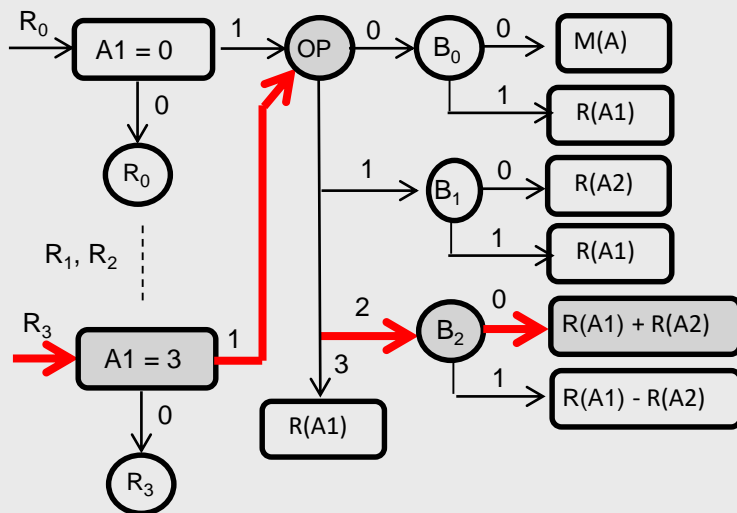
**ADD A1 A2**

OP=2. B=0. A1=3. A2=2

**$R_3 = R_3 + R_2$**   
 **$PC = PC + 1$**



# Uniform Conditional Node Fault Model

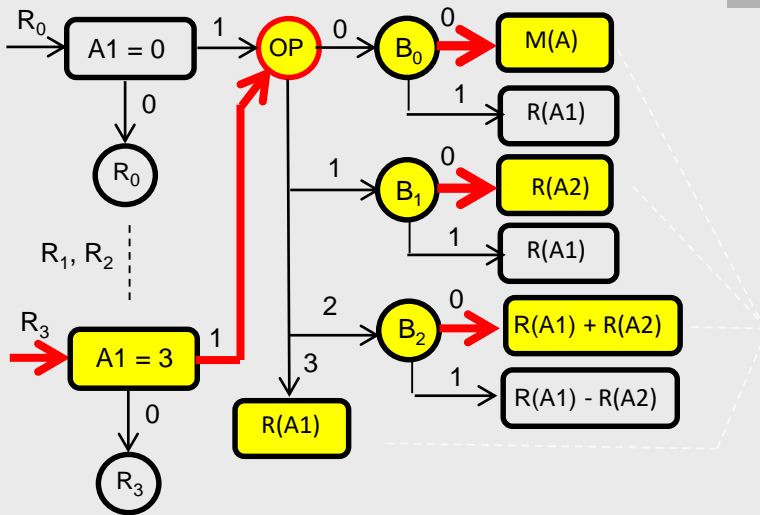


## Test data calculation rules:

$$\forall m^T \in M^T(OP): [ f(m^T) \neq \text{ZERO} ]$$

$$\forall m_i, m_j \in M^T(OP): [ (f(m_i) < f(m_j)) ]$$

Activated  $f(m_i)$

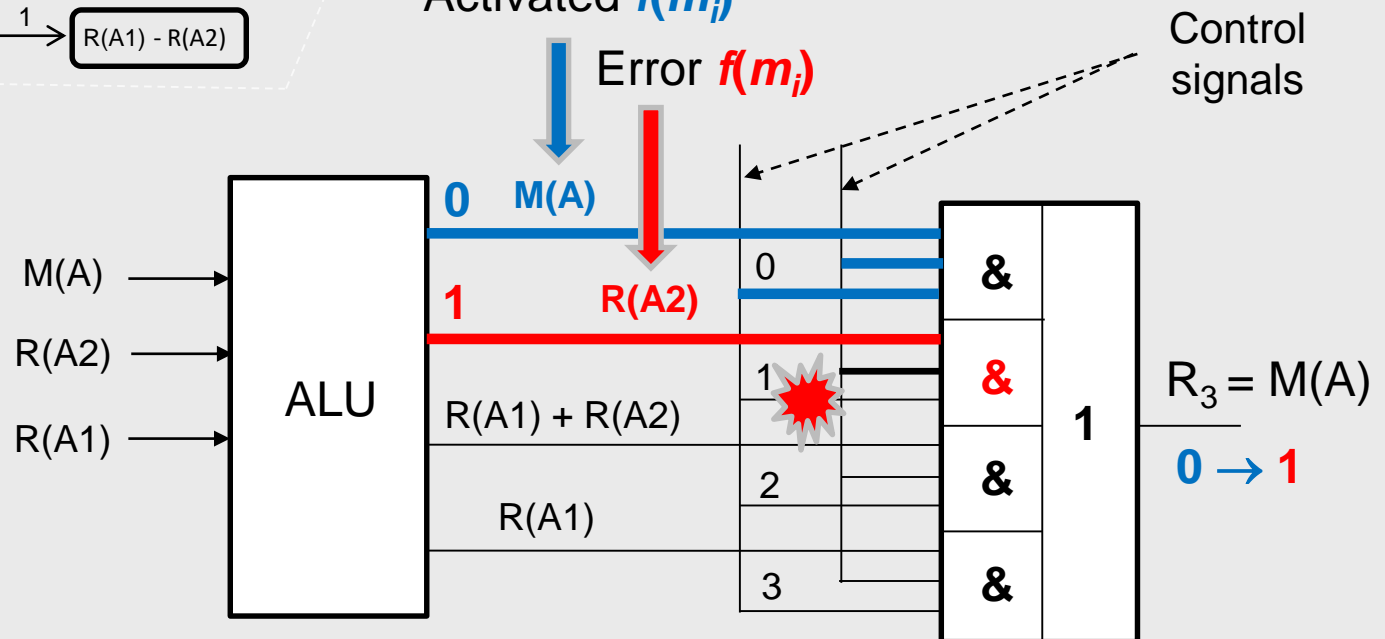Explanation of the meaning of constraints (rules):




To detect the fault:  $R_3 = M(A) \vee R(A2) \longrightarrow M(A) < R(A2)$  is needed

# High-Level Control Fault Coverage Table

 **Functional fault model (for control nodes):**

$$\forall j [f_j \neq \text{ZERO}]$$

$$\forall i, j: \forall k [(f_{i,k} < f_{j,k})]$$



Distinguished Operations $f_i$		Distinguished Operations $f_j$								
		$f_0$	$f_1$	$f_2$	$f_3$	$f_4$	$f_5$	$f_6$	$f_7$	$f_8$
		MOV	ADD	SUB	CMP	AND	OR	XOR	NOT	NOP
$f_0$	MOV	00000000	00110000	00010000	00100000	00000000	00100000	00100000	00110000	00000000
$f_1$	ADD	01001000	00000000	00001000	01001000	01001000	01001000	00000000	00000000	00000000
$f_2$	SUB	11000110	10100110	00000000	11100000	11000000	11100110	00100110	00100000	00000000
$f_3$	CMP	00000111	00010111	00000000	00000000	00000000	00000111	00000111	00010000	00000000
$f_4$	AND	00000111	00110111	00000000	00000000	00000000	00100111	00100111	00110000	00000000
$f_5$	OR	00000000	00010000	00010000	00000000	00000000	00000000	00000000	00010000	00000000
$f_6$	XOR	11001000	10010000	00011000	11001000	11001000	11001000	00000000	00010000	00000000
$f_7$	NOT	11001111	10000111	00001001	11001000	11001000	11001000	11001000	11001000	11001000
$f_8$	NOP	11001111	10110111	00011001	11101000	11101000	11101000	11101000	11101000	11101000


$$f_{i,k} < f_{j,k}$$

**Fault coverage measure:**  
 Percentage of 1-s in the fault coverage table  
 1 – means that the constraint is satisfied by at least one pair of data operands



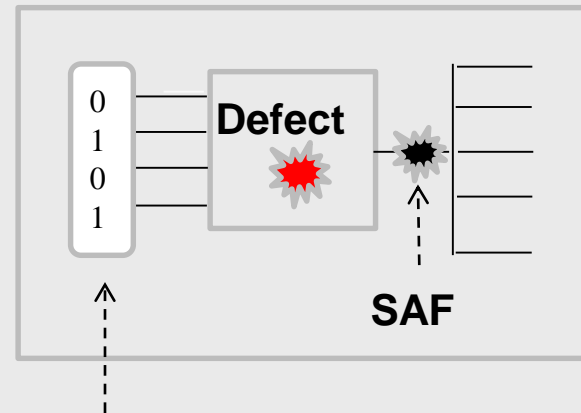
# Uniform Conditional Node Fault Model

**Logic level analog:  
Conditional SAF model**



Condition (constraint)

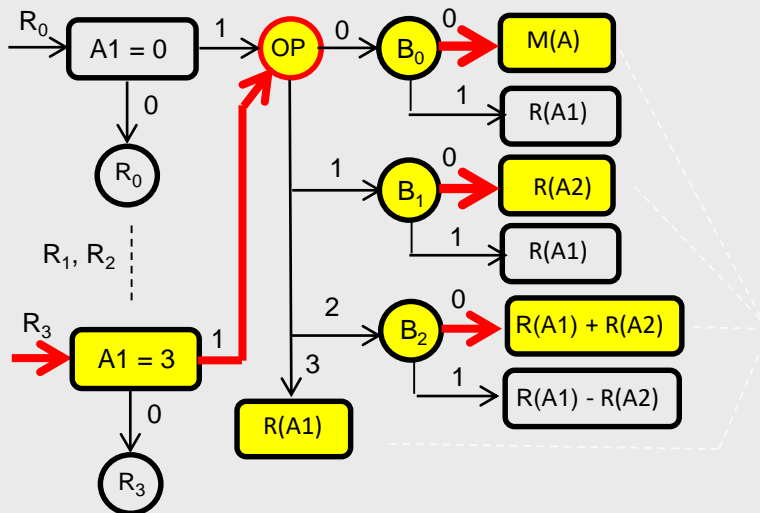**High level fault model: Constraints  
for testing a node *OP* in HLDD:**



**High-level fault model:**

**Test data calculation rules:**


$$\forall m^T \in M^T(OP): [f(m^T) \neq \text{ZERO}]$$

$$\forall m_i, m_j \in M^T(OP): [(f(m_i) < f(m_j))]$$
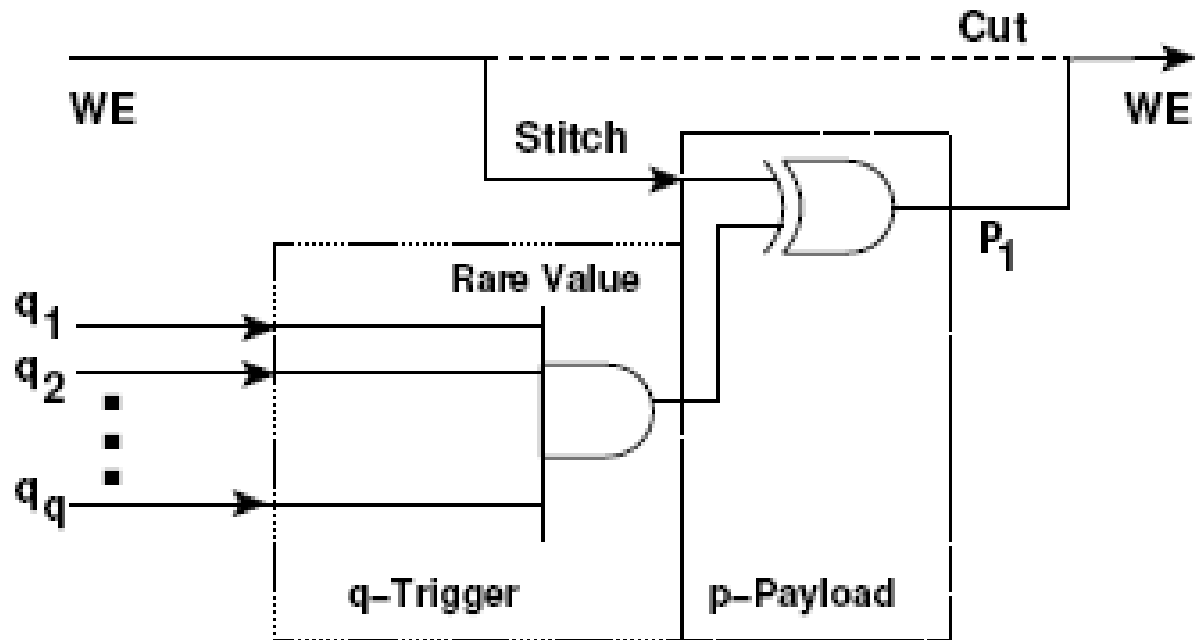
# Functional Fault Modeling: Trojans

A trojan is inserted into a main circuit at manufacturing and is mostly inactive unless it is triggered by a rare value or time event

Then it produces a payload error in the circuit, potentially catastrophic



Copyright © F.Wolf, Ch. Papachristou, S.Bhunia, R.S.Chakraborty 2008

# Conclusions

---

- **Different fault models for different representation levels of digital systems can be replaced on DDs by the uniform node fault model**
- **It allows to represent groups of structural faults through groups of functional faults**
- **As the result, the complexity of fault representation can be reduced, and the simulation speed can be raised**
- **The fault model on DDs can be regarded as a generalization**
  - **of the classical gate-level stuck-at fault model, and**
  - **of the known higher level fault models**