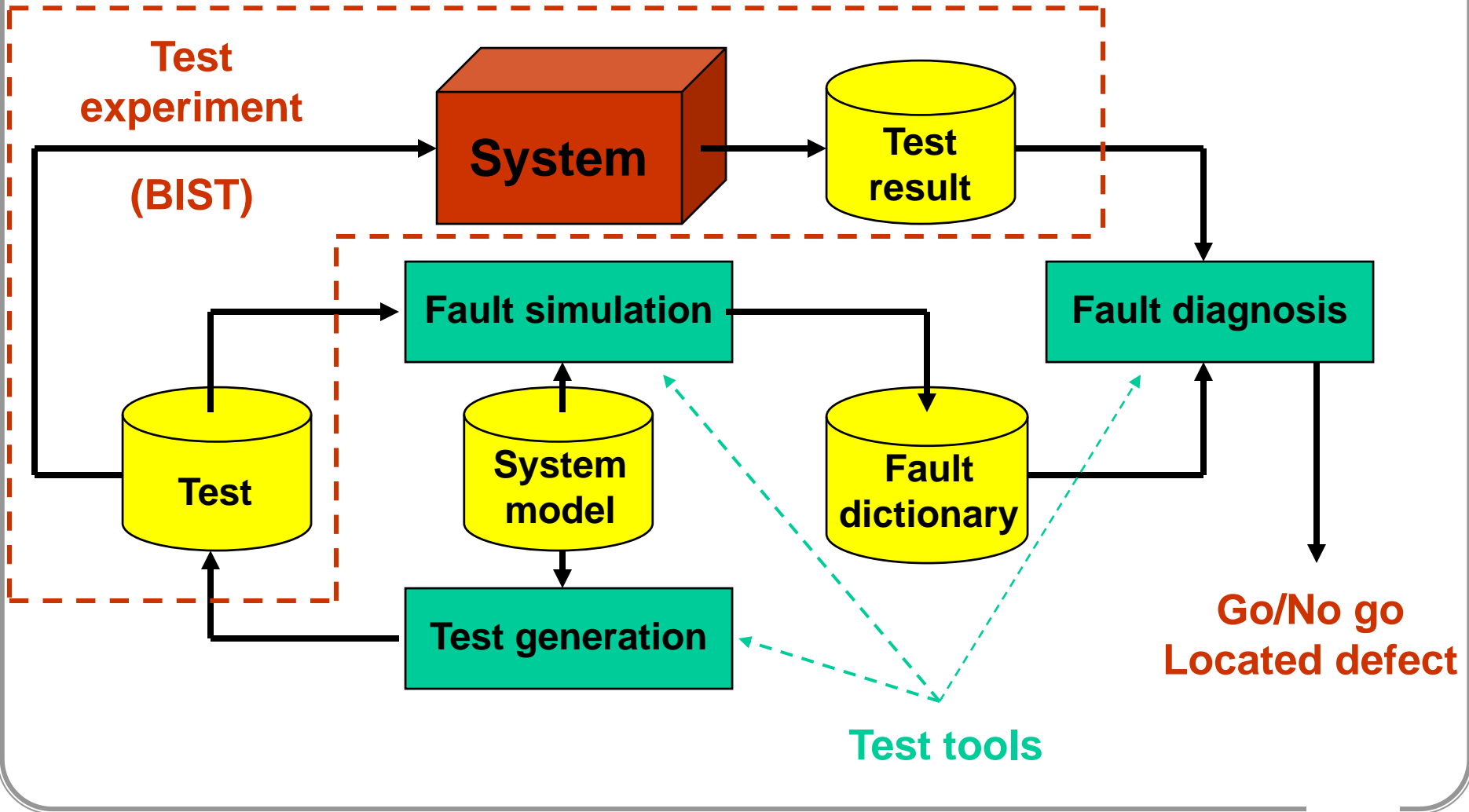



Overview about TESTING: Testing World




Test Related Basic Problems

Relationships between different test tasks

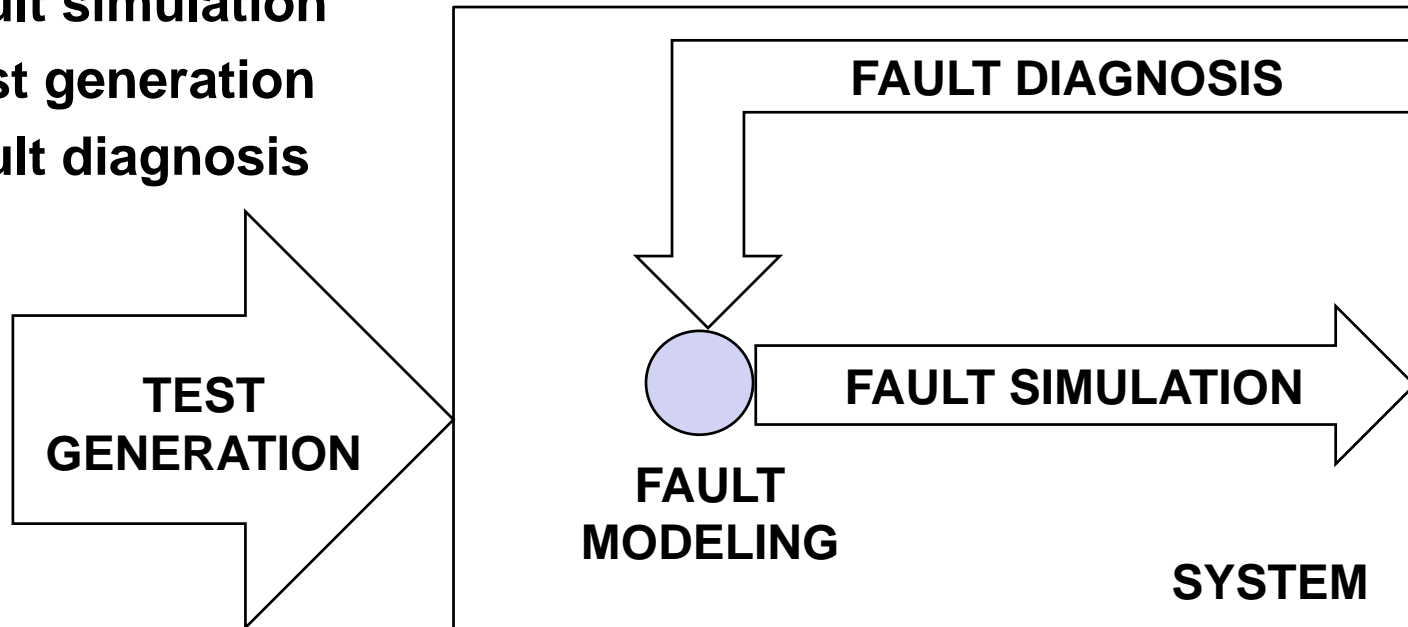- Fault modeling
- Fault simulation
- Test generation
- Fault diagnosis



Test Related Basic Problems

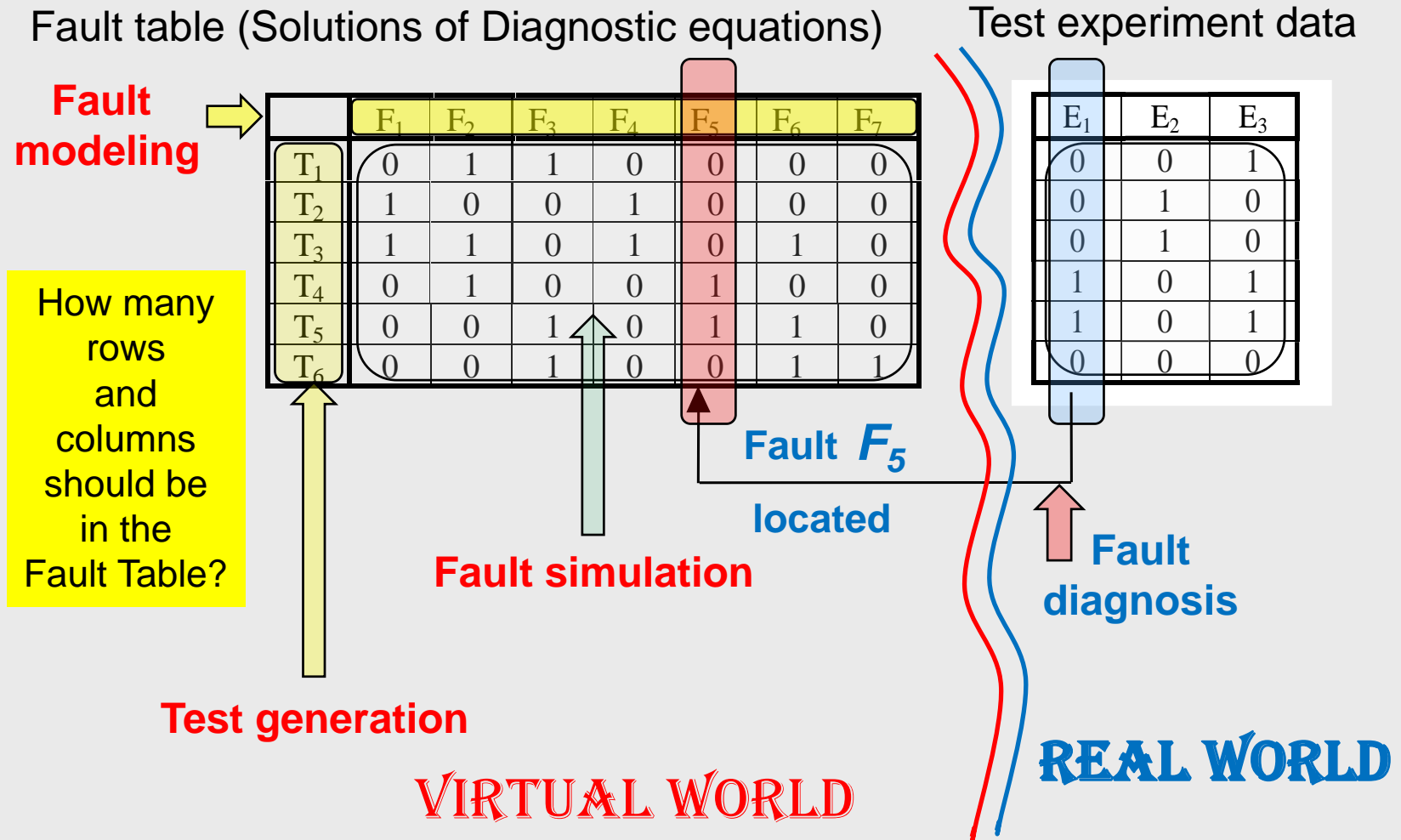


Why We Need Fault Models?

- Fault models are needed for
 - test generation,
 - test quality evaluation and
 - fault diagnosis
- To handle real physical defects is too difficult
- The fault model should
 - reflect accurately the behaviour of defects, and
 - be **computationally efficient**
- Usually combination of different fault models is used
- Fault model free approaches (!)


Fault Modeling: Defects and Faults

Defects, faults and errors

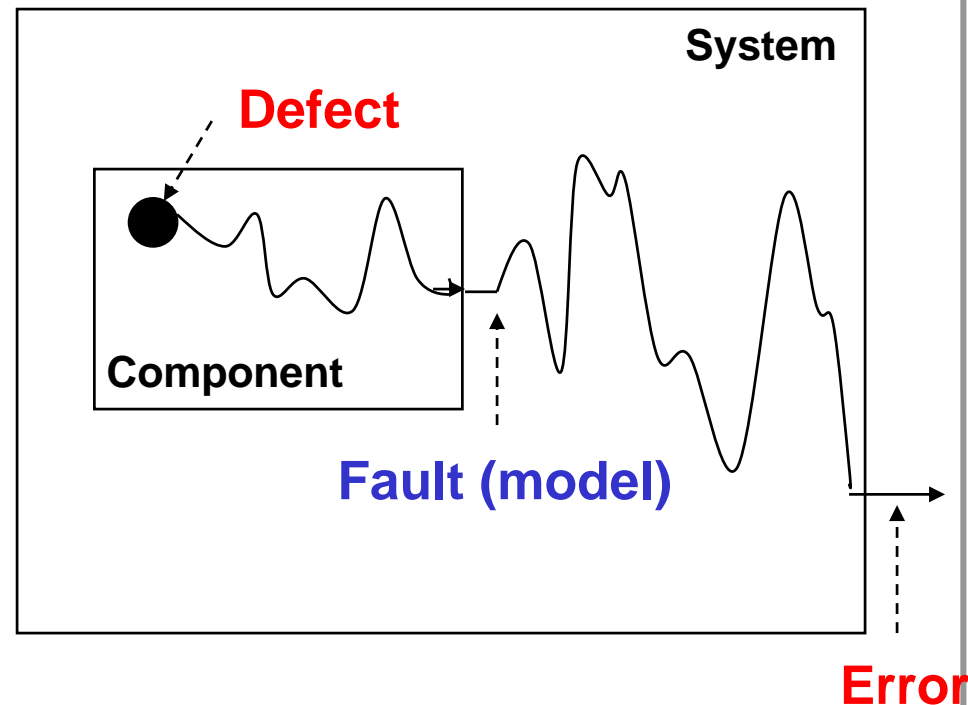- An instance of an incorrect operation of the system being tested is referred to as an **error**
- The causes of the observed errors may be **design errors** or **physical faults (defects)**
- Physical defects do not allow a direct mathematical treatment of testing and diagnosis
- The solution is to deal with **logical fault models**



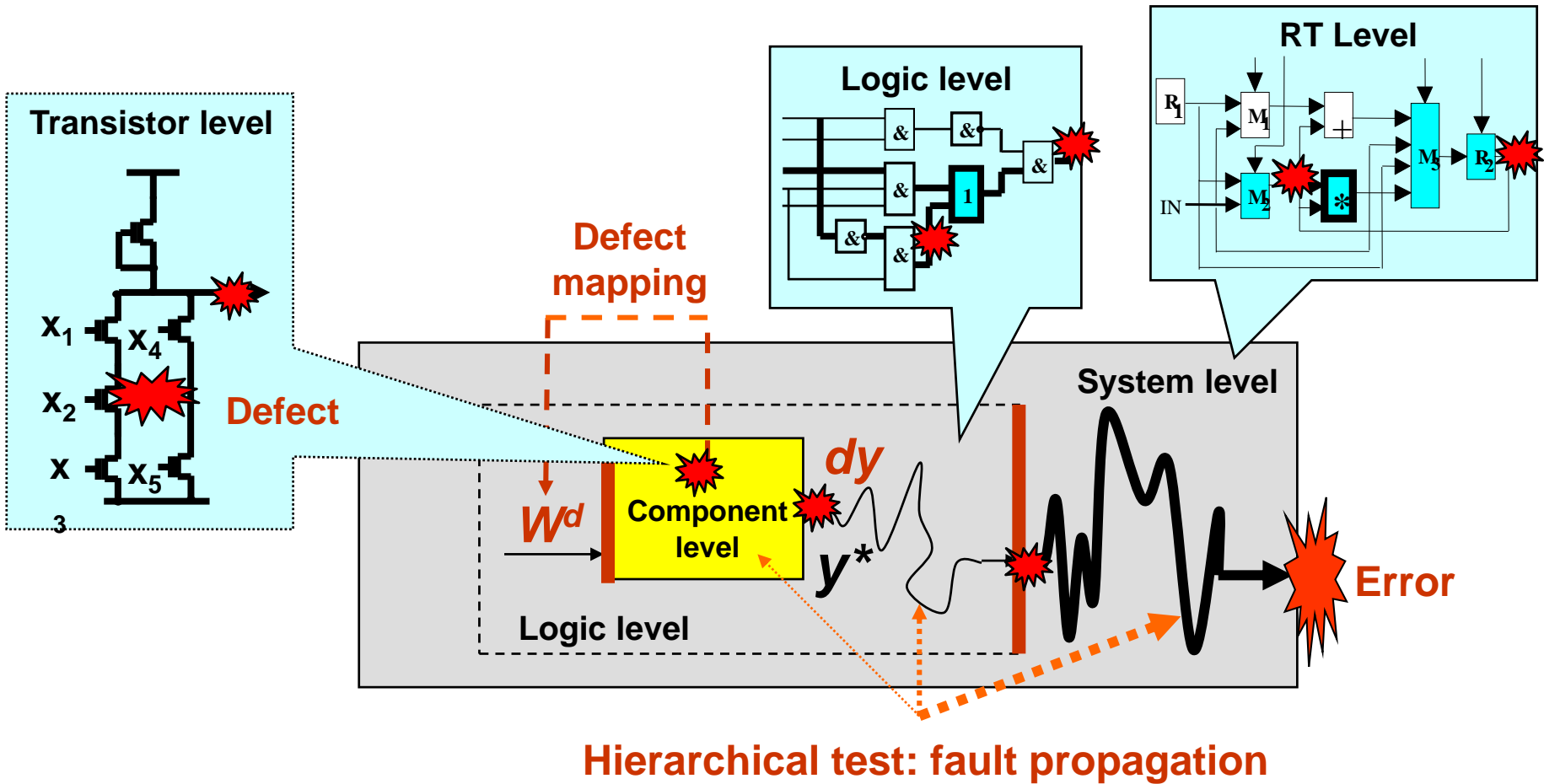Divide & Conquer: Hierarchy is the Solution



N-Dimensional Space of (46?) Test Problems

Test Generation:

Deterministic
Random
Genetic



Test Optimization:

Test Compaction
Testability Design
Signature Analysis



Testing:

External Test
Built-In Self-Test



Fault Diagnosis:

Combinational
Sequential
Fault dictionaries

Fault Simulation:

Single Fault
Parallel Fault
Parallel Pattern

Fault Analysis:

Deductive
Concurrent
Reversible

System classes:

Combinational circuits
Sequential circuits
Finite State Machines
Data Flow Circuits
Microprocessors
Memories
Systems on Chip

Timing:

Synchronous
Asynchronous
Multi-Clocking

Models:

Structural
Functional
Procedural
Behavioral

Hierarchy:

Bottom-up
Top-down
Jo-jo

1 selected
problems field

Fault classes:


Stuck-at-Faults
Bridging faults
Opens
Delay Faults
Physical defects
Functional Faults

Fault Problems:

Multiple Faults
Fault Masking
Fault Dominance
Fault Equivalence
Fault Collapsing
Redundancy

12 dimensions

Faults and fault models

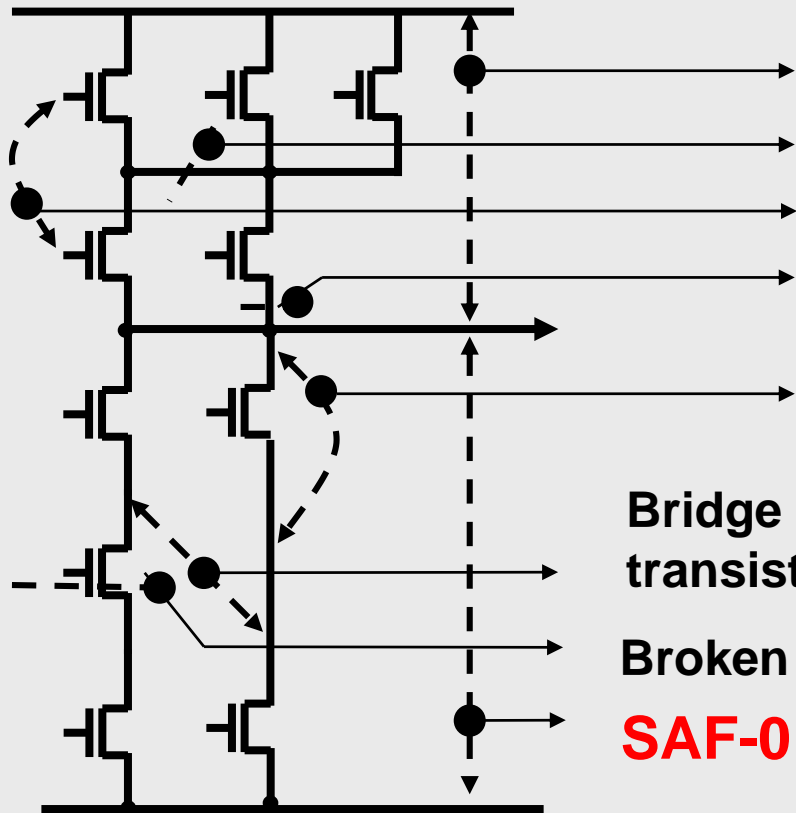

SAF-1

Broken wire

Bridge between wires

Wire "is hanging in then air"



Capacity → Sequential behavior

Short in the transistor

Bridge between transistors

Broken transistor



SAF-0

  

© Mani Soma

Transistor Level Stuck-open Faults

NOR gate

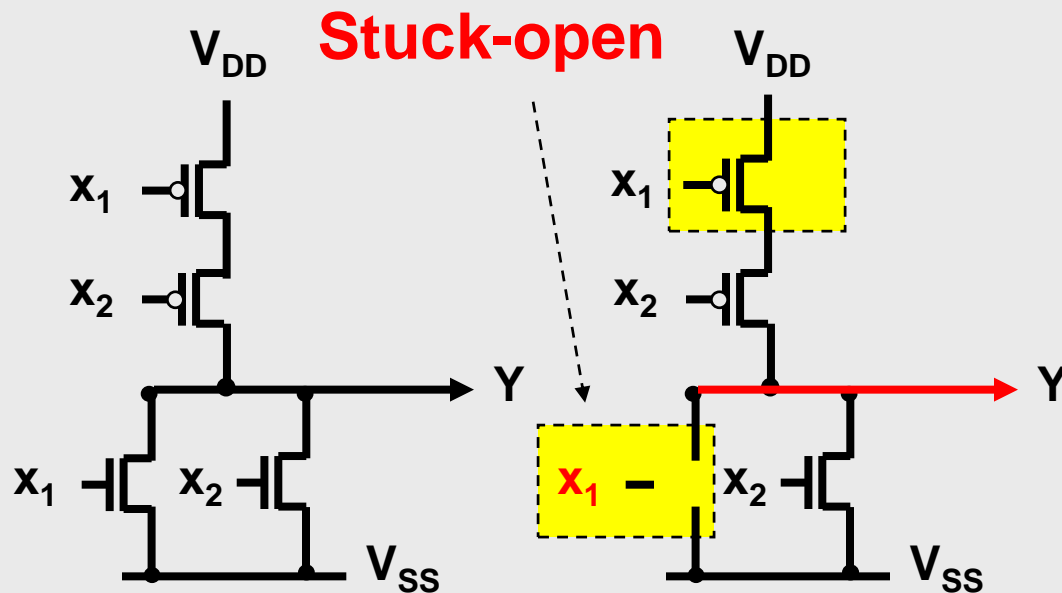 

x_1	x_2	y	y^d
0	0	1	1
0	1	0	0
1	0	0	Y'
1	1	0	0


Test sequence is
needed: 00,10

No conducting path from V_{DD} to V_{SS} for "10"

The wire Y is floating → Capacity is working as a memory

Transistor Level Stuck-On Faults

NOR gate

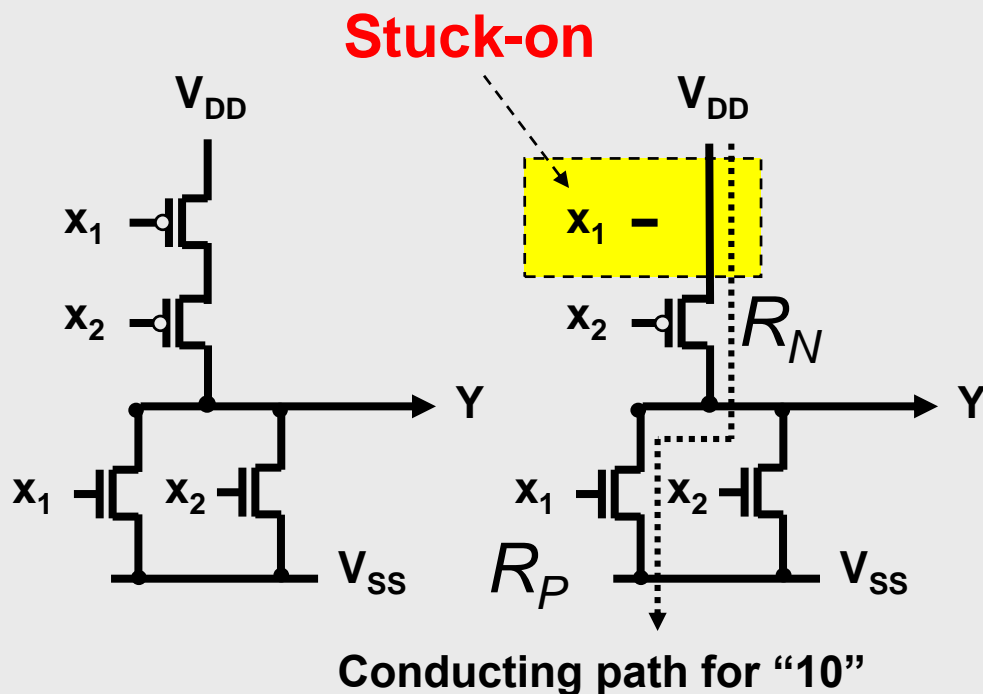

x_1	x_2	y	y^d
0	0	1	1
0	1	0	0
1	0	0	V_Y
1	1	0	0

$$V_Y = \frac{V_{DD} R_P}{(R_P + R_N)}$$

Fault Modeling: Logic Level Faults - SAF


Why logic fault models?

- complexity of simulation reduces (many physical faults may be modeled by the same logic fault)
- one logic fault model is applicable to many technologies
- logic fault tests may be used for physical faults whose effect is not completely understood
- **they give a possibility to move from the lower physical level to the higher logic level**


Stuck-at fault model:

Stuck-at-0

Broken line

 


Bridge to ground

 


Stuck-at-1

Broken line

 


Bridge to Power Supply

 

Fault Cover and Fault Redundancy

- **Fault cover** is a measure of the number of detectable faults
- Why **fault redundancy** is an important and troublesome problem
 - It makes test generation (search for a proper test pattern for the given fault extremely time consuming)

 - n – number of inputs of the circuit
- The search space is 2^n where **backtracks are needed**
- If 64 inputs, then the search space is $2^{64} = 10^{19}$
- **Redundant fault needs the search throughout the full search space**
If not done, the fault cover cannot be calculated trustworthy



- F – number of all faults
 - F_D – number of detected faults
 - FC – fault coverage
 - F_R – number of redundant faults
 - TE – test efficiency
- Fault coverage: $FC = F_D / F$
 - Test efficiency: $TE = F_D / (F - F_R)$

Example:

Faults: $F = 1000$

Redundant faults: $FR = 100$

Detected faults: $FD = 880$

Fault coverage: $FC = 880/1000 = 88\%$

Test efficiency: $TE = 880/900 = 98\%$

Contradiction: between fault tolerance and fault coverage

Problems with Testing: Multiple Faults

- Multiple stuck-fault (**MSF**) model is an extension of the single stuck-fault (**SSF**) where several lines can be simultaneously stuck
- If n - is the number of possible **SSF** sites, there are $2n$ possible **SSFs**, but there are

But $3^n - 1$ possible **MSFs**



Wire a 0,1,x
Wire b 0,1,x


- If we assume that the multiplicity of faults is no greater than k , then the number of possible **MSFs** is

$$N = \sum_{i=1}^k \{C_n^i\} 2^i \ll 3^n - 1 \quad C_n^i = \frac{n!}{i!(n-i)!}$$

- C_n^i - number of sets of i lines, 2^i - number of faults on the set

Fault Modeling: Conditional SAF

 
Very complex faults can be translated (reduced) to SAF model:



Conditional fault
 Pattern fault
 Constrained SAF
Single faulty signal

X-fault
 Byzantine fault
 Bridges
 Stuck-opens
Multiple faulty signal

Resistive bridge fault

 

Gate-Level Faults: SAF Model


Complexity problem:

Number of single faults – $2n$

Number of **multiple** faults – $3^n - 1$

n – is number of wires


**Things are
even worse**

 

Delay Fault Models

Delay faults are tested by test pattern pairs:

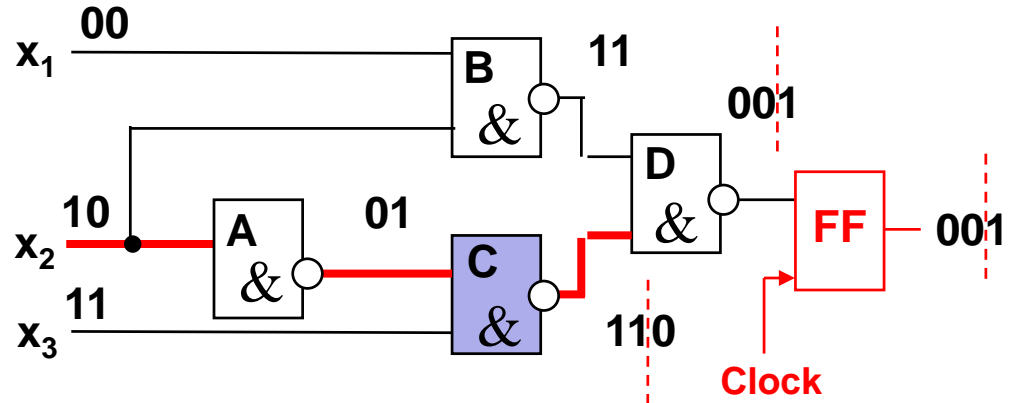
- the first test pattern **initializes** the circuit, and
- the second pattern **sensitizes** the fault



Delay fault models:

- **Gate delay fault** (delay fault is lumped at a single gate, quantitative model)
- **Transition fault** (qualitative model, gross delay fault model, independent of the activated path)
- **Path delay fault** (sum of the delays of gates along a given path)
- **Line delay fault** (is propagated through the longest sensitizable path)
- **Segment delay fault** (tradeoff between the transition and the path delay fault models)

Transition Delay and Path Delay Faults

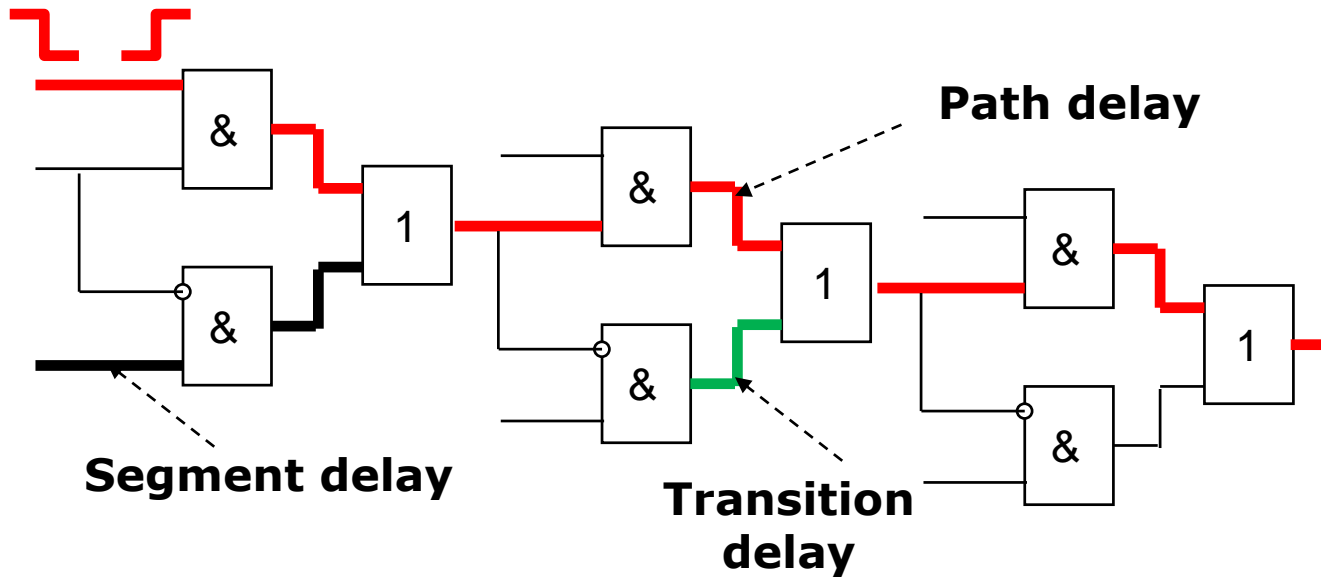

Numbers of faults:

- **Transition faults:** $2 \cdot (18 \text{ lines}) = 36$
- Segment delay faults: $2 \cdot (12 \text{ segments}) = 24$
- **Path delay faults:** $2 \cdot (22 \text{ paths}) = 44$

Number of Paths in Circuits

ISCAS'85 Family of benchmark circuits:

Circuit	Inputs	Outputs	Gates	Levels	Paths
c17	5	2	13	4	11
c32	36	7	203	18	83926
c499	41	32	275	12	9440
c880	60	26	469	25	8642
c1355	41	32	619	25	4173216
c1908	33	25	938	41	729057
c2670	233	140	1566	33	679960
c3540	50	22	1741	48	28676671
c5315	178	123	2608	50	1341305
c6288	32	32	2480	125	98943441738294937238
c7552	207	108	3827	44	726494

Comparison of Delay Faults






Fault models	Advantages	Limitations
Gate delay	All gates can be modeled	<ul style="list-style-type: none"> • Distributed failures not considered • Exact defect size not possible
Transition fault	Easy to model all gates	Distributed failures not considered
Path delay	Distributed failures considered	Impossible to enumerate all paths
Line delay	<ul style="list-style-type: none"> • All gates are modeled • Distributed failures considered • Better coverage metric • Additional fault coverage by using multi-path technique 	<ul style="list-style-type: none"> • Existence of nonrobust test • May fail for some shorter paths
Segment delay	Considers general delay defect from spot to distributed failures	Longest delay path may not be tested

Copyright © A.K.Majhi, V.D.Agrawal 1997

Universal Functional Faults

Exhaustive combinational fault model:

     - exhaustive test patterns
- pseudoexhaustive test patterns
 - exhaustive **output line oriented** test patterns
 - exhaustive **module oriented** test patterns



Advantage: The way to hierarchical approach and to „conquer and divide“ strategy

Fault Modeling: Register Level Faults

RTL statement:

vs. Boolean formulas with Boolean variable
and SAF model ($x \equiv 0, x \equiv 1$)

K: (If T,C) $R_D \leftarrow F(R_{S1}, R_{S2}, \dots R_{Sm}), \rightarrow N$

Components of the statement:
(variable types)

K - label
T - timing condition
C - logical condition
 R_D - destination register
 R_S - source register
F - operation (microoperation)
 \leftarrow - data transfer
 $\rightarrow N$ - jump to the next statement

RT level faults:

$K \rightarrow K'$ - label faults
 $T \rightarrow T'$ - timing faults
 $C \rightarrow C'$ - logical condition faults
 $R_D \rightarrow R_D$ - register decoding faults
 $R_S \rightarrow R_S$ - data storage faults
 $F \rightarrow F'$ - operation decoding faults
 \leftarrow - data transfer faults
 $\rightarrow N$ - control faults
 $(F) \rightarrow (F)'$ - data manipulation faults

Disadvantage: Too many fault dedicated models, abstraction, formalization and tool support are missing, test program generation is a manual work today

Microprocessor Fault Model

Faults affecting the operation of microprocessor can be divided into the following classes:

- addressing faults affecting **register decoding**
- addressing faults affecting the **instruction decoding** and – sequencing functions;
- faults in the **data-storage** function;
- faults in the **data-transfer** function;
- faults in the **data-manipulation** function

Disadvantage: Formalization and tool support are missing, test program generation is a manual work today

Summary of Overview

- **Main tools and tasks**
 - Test generation
 - Fault Simulation
 - Fault Diagnosis
- **Different fault types**
 - Logic faults, X-faults, Timing (delay) faults, High-Level faults
- **Fault modeling**
 - Low-level fault models (SAF, transistor faults, bridging, delays)
 - High-level fault models (RTL, microprocessors)

Fault Simulation

Fault table

Test experiment data

Fault modeling

How many rows and columns should be in the Fault Table?

Test generation

	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇
T ₁	0	1	1	0	0	0	0
T ₂	1	0	0	1	0	0	0
T ₃	1	1	0	1	0	1	0
T ₄	0	1	0	0	1	0	0
T ₅	0	0	1	0	1	1	0
T ₆	0	0	1	0	0	1	1

E ₁	E ₂	E ₃
0	0	1
0	1	0
0	1	0
1	0	1
1	0	1
0	0	0

Fault F₅ located

Fault simulation

Fault diagnosis

Testing

Comparison of Fault Simulation Methods


Fault simulation techniques:

- serial fault simulation
- parallel fault simulation
- deductive fault simulation
- concurrent fault simulation
- critical path analysis
- parallel critical path analysis

Common concepts:

- fault specification (fault collaps)
- fault insertion
- fault effect propagation
- fault discarding (dropping)

Comparison of methods:

 


Entry $(i,j) = 1(0)$ if F_i is detectable
(not detectable) by T_j

Single and Parallel Fault Simulation


Single pattern

Parallel patterns


Fault-free circuit:

 


Fault-free circuit: Three test patterns

 

Faulty circuit:

 


Faulty circuit:

 


Fault Simulation: Critical Path Tracing

 
Activated (critical) path
is traced backwards



Problems:

 


The critical path is not continuous

 


The critical path breaks on the fan-out

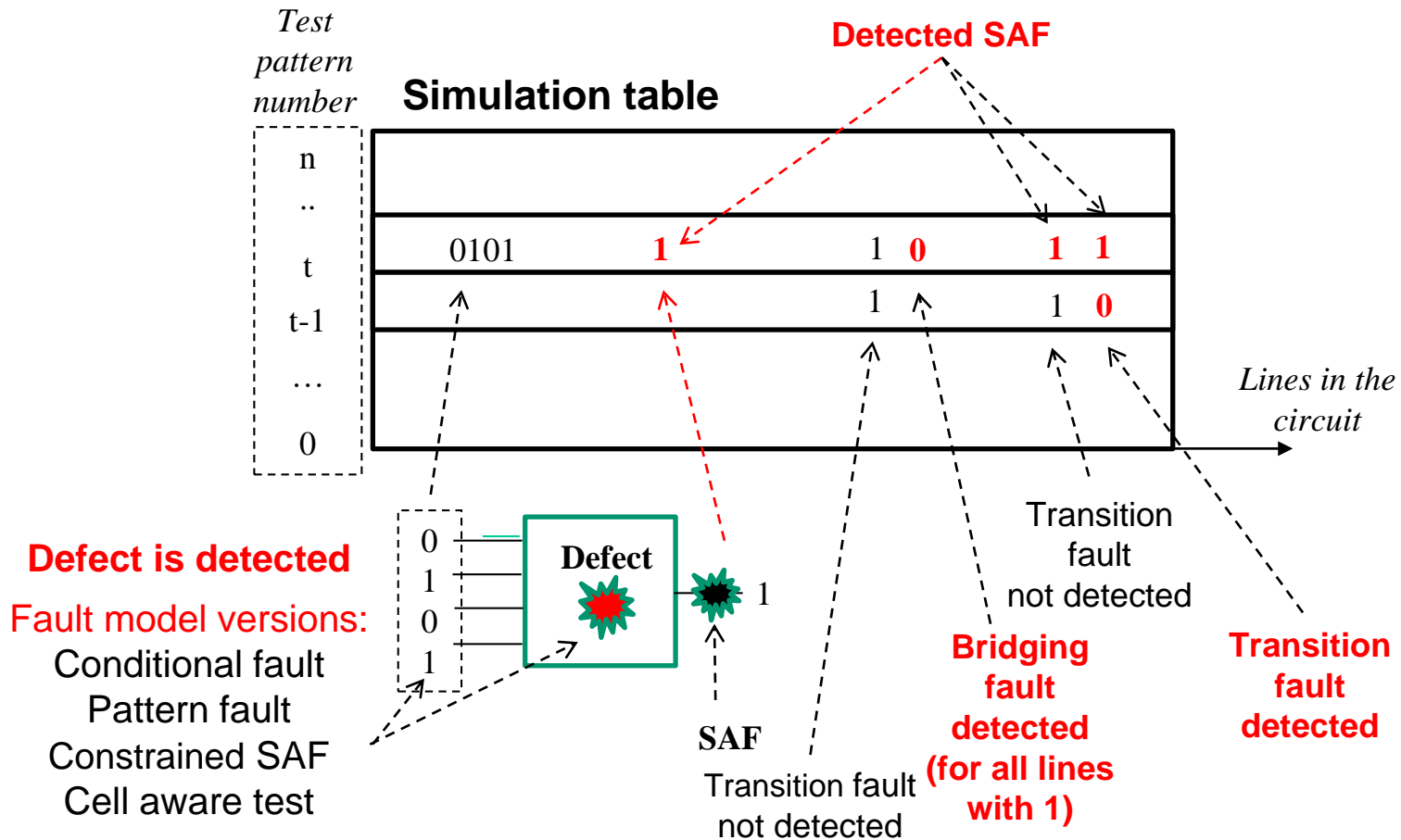Simulation of Different Classes of Faults





Testing of Bridging Fault Models

Wired AND model

 

W-AND:

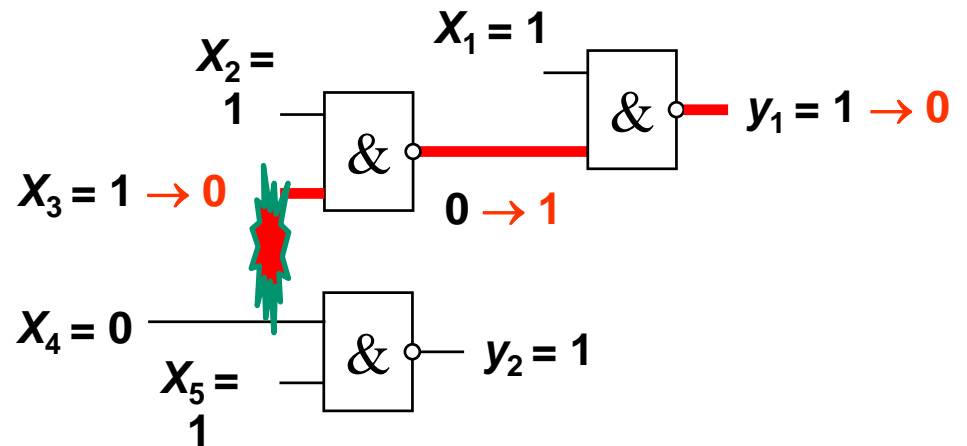 


Turbo-Tester Data Formats

Circuit

Blue colour – variables

Red colour – nodes (fault locations)

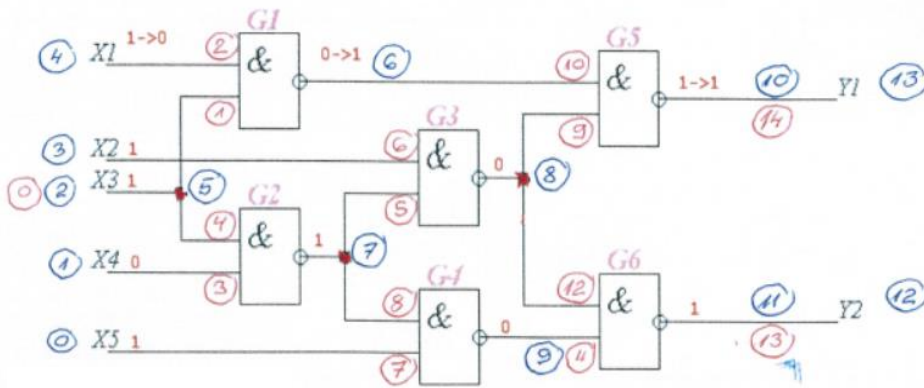

Circuit model

STAT# 15 Nods, 14 Vars, 9 Grps, 5 Inps, 0 Cons, 2 Outs

MODE# STRUCTURAL

```

VAR# 0: (i_____) "i_5"
VAR# 1: (i_____) "i_4"
VAR# 2: (i_____) "i_3"
VAR# 3: (i_____) "i_2"
VAR# 4: (i_____) "i_1"

VAR# 5: (_____) "i_3"
GRP# 0: BEG = 0, LEN = 1 -----
0 0: (_____) ( 0 0) V = 2 "i_3"

VAR# 6: (_____) "inst_0>o"
GRP# 1: BEG = 1, LEN = 2 -----
1 0: (I____) ( 1 0) V = 5 "inst_0>i_1"
2 1: (I____) ( 0 0) V = 4 "i_1"

VAR# 7: (_____) "inst_1>o"
GRP# 2: BEG = 3, LEN = 2 -----
3 0: (I____) ( 1 0) V = 1 "i_4"
4 1: (I____) ( 0 0) V = 5 "inst_1>i_2"

VAR# 8: (_____) "inst_2>o"
GRP# 3: BEG = 5, LEN = 2 -----
5 0: (I____) ( 1 0) V = 7 "inst_2>i_1"
6 1: (I____) ( 0 0) V = 3 "i_2"

VAR# 9: (_____) "inst_3>o"
GRP# 4: BEG = 7, LEN = 2 -----
7 0: (I____) ( 1 0) V = 0 "i_5"
8 1: (I____) ( 0 0) V = 7 "inst_3>i_2"

VAR# 10: (_____) "inst_4>o"
GRP# 5: BEG = 9, LEN = 2 -----
9 0: (I____) ( 1 0) V = 8 "inst_4>i_1"
10 1: (I____) ( 0 0) V = 6 "inst_0>o"

VAR# 11: (_____) "inst_5>o"
GRP# 6: BEG = 11, LEN = 2 -----
11 0: (I____) ( 1 0) V = 9 "inst_3>o"
12 1: (I____) ( 0 0) V = 8 "inst_5>i_2"

VAR# 12: (o_____) "o_2"
GRP# 7: BEG = 13, LEN = 1 -----
13 0: (_____) ( 0 0) V = 11 "inst_5>o"

VAR# 13: (o_____) "o_1"
GRP# 8: BEG = 14, LEN = 1 -----
14 0: (_____) ( 0 0) V = 10 "inst_4>o"
    
```

Simulation table (variables)

01234 5678901 23

```

11110 hhlhhl LL
11001 lhhhll HL
00011 lhhllh HH
10101 hlhhll HH
01000 lhhhl LL
    
```

Fault table (nodes)

25415 73078 69810 < variables
01234 56789 01234 < nodes


```

0X100 1XX10 00011
11XX1 X1000 01X01
XXXXX 00XX1 XX100
0001X XX00X 11X00
XXXXX X11X0 00011
    
```

Delay Fault Models

Delay faults are tested by test pattern pairs:

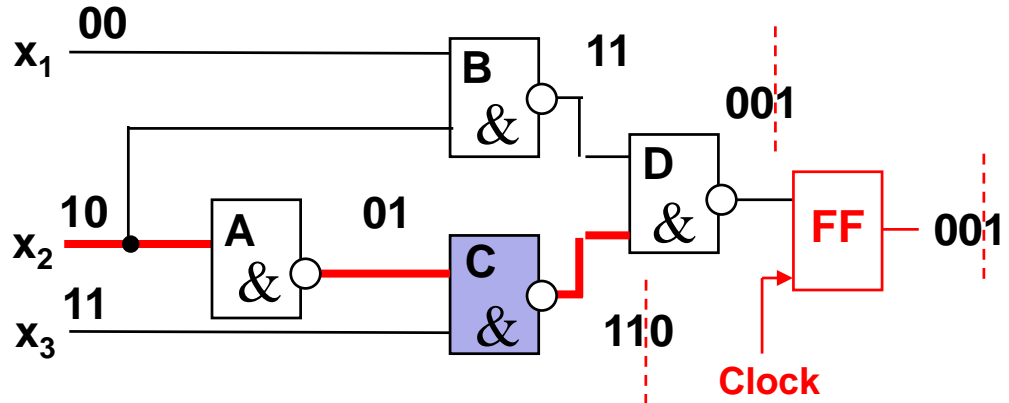- the first test pattern **initializes** the circuit, and
- the second pattern **sensitizes** the fault



Delay fault models:

- **Gate delay fault** (delay fault is lumped at a single gate, quantitative model)
- **Transition fault** (qualitative model, gross delay fault model, independent of the activated path)
- **Path delay fault** (sum of the delays of gates along a given path)
- **Line delay fault** (is propagated through the longest sensitizable path)
- **Segment delay fault** (tradeoff between the transition and the path delay fault models)

Simulation of Delay Faults

Optimization of the test sequence by reordering the patterns

Example: Converting of SAF fault table into the delay fault table

	1	2	3	4
T1	0	1	1	0
T2	1	1	1	0
T3	1	0	1	1
T4	0	1	0	0
7	1	2	2	2



	1	2	3	4
T1	0	1	1	0
T3	1	0	1	1
T2	1	1	1	0
T4	0	1	0	0
6	1	2	1	2



	1	2	3	4
T1	0	1	1	0
T3	1	0	1	1
T4	0	1	0	0
T2	1	1	1	0
8	2	2	2	2

↑
Number of all detected delay faults

Numbers of detected delay faults in columns

Full fault coverage is achieved

Procedure (greedy algorithm):

- 1) Find the test pair with maximum of the Hamming distance and set this pair as the first two patterns
- 2) Find for the second pattern the companion from the rest of patterns with maximum of the Hamming distance
- 3) Continue the algorithm till the next to the last pattern

Fault Table based Diagnosis

Combinational fault diagnosis

Two phases:

- 1) The full test (all test patterns) is executed, and the **result vector** E_k is fixed
- 2) A match for E_k in the fault table with a column vector F_j is found
- 3) The column vector F_j refers to the **fault** F_j

	F_1	F_2	F_3	F_4	F_5	F_6	F_7
T_1	0	1	1	0	0	0	0
T_2	1	0	0	1	0	0	0
T_3	1	1	0	1	0	1	0
T_4	0	1	0	0	1	0	0
T_5	0	0	1	0	1	1	0
T_6	0	0	1	0	0	1	1

E_1	E_2	E_3
0	0	1
0	1	0
0	1	0
1	0	1
1	0	1
0	0	0

Faults F_1 and F_4 are not distinguishable

Fault F_5 located

No match, diagnosis not possible

Fault Diagnosis

Sequential (adaptive) fault diagnosis by **Edge-Pin Testing**

Test patterns are executed in a sequence one-by-one. Depending on the test result, the next pattern will be selected and executed. Beforehand a diagnostic tree can be constructed

	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇
T ₁	0	1	1	0	0	0	0
T ₂	1	0	0	1	0	0	0
T ₃	1	1	0	1	0	1	0
T ₄	0	1	0	0	1	0	0
T ₅	0	0	1	0	1	1	0
T ₆	0	0	1	0	0	1	1


Diagnostic tree:

Two faults F_1, F_4 remain indistinguishable

Not all test patterns used in the fault table are needed

Different faults need for identifying test sequences with different lengths


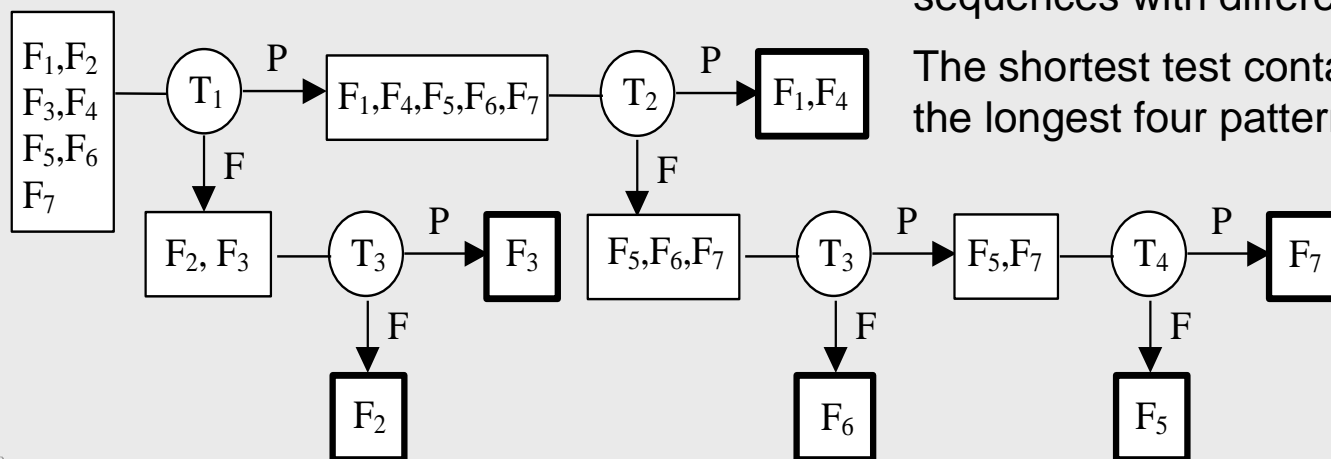
The shortest test contains two patterns, the longest four patterns



Sequential Fault Diagnosis

Guided-probe testing inside the circuit

Search tree:

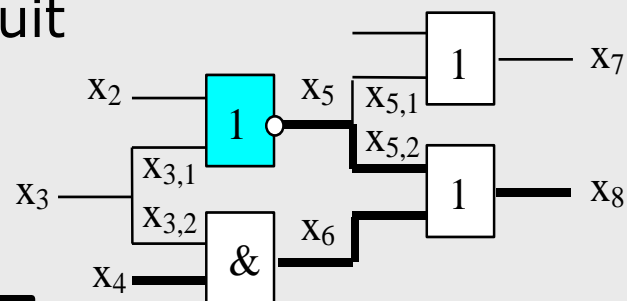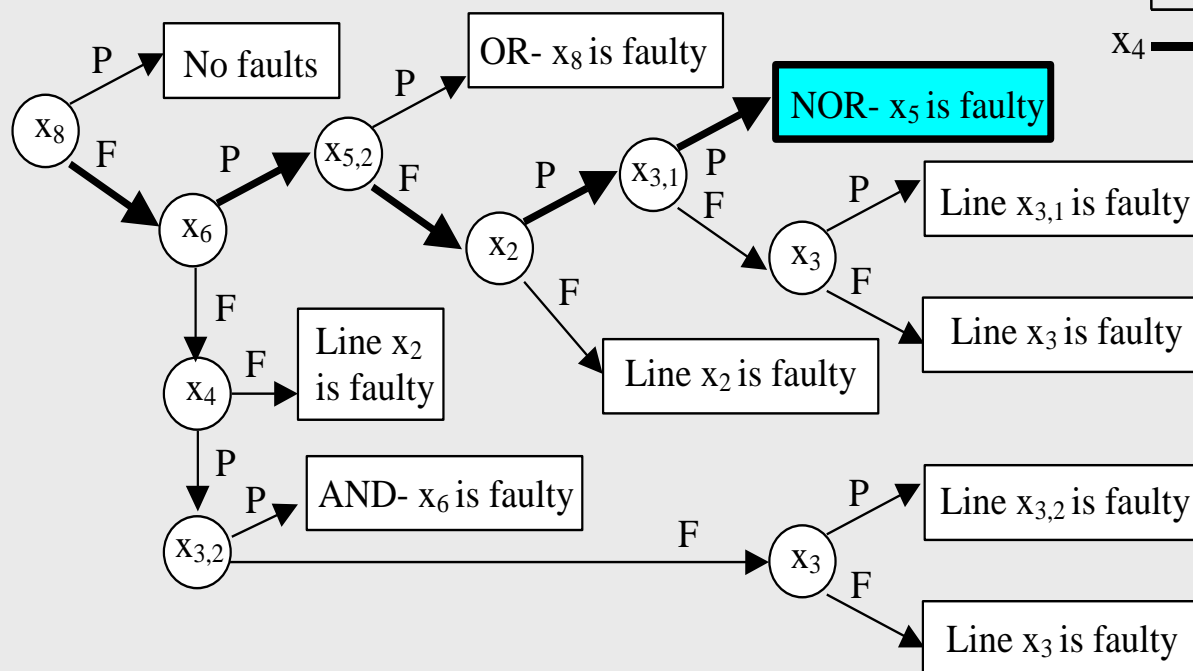


Faulty circuit

Differently from the previous methods, in this approach multiple faults can be independently located

The Problem of Diagnosis: A Good Strategy

Let us begin from the whole picture

 

Fault candidates

↓
1,2,3,4
T1

+ OK

+ 3,4
T4

- 1,2
T2

- 1
T3

+ 4

- 3

+ 2

- 1



Thereafter: divide and conquer

The average length of the fault location procedure:

$$1 + 4 * 3 = 13/5 = 2,6$$

An Example of a Bad Strategy

One-by-one search

 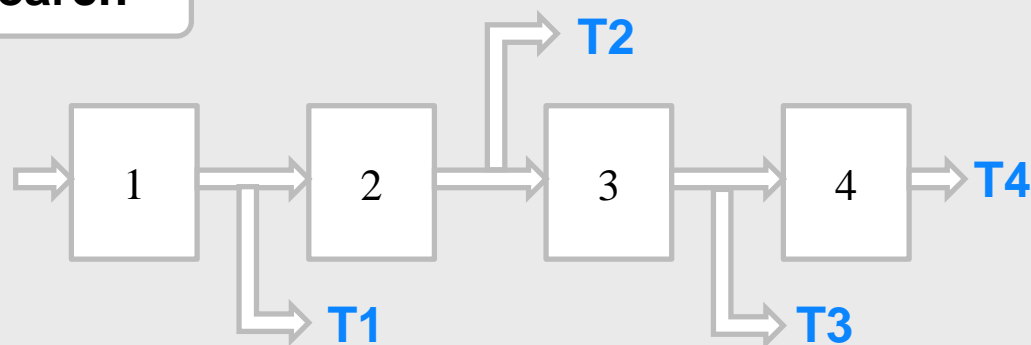



The previous
result was :
2,6

The average length of the fault location procedure:

$$(1 + 2 + 3 + 4 * 2) / 5 = 14 / 5 = 2,8$$

Optimization Using Statistics

  Probability of faults may be different in different modules



The previous results were :

2,6 & 2,8

The average length of the fault location procedure:

$$(1 * 0,6 + 2 * 0,2 + 3 * 0,1 + 4 * 0,1 * 2) = \mathbf{2,1}$$

Test Generation

Fault table

Test experiment data

Fault modeling

	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇
T ₁	0	1	1	0	0	0	0
T ₂	1	0	0	1	0	0	0
T ₃	1	1	0	1	0	1	0
T ₄	0	1	0	0	1	0	0
T ₅	0	0	1	0	1	1	0
T ₆	0	0	1	0	0	1	1

E ₁	E ₂	E ₃
0	0	1
0	1	0
0	1	0
1	0	1
1	0	1
0	0	0

How many rows and columns should be in the Fault Table?

Fault simulation

Fault F_5 located

Fault diagnosis

Testing

Test generation

Test Generation Methods

Gate-level methods

- **Functional testing:** universal test sets
- **Structural test generation**
 - Path activation conception
 - Algorithms: D, Podem, Fan
 - Test generation for multiple faults
 - Test generation for sequential circuits
- **Random test generation**
- **Genetic algorithms for test generation**

High-level and hierarchical methods

- Test generation for **digital systems**
- Test generation for **microprocessors**

Exhaustive Testing

Universal test sets

1. Exhaustive test (trivial test)

2. Pseudo-exhaustive test

Properties of (pseudo)exhaustive tests

1. **Advantages** (concerning the stuck at fault model):

- test pattern generation is not needed
- fault simulation is not needed
- no need for a fault model
- **easily generated on-line by hardware**
- redundancy problem is eliminated
- single and multiple stuck-at fault coverage is 100%

2. **Shortcomings:**


- long test length (2^n patterns are needed, n - is the number of inputs)
- CMOS stuck-open fault problem

Pseudoexhaustive Testing


Pseudo-exhaustive test sets:

- Output function verification
 - maximal parallel testability
 - partial parallel testability
- Segment function verification

Output function verification

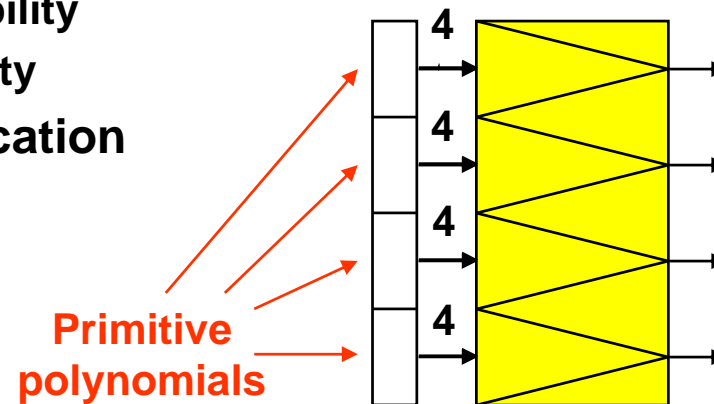

Segment function verification

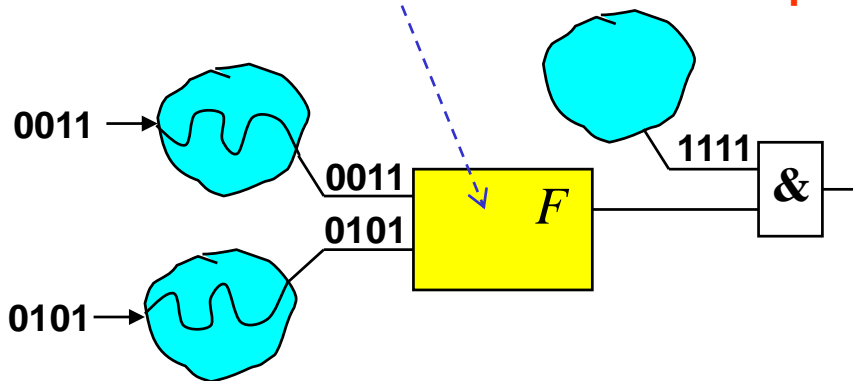


$$2^{16} = 65536 \gg 4 \times 16 = 64 > 16$$

Exhaustive test

Pseudo-exhaustive sequential

Pseudo-exhaustive parallel

Faults as Test Generation Objectives

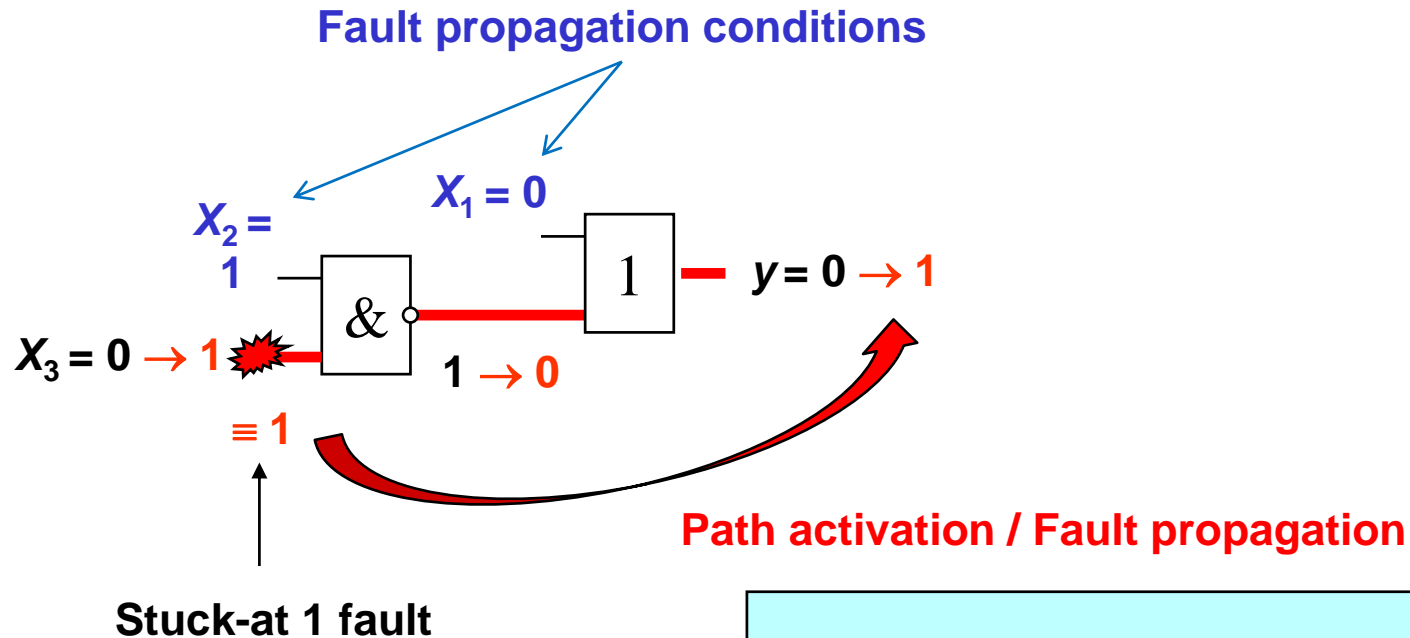

$(x_3 = 0 \rightarrow 1) \rightarrow (y = 0 \rightarrow 1)$

Output is depending on input change

Test Generation: Stuck-at-Faults (SAF)


Structural gate-level testing: fault sensitization

Fault detection

- A test $t = 1101$ is simulated, both without and with the fault $a/0$
- The fault is detected since the output values in the two cases are different


Why is fault detected?

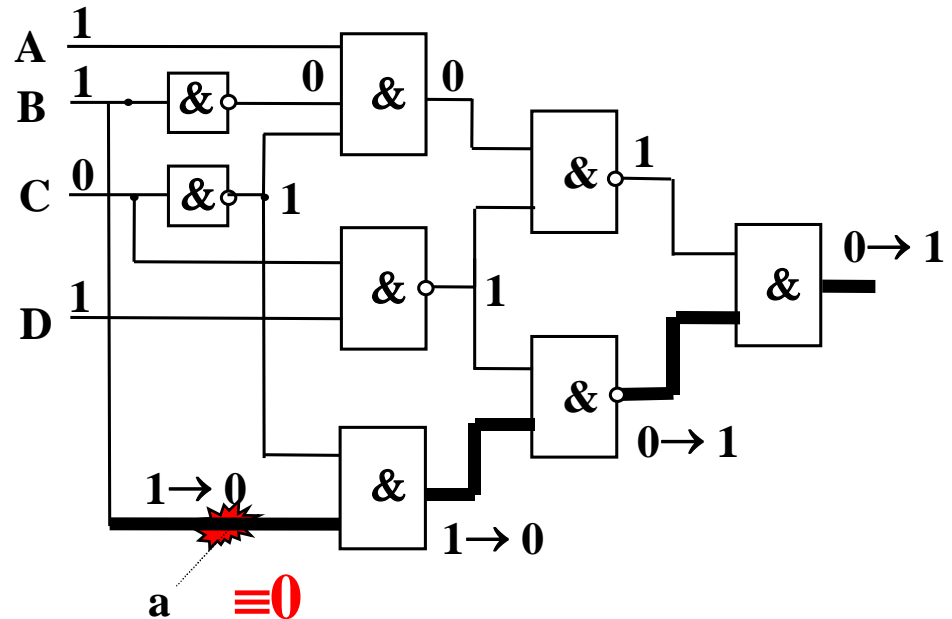- A **fault $a/0$ is sensitized** by the value 1 on a line a
- A **path** from the faulty line a **is sensitized** (bold lines) to the primary output




Fault Propagation Problem

Logic gate

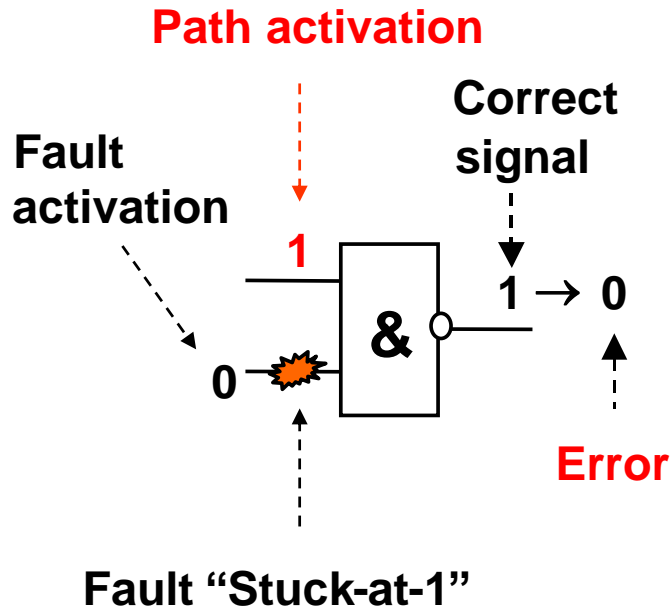


Logic circuit

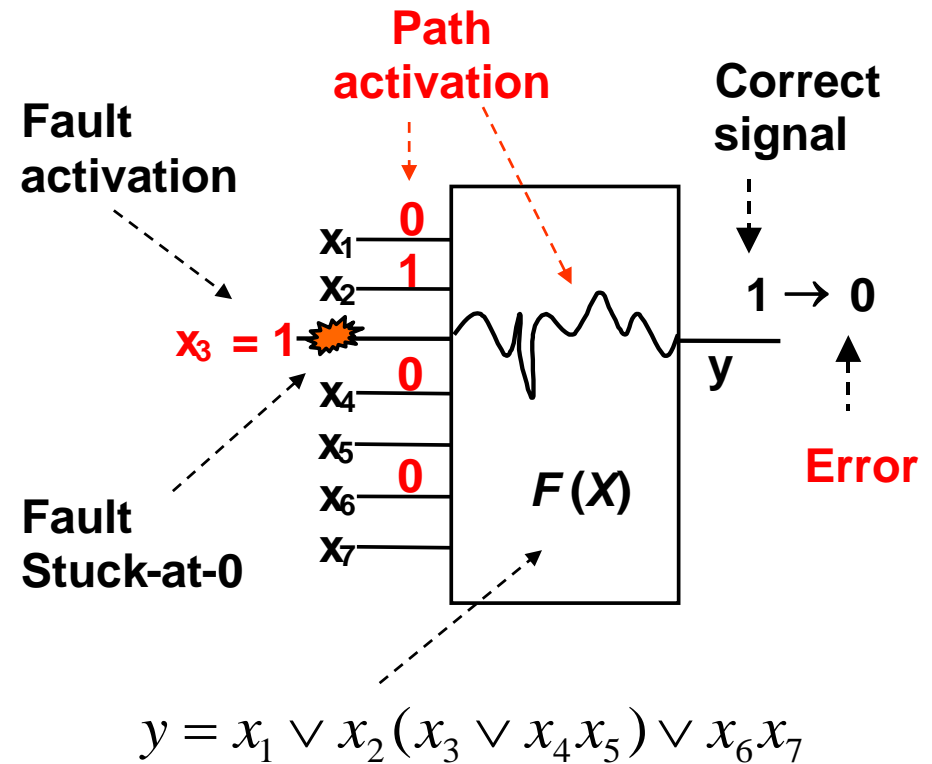

Structural Test Generation: Main Principles

Single path fault propagation:

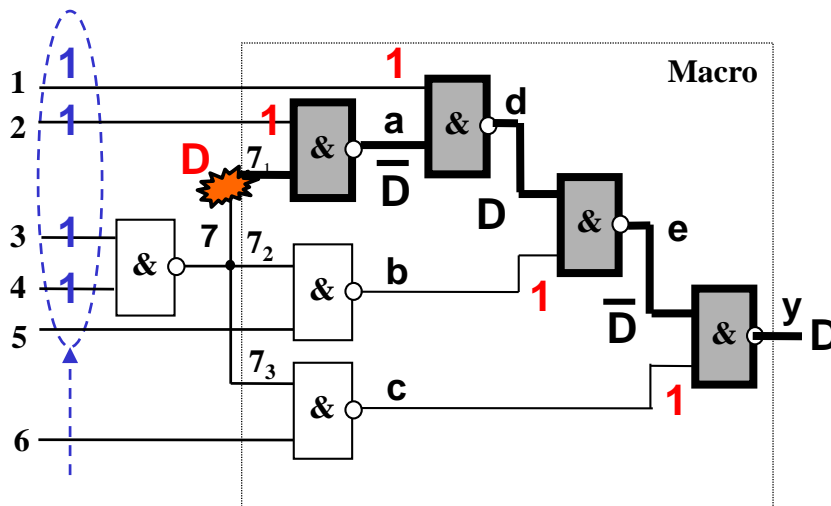

Test pattern

$$y = x_6 x_{7,3} \vee (\overline{x_1} \vee x_2 x_{7,1}) (\overline{x_5} \vee \overline{x_{7,2}})$$

Fault sensitisation:

$$x_{7,1} = D$$

Fault propagation:

$$x_2 = 1, x_1 = 1, b = 1, c = 1$$

Line justification:

$$x_7 = D = 0: x_3 = 1, x_4 = 1$$

b = 1: (already justified)

c = 1: (already justified)


Symbolic fault modeling:

D = 0 - if fault is missing

D = 1 - if fault is present


Test Generation: Conditional SAF

 Generalization: Bridging Fault > Conditional SAF




Conditional fault
 Pattern fault
 Constrained SAF
Single faulty signal

 X-fault
 Byzantine fault
 Bridges
 Stuck-opens
Multiple faulty signal



SAF:

 


$x_3 = 1 \rightarrow 0$

Bridge \rightarrow

$x_4 = 0$




Condition

 

Boolean Derivatives

Traditional algebra: **speed**

 

Boolean algebra: **change**

$$x \in \{0,1\}, Y = F(X)$$

$$Y \in \{0,1\}$$

$$\frac{\partial F(X)}{\partial x_i} = 1$$

F(X) will change
if x_i changes

$$\frac{\partial F(X)}{\partial x_i} = 0$$

F(X) will not change
if x_i changes

Reverse function: **$Y = F(X, dX)$**

Test generation:
(Calculation of the value of
reverse function)

$$X = g^{-1}(dY = 1, dX)$$

Boolean derivatives

Boolean function:

$$Y = F(x) = F(x_1, x_2, \dots, x_n)$$

Boolean partial derivative:

$$\frac{\partial F(X)}{\partial x_i} = F(x_1, \dots, x_i, \dots, x_n) \oplus F(x_1, \dots, \bar{x}_i, \dots, x_n) = \mathbf{1}$$

Simplified equation:

$$\frac{\partial F(X)}{\partial x_i} = F(x_1, \dots, x_i = 0, \dots, x_n) \oplus F(x_1, \dots, x_i = 1, \dots, x_n) = \mathbf{1}$$

Test generation: $X = g^{-1}(dY = 1, dX)$

Boolean Derivatives

Useful properties of Boolean derivatives:

For $F(x)$ not depending on x_i

$$\frac{\partial [F(X)G(X)]}{\partial x_i} = F(X) \frac{\partial G(X)}{\partial x_i}$$

$$\frac{\partial [F(X) \vee G(X)]}{\partial x_i} = \overline{F(X)} \frac{\partial G(X)}{\partial x_i}$$

Example: $x_1 x_4 (x_2 x_3 \vee x_2 \overline{x_3})$

$$F(X) = x_1 x_4 \quad G(X) = x_2 x_3 \vee x_2 \overline{x_3}$$

$$\frac{\partial [F(X)G(X)]}{\partial x_2} = x_1 x_4 \frac{\partial G(X)}{\partial x_2}$$

Continue the same for $\frac{\partial G(X)}{\partial x_i}$

These properties allow to simplify the Boolean differential equation to be solved for generating test pattern for a fault at x_i

Calculation of Boolean Derivatives

Special cases for differential equations:

$$\frac{\partial F(X)}{\partial x_i} \equiv 0 \quad - \quad \text{if } F(x) \text{ is independent of } x_i$$

$$\frac{\partial F(X)}{\partial x_i} \equiv 1 \quad - \quad \text{if } F(x) \text{ depends always on } x_i$$

$$\frac{\partial F(X)}{\partial x_i} = F(x_1, \dots, x_i = 0, \dots, x_n) \oplus F(x_1, \dots, x_i = 1, \dots, x_n)$$

Examples:

$$F(X) = x_1(x_2x_3 \vee x_2\bar{x}_3) : \quad \frac{\partial F(X)}{\partial x_3} = x_1x_2 \oplus x_1x_2 \equiv 0$$

$$F(X) = x_1 \oplus x_2 : \quad \frac{\partial F(X)}{\partial x_1} = \bar{x}_2 \oplus x_2 \equiv 1$$

Calculation of Boolean Derivatives

Example:

Given: $y = x_1 x_2 \vee x_3 (\overline{x_2 x_4} \vee \overline{x_1 (x_4 \vee (x_5 \vee \overline{x_2 x_6}))}) \vee \overline{x_1 x_3}$

Calculation of the Boolean derivative:

$$\begin{aligned} \frac{\partial y}{\partial x_5} &= \overline{x_1 x_2 \vee x_1 x_3} \frac{\partial (x_3 (\overline{x_2 x_4} \vee \overline{x_1 (x_4 \vee (x_5 \vee \overline{x_2 x_6}))}))}{\partial x_5} = \\ &= \overline{x_1 x_2 \vee x_1 x_3} x_3 \frac{\partial (\overline{x_2 x_4} \vee \overline{x_1 (x_4 \vee (x_5 \vee \overline{x_2 x_6}))})}{\partial x_5} = \\ &= \overline{x_1 x_2 \vee x_1 x_3} x_3 \overline{x_2 x_4} \frac{\partial (\overline{x_1 (x_4 \vee (x_5 \vee \overline{x_2 x_6}))})}{\partial x_5} = \\ &= \overline{x_1 x_2 \vee x_1 x_3} x_3 \overline{x_2 x_4} \overline{x_1} \frac{\partial (x_4 \vee (x_5 \vee \overline{x_2 x_6}))}{\partial x_5} = \overline{x_1 x_2 \vee x_1 x_3} x_3 \overline{x_2 x_4} \overline{x_1} x_4 x_2 x_6 \frac{\partial x_5}{\partial x_5} \end{aligned}$$

Calculation of Boolean derivatives

Finding a solution of the differential equation:


$$\begin{aligned} \frac{\partial y}{\partial x_5} &= \overline{(x_1 x_2 \vee x_1 x_3)} x_3 \overline{(x_2 x_4)} x_1 x_4 \overline{(x_2 x_6)} \frac{\partial x_5}{\partial x_5} = \\ &= (\overline{x_1} \vee \overline{x_2})(\overline{x_1} \vee \overline{x_3}) x_3 (x_2 \vee \overline{x_4}) x_1 x_4 (x_2 \vee \overline{x_6}) = \\ &= \overline{x_1} \overline{x_4} x_3 x_2 \vee \dots = 1 \end{aligned}$$

The DNF will include all solutions

$$\frac{\partial y}{\partial x_5} = \overline{x_1} \overline{x_4} x_3 (x_2 \vee \overline{x_6}) = \overline{x_1} \overline{x_4} x_3 x_2 = 1 \quad \Longrightarrow \quad \left\{ \begin{array}{l} x_1 = 0 \\ x_4 = 0 \\ x_3 = 1 \\ x_2 = 1 \end{array} \right.$$


Test pattern is found:

BDDs and Testing of Logic Circuits

 

$$y = x_1 \vee x_2 (x_3 \vee x_4 x_5) \vee x_6 x_7$$

 Topological view on Binary Decision Diagrams:



Test Generation with BD and BDD

BD:


$$y = x_1 x_2 \vee x_3 (\overline{x_2} x_4 \vee \overline{x_1} (x_4 \vee (x_5 \vee \overline{x_2} x_6))) \vee x_1 \overline{x_3}$$

$$\begin{aligned} \frac{\partial y}{\partial x_5} &= (\overline{x_1} \overline{x_2} \vee \overline{x_1} x_2) x_3 (\overline{x_2} x_4) x_1 x_4 (\overline{x_2} x_6) \frac{\partial x_5}{\partial x_5} = \\ &= (\overline{x_1} \vee x_2) (\overline{x_1} \vee x_2) x_3 (\overline{x_2} \vee x_4) x_1 x_4 (\overline{x_2} \vee x_6) = \\ &= \overline{x_1} x_4 x_3 x_2 \vee \dots = 1 \end{aligned}$$

Test pattern:

x_1	x_2	x_3	x_4	x_5	x_6	y
0	1	-	0	D	-	D


BDD:

 


Functional Synthesis of BDDs

Shannon's Expansion Theorem: $y = F(X) = x_k F(X)|_{x_k=1} \vee \overline{x_k} F(X)|_{x_k=0}$

$$y = x_1 \underbrace{\overline{x_2(x_3 \vee x_4) \vee x_2}}_{x_1 F(X)|_{x_1=1}} \vee \overline{x_1} \underbrace{x_3 x_4}_{\overline{x_1} F(X)|_{x_1=0}}$$

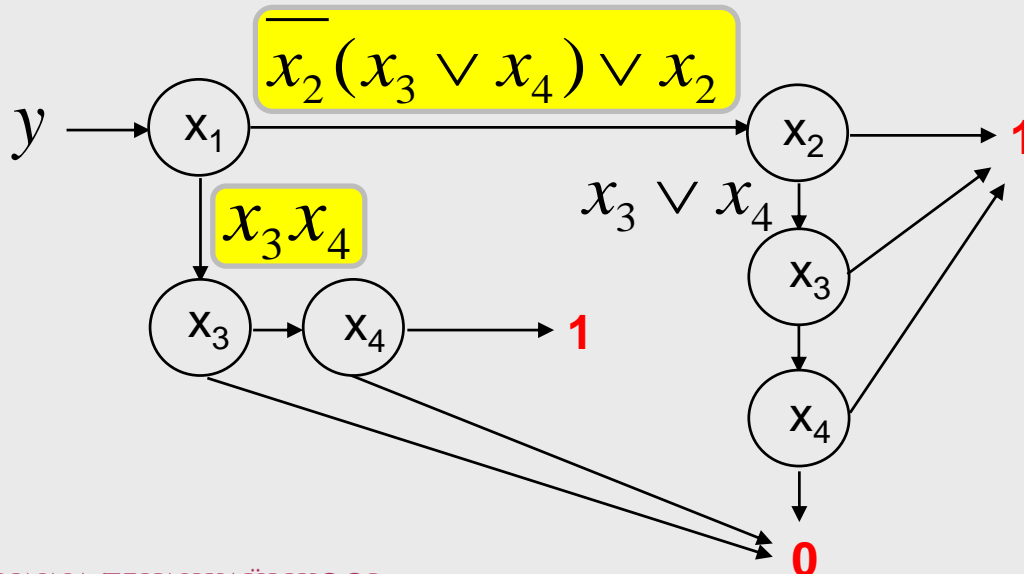



Using the Theorem for BDD synthesis:

 

Functional Synthesis of BDDs

Shannon's Expansion Theorem: $y = F(X) = x_k F(X)|_{x_k=1} \vee \overline{x_k} F(X)|_{x_k=0}$
  
$$y = x_1(\overline{x_2}(x_3 \vee x_4) \vee x_2) \vee \overline{x_1}x_3x_4$$




Optimization possibilities:

- ✓ Several terminal nodes with the same variables can be merged
- ✓ Equivalent terminal subgraphs can be also merged

BDDs and Complexity

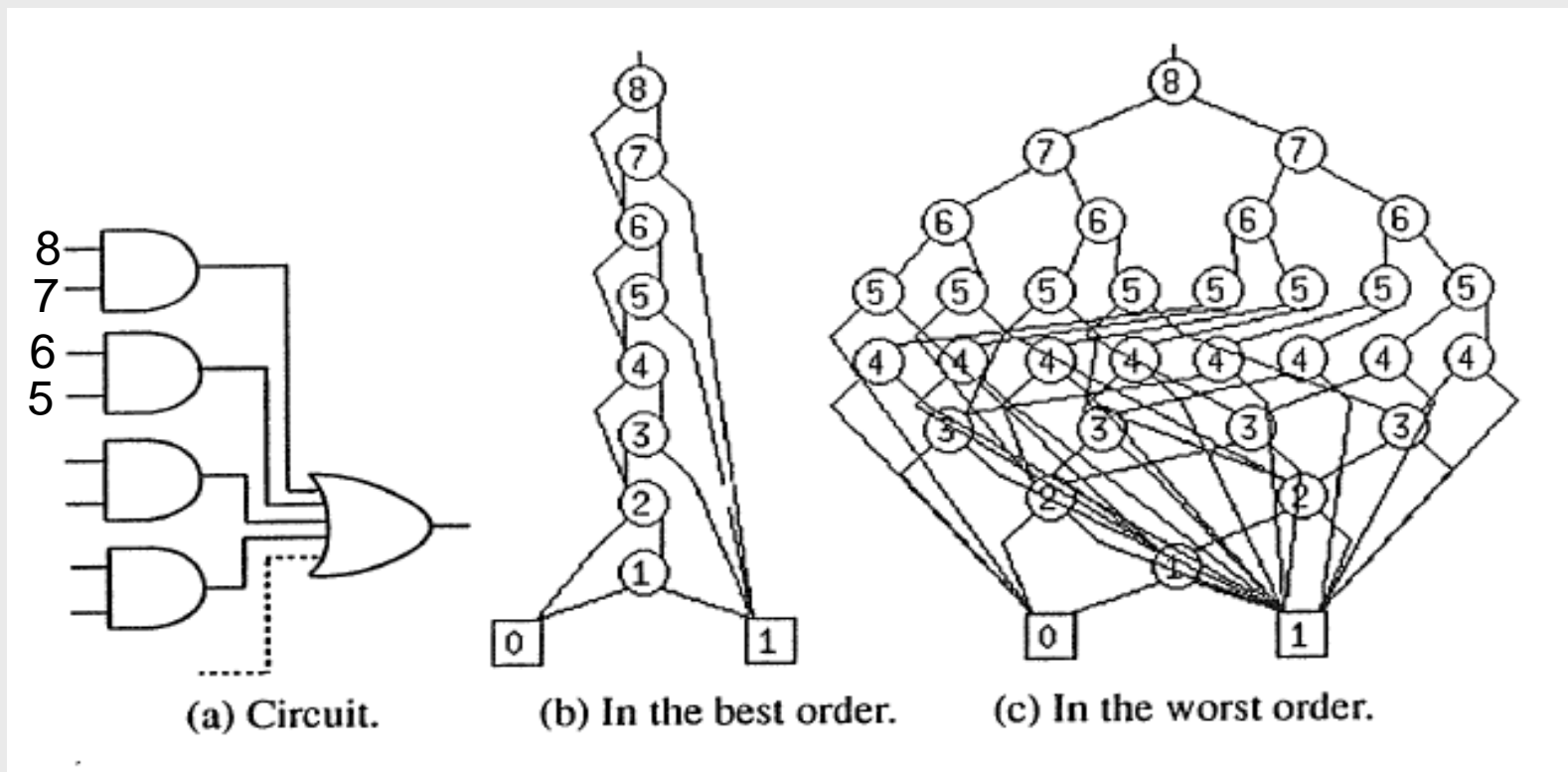
Optimization (by ordering of nodes): BDDs for a 2-level AND-OR circuit




$(2n)$ nodes

$(2 \cdot 2^n - 2)$ nodes

BDDs and Complexity

 

(a) In the best order.

 


(b) In the worst order.

BDDs for an 8-bit data selector

BDDs and Complexity


Elementary BDDs

D Flip-Flop

 

$$q = cD \vee \bar{c}q'$$


RS Flip-Flop

 


$$q = c(S \vee q' \bar{R}) \vee \bar{c}q'$$

$$SR = 0$$

U - unknown value

 

JK Flip-Flop

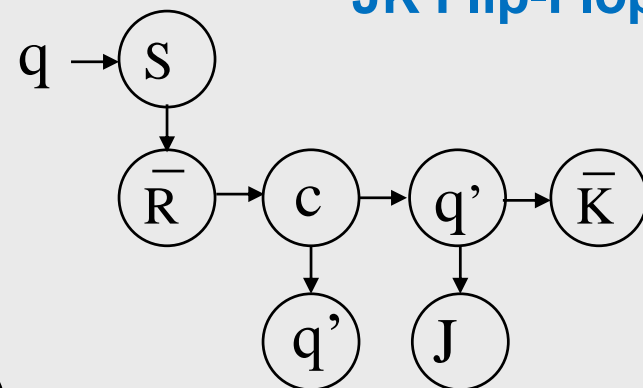



BDD optimization:

We may start synthesis:

- from the **most important** variable, or
- from the **most repeated** variable

Test Generation with SSBDDs

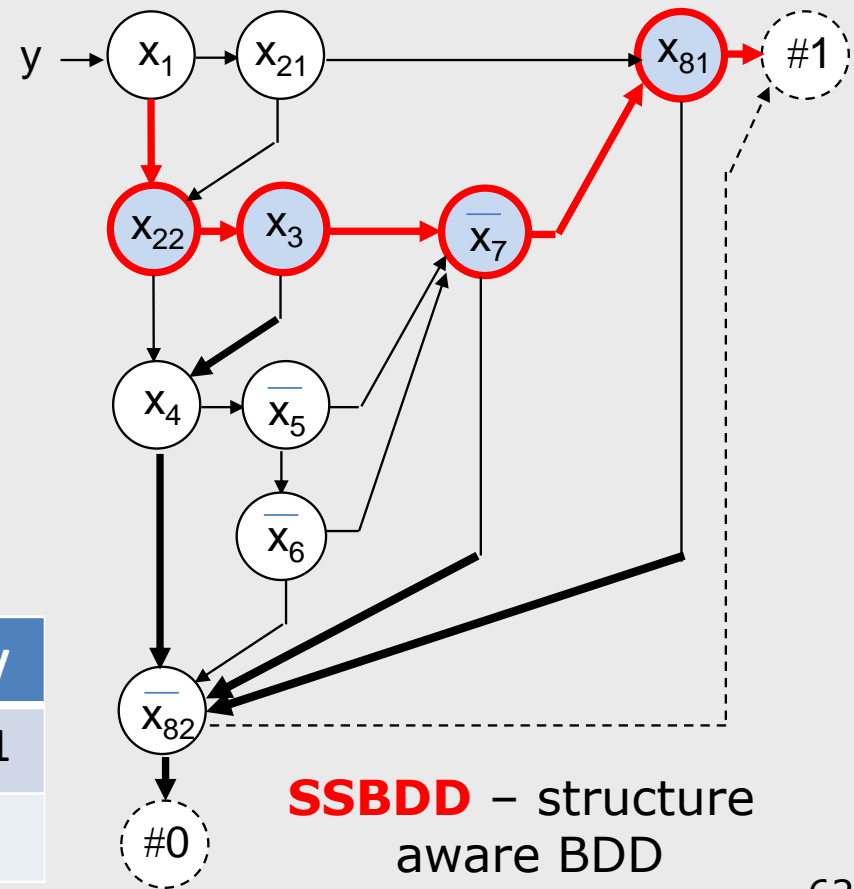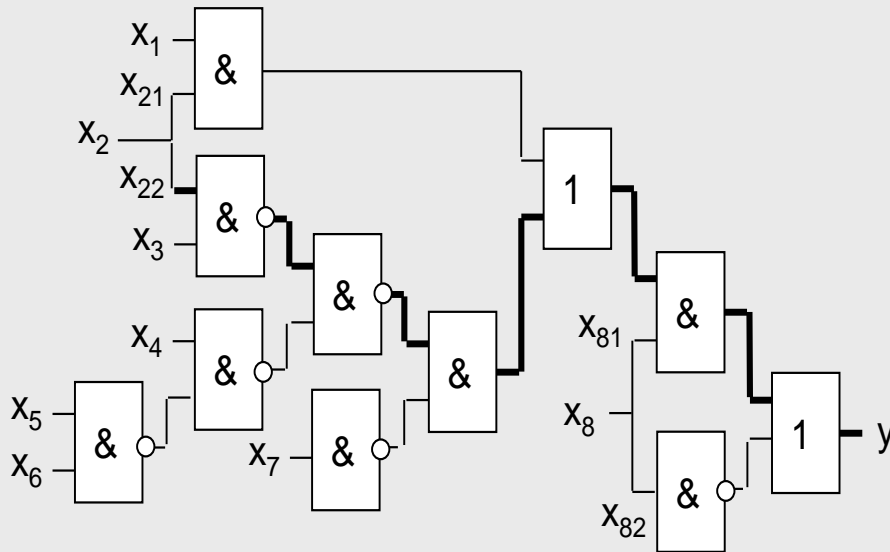
$$y = f(X) = (x_1 x_{21} \vee (x_{22} x_3 \vee x_4 (\overline{x_5} \vee \overline{x_6})) \overline{x_7}) x_{81} \vee \overline{x_{82}}$$






X	x ₁	x ₂	x ₃	x ₄	x ₅	x ₆	x ₇	x ₈	y
X ^t	0	1	1	0	-	-	0	1	1
Tested: x ₂₂ ≡ 0, x ₃ ≡ 0, x ₇ ≡ 1, x ₈₁ ≡ 0									

BDDs for Logic Gates

Elementary BDDs:

 

How about a circuit?

 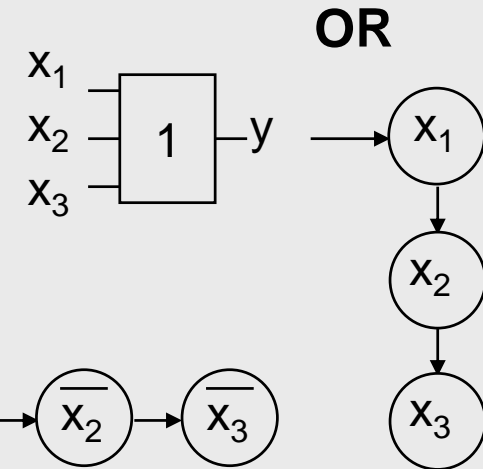 


SSBDD synthesis:

SSBDDs for a given circuit are built by **superposition** of BDDs for gates

Synthesis of BDD for a Circuit

Given circuit:

 


Structurally Synthesized BDD:

Compare to


Superposition of Boolean functions:

$$y = a \& b = (x_1 \vee x_{21})(\overline{x_{22}} \vee x_3)$$

Superposition of BDDs:

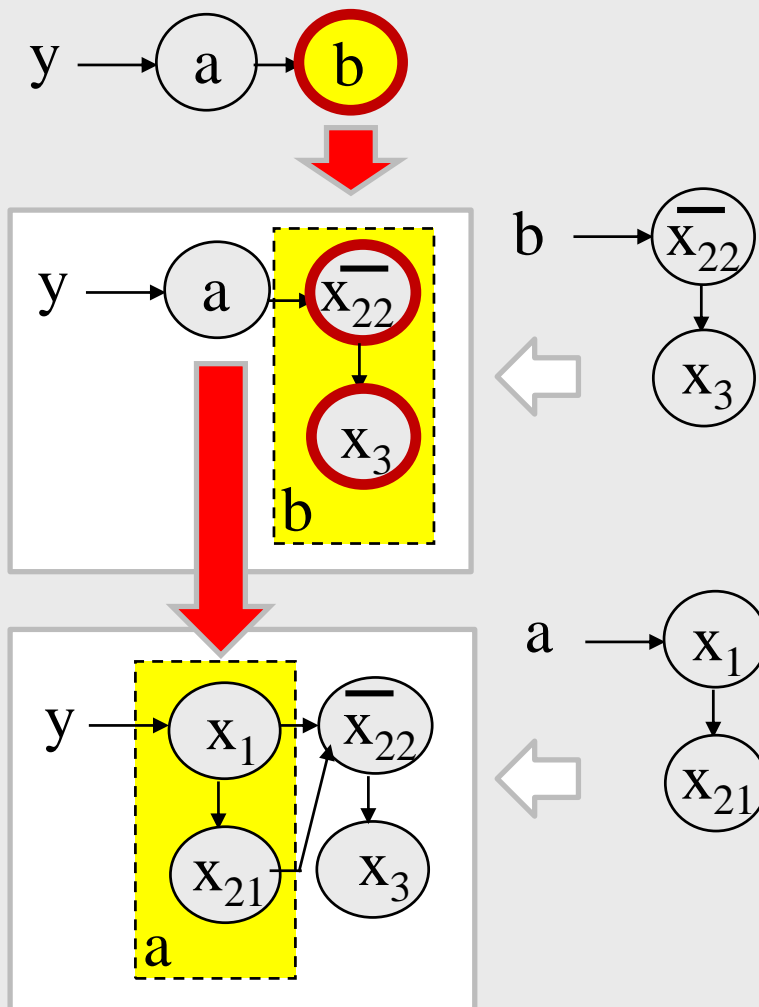


Transformation of SSBDDs to FBDDs

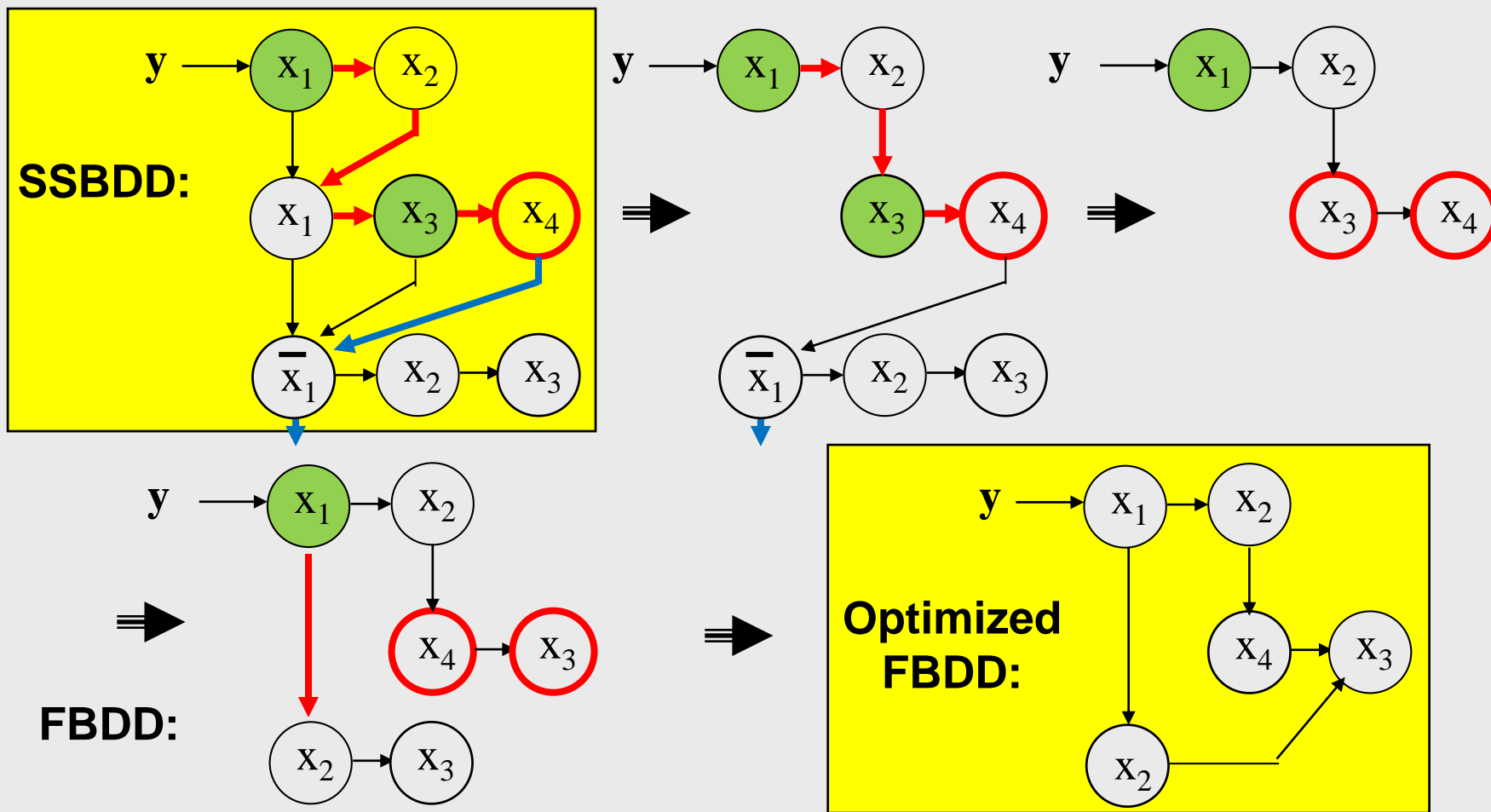

Test Generation with SSBDDs and FBDDs


Test generation for: $x_{11} \equiv 0$

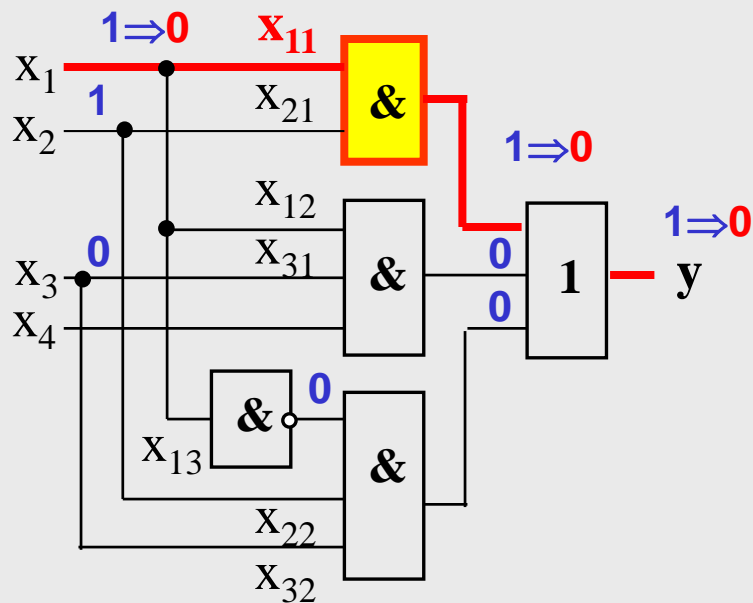


Test pattern:

x_1	x_2	x_3	x_4	y
1	1	0	-	$1 \Rightarrow 0$


Structural BDD:

 


Functional BDD:

 


Complexity: Hierarchical Test Generation

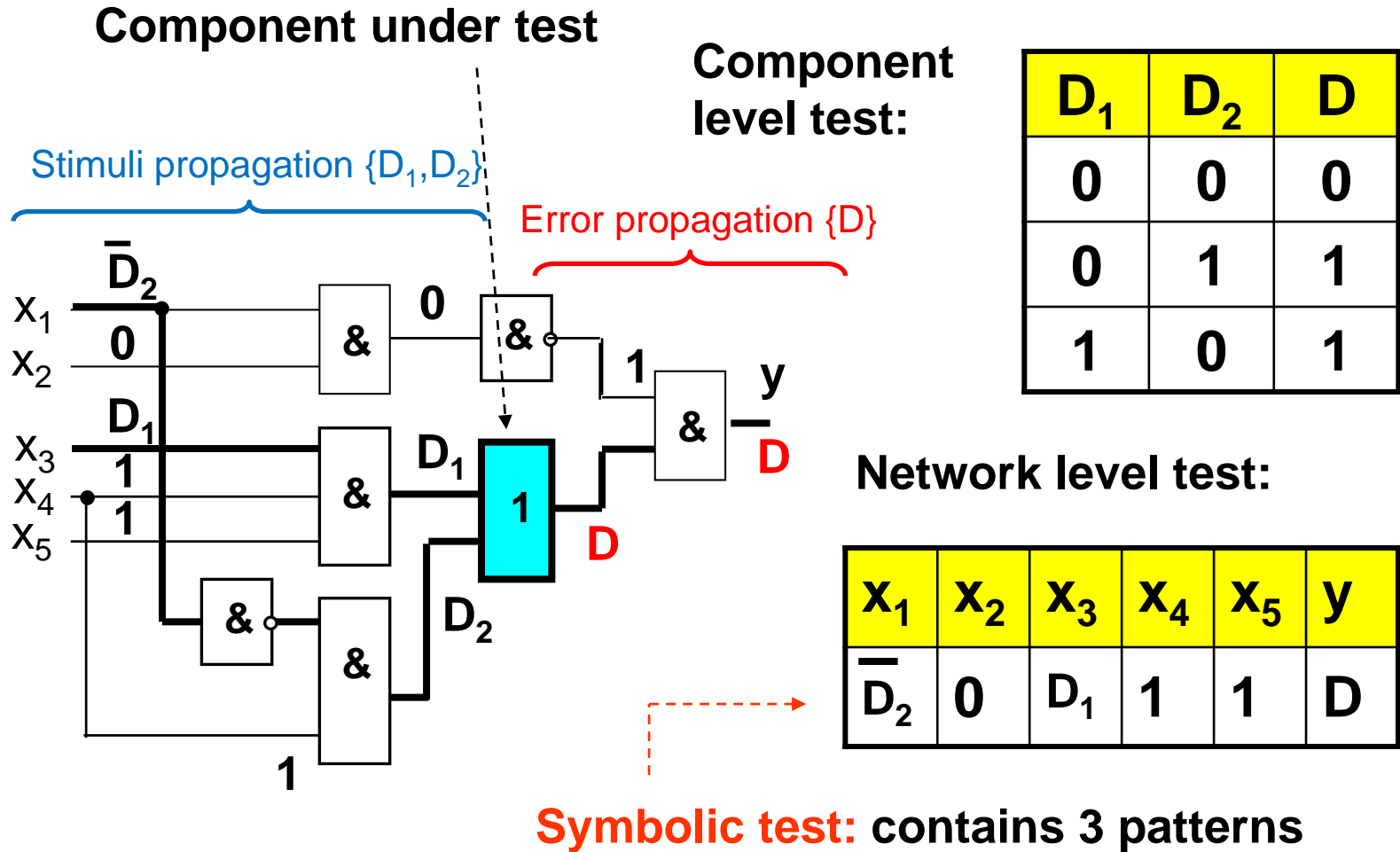

Generalization of BDDs

 

The basic idea of simulation with BDDs:

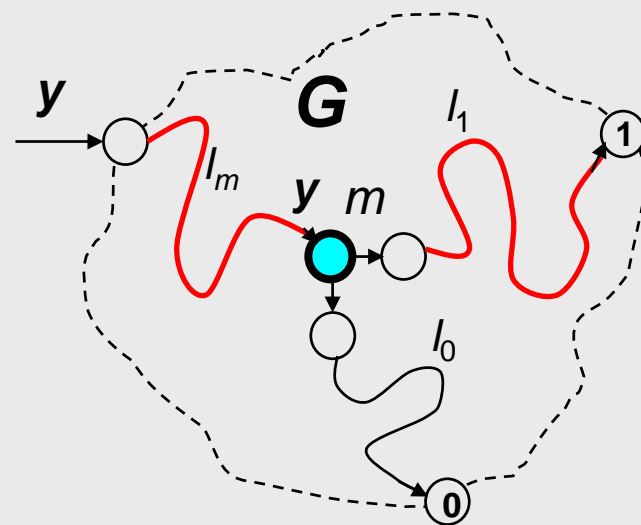


Boolean functions represent the **low** 2-valued logic **level**

Is it possible to use the topological **graph-based modeling** to generalize to **higher** functional **levels** like RTL

Generalization of BDDs


Binary DD

 2 terminal nodes and
2 edges from each node



General case of DD

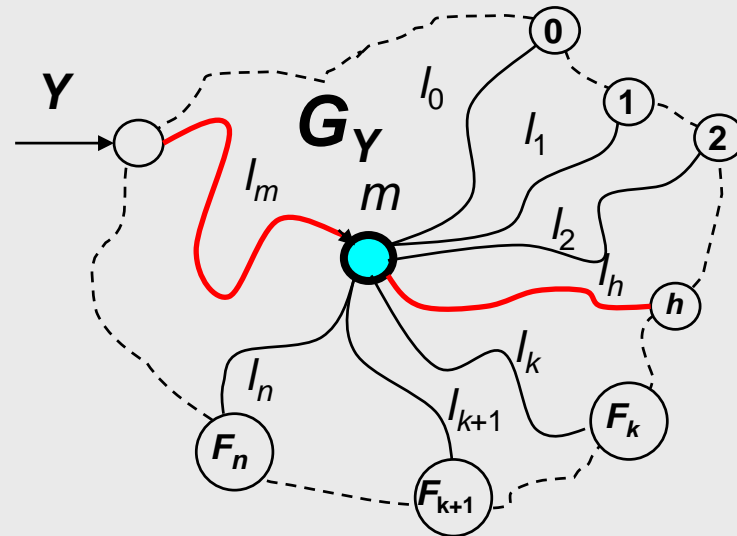$n \geq 2$ terminal nodes and
 $n \geq 2$ edges from each node





Novelty: Boolean methods can be generalized in a straightforward way to higher functional levels

HLDD - High-Level Decision Diagrams

RTL-statement:

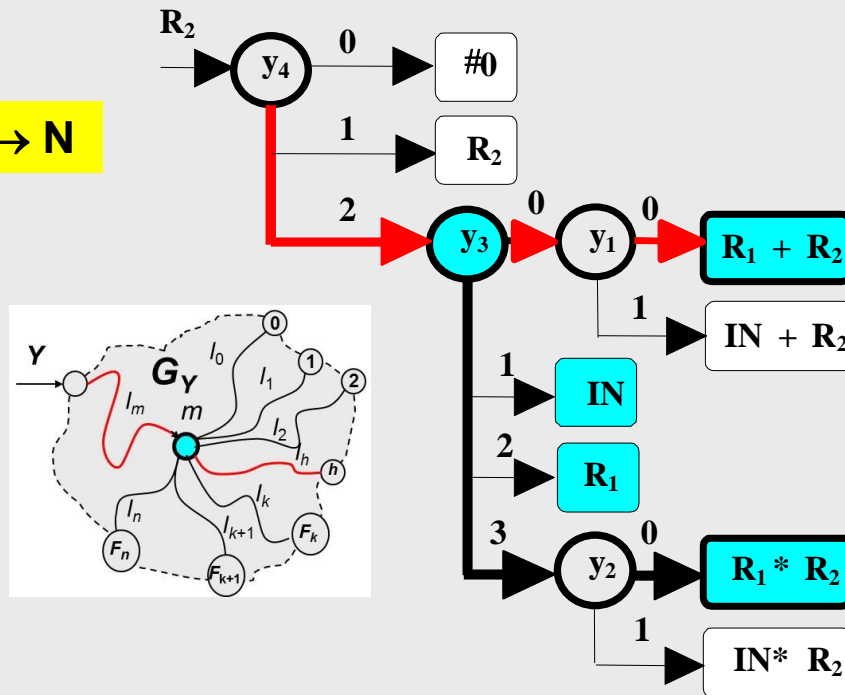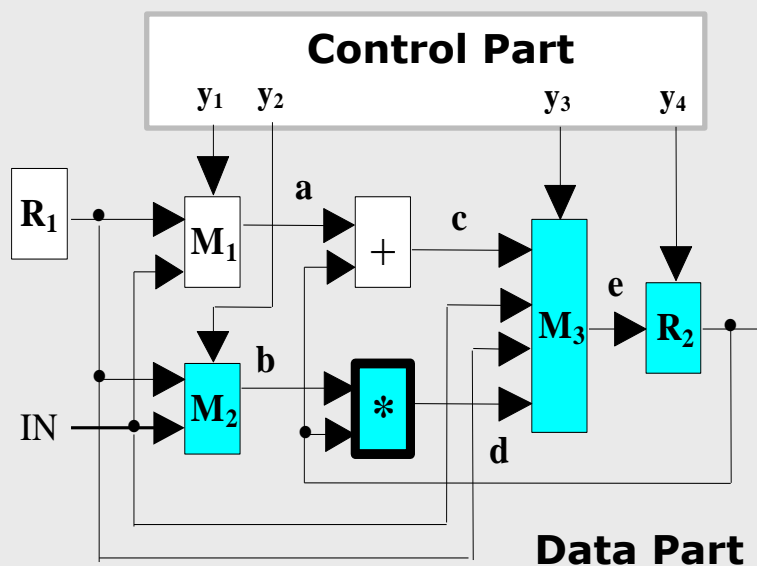K: (If T,C) $R_D \leftarrow F(R_{S1}, R_{S2}, \dots, R_{Sm}), \rightarrow N$



Control part:
Internal nodes in the **HLDD**
Data Part:
Terminal nodes

Interpretation of HLDDs – Nodes and Faults

RTL-statement:

K: (If T,C) $R_D \leftarrow F(R_{S1}, R_{S2}, \dots, R_{Sm}), \rightarrow N$

Nonterminal nodes



RTL-statement faults:

label,
timing condition,
logical condition,
register decoding,
operation decoding,
control faults

Terminal nodes

RTL-statement faults:

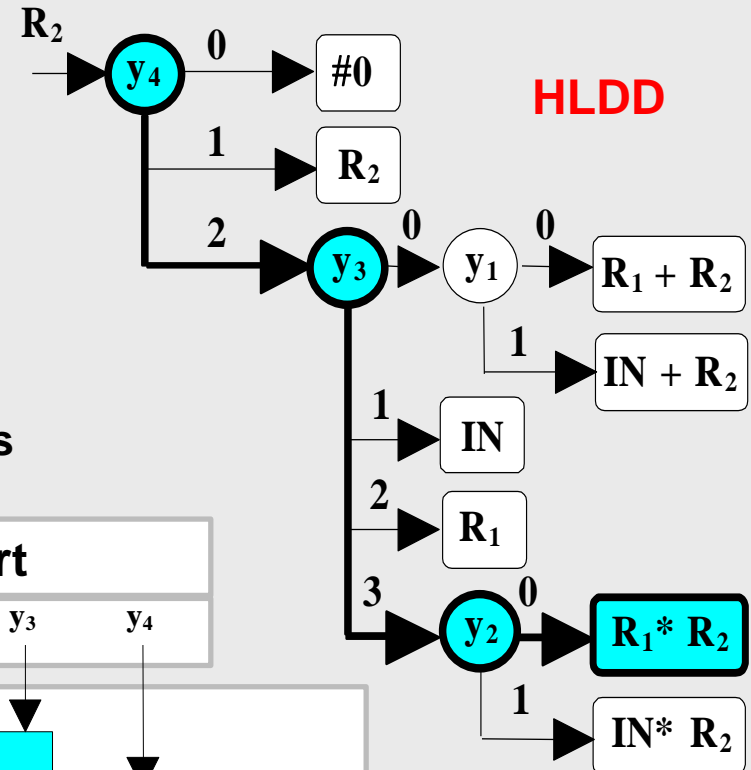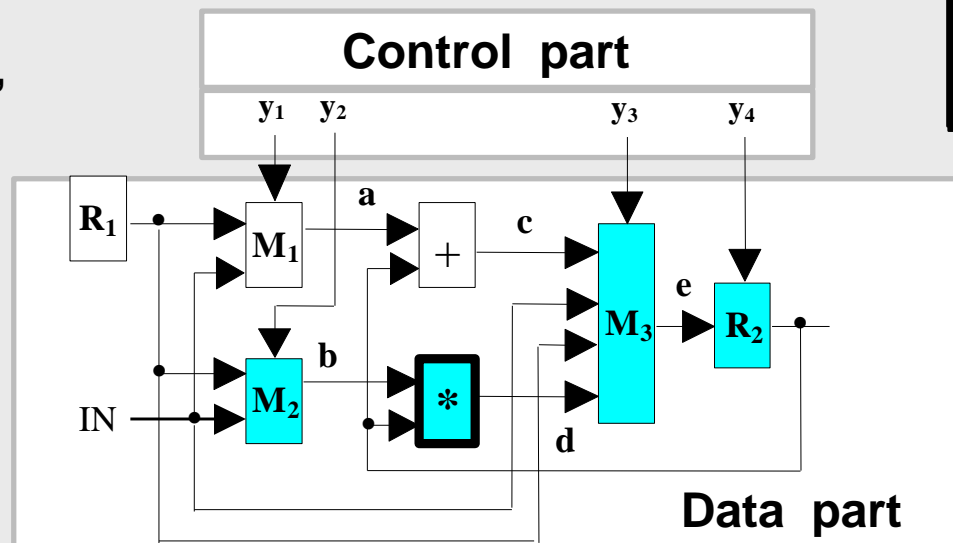data storage,
data transfer,
data manipulation faults




High Level Test Generation for Systems

RTL test generation with DDs: Scanning test


Single path activation in a single DD
Data function $R_1 * R_2$ is tested

Data path

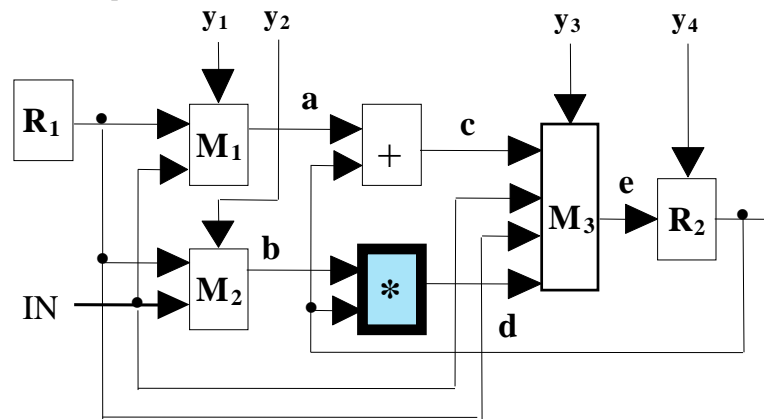

Test program: **Control:** $y_1 y_2 y_3 y_4 = - 032$
Data: *For all specified pairs of (R_1, R_2)*

Decision Diagram

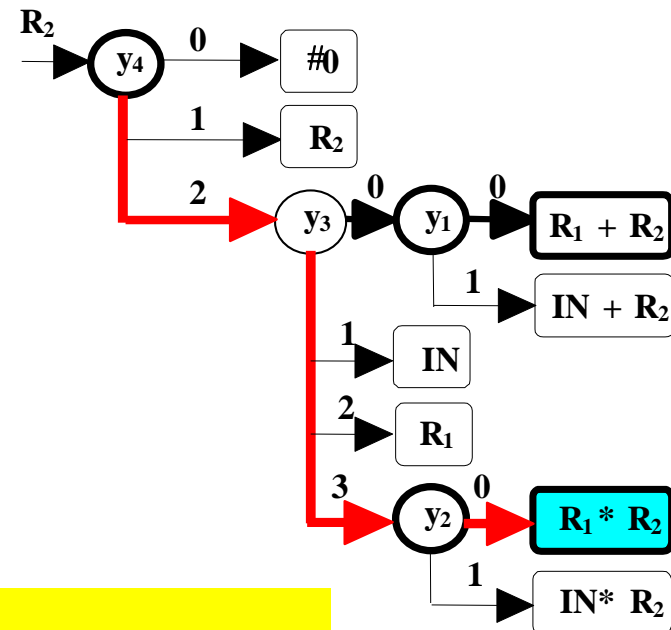

Test Program Synthesis for Digital Systems

High-level test generation with DDs: **Scanning test program**

Test program:

For $j=1,n$

Begin


Load $R_1 = IN(j_1)$

Load $R_2 = IN(j_2)$

$y_1 y_2 y_3 y_4 = 0032$:

Read **R_2**

End

 


Test data

Test results

Test template:

Control: $y_1 y_2 y_3 y_4 = 0032$

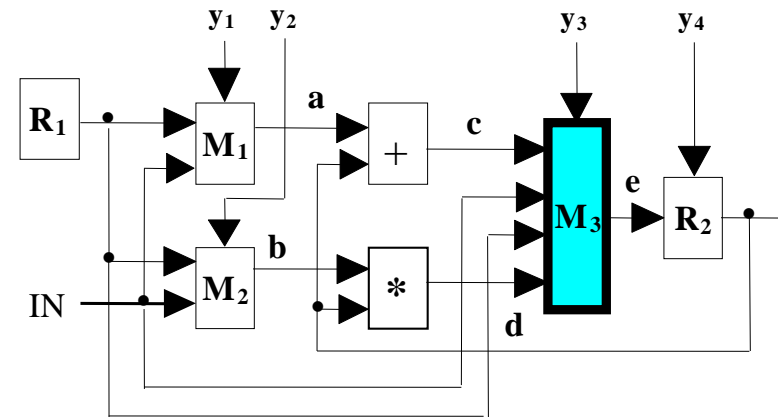Data: For all specified pairs of (R_1, R_2)





Test Generation with HLDDs for Systems

High-level test generation with DDs: **Conformity test**

Multiple paths activation in a single DD
Control function y_3 is tested

Decision Diagram

Data path

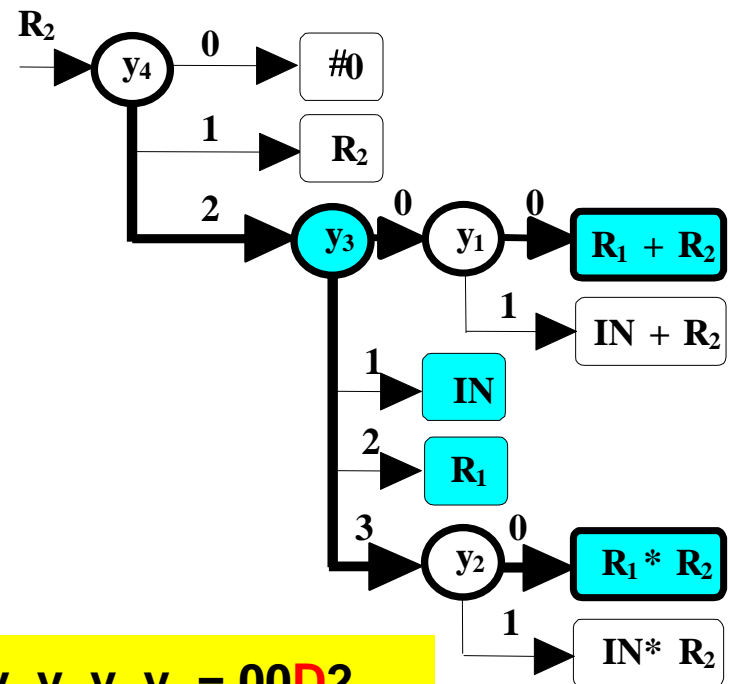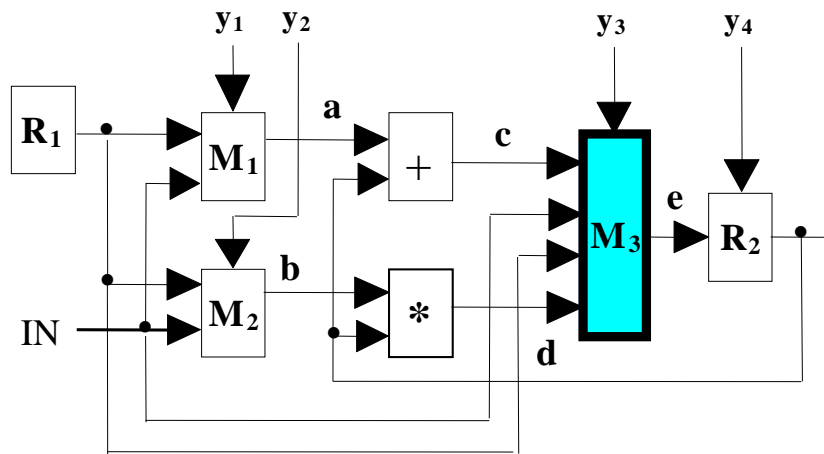

Test program: **Control:** For $D = 0,1,2,3$: $y_1 y_2 y_3 y_4 = 00D2$
Data: Solution of $R_1 + R_2 \neq IN \neq R_1 \neq R_1 * R_2$

Test Generation with HLDDs for Systems

High-level test generation with DDs: **Conformity test**

Test program:

For $D = 0,1,2,3$

Begin

Load $R_1 = IN_1$

Load $R_2 = IN_2$


Apply

$IN = IN_3$

$y_1 y_2 y_3 y_4 = 00D2$

Read R_2


End

 

Test template:

Control: *For* $D = 0,1,2,3$: $y_1 y_2 y_3 y_4 = 00D2$

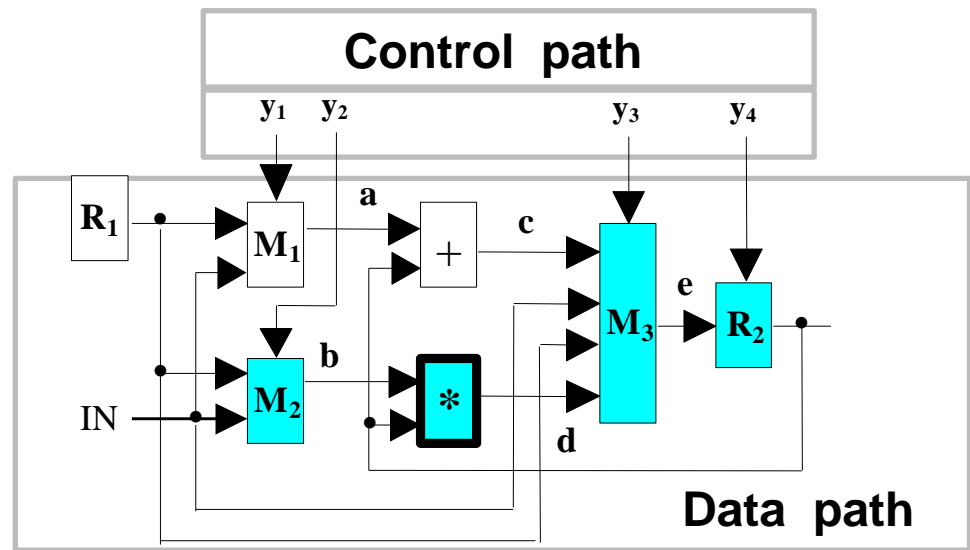Data: *Solution of* $R_1 + R_2 \neq IN \neq R_1 \neq R_1 * R_2$




Microprocessor Modeling with HLDDs

HLDD-model of a microprocessor:


Instruction set:

I_1 :	MVI A,M	$A \leftarrow IN$
I_2 :	MOV R,A	$R \leftarrow A$
I_3 :	MOV M,R	$OUT \leftarrow R$
I_4 :	MOV M,A	$OUT \leftarrow A$
I_5 :	MOV R,M	$R \leftarrow IN$
I_6 :	ADD R	$A \leftarrow A + R$
I_7 :	ORA R	$A \leftarrow A \vee R$
I_8 :	ANA R	$A \leftarrow A \wedge R$
I_9 :	SUB R	$R \leftarrow R - 1$
I_{10} :	MOV C,R	$C \leftarrow R$
I_{11} :	CMA R,C	$R \leftarrow C$
I_{12} :	JMP PC, C	$PC = IN$ IF $C=0$
	For all I_k	$PC = PC + 1$

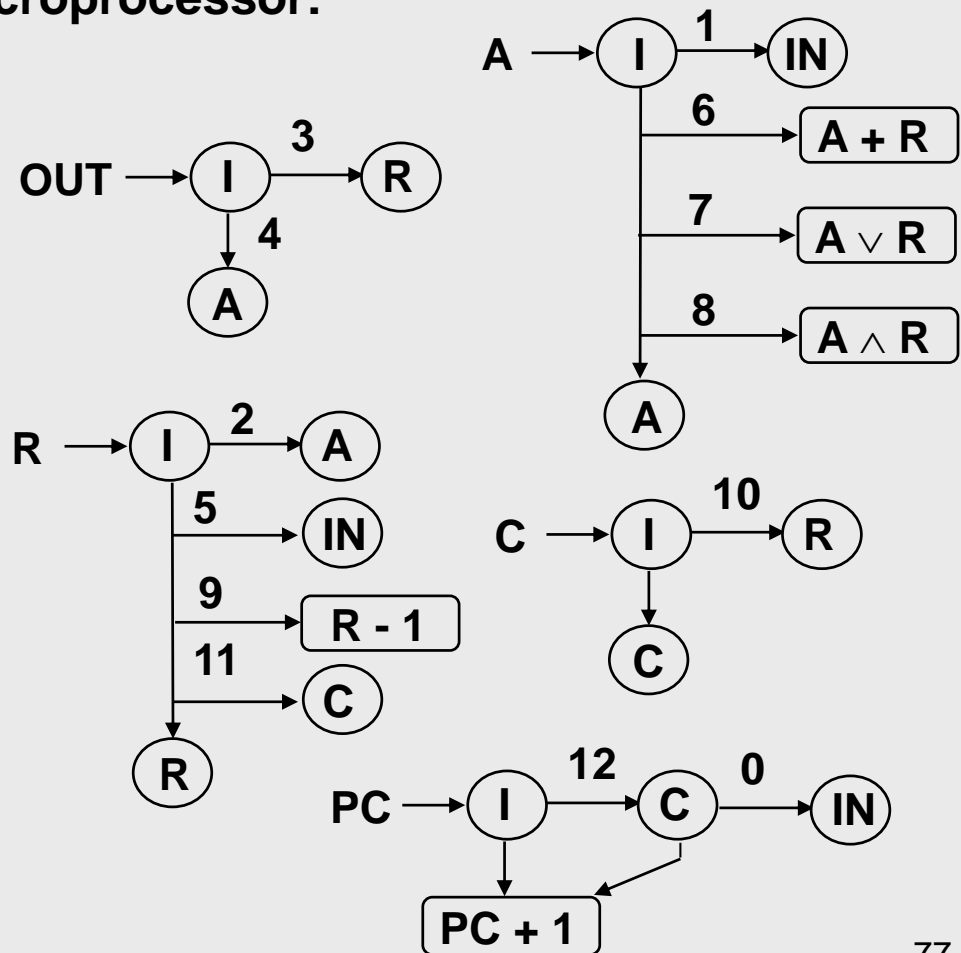



Microprocessor Modeling with HLDDs

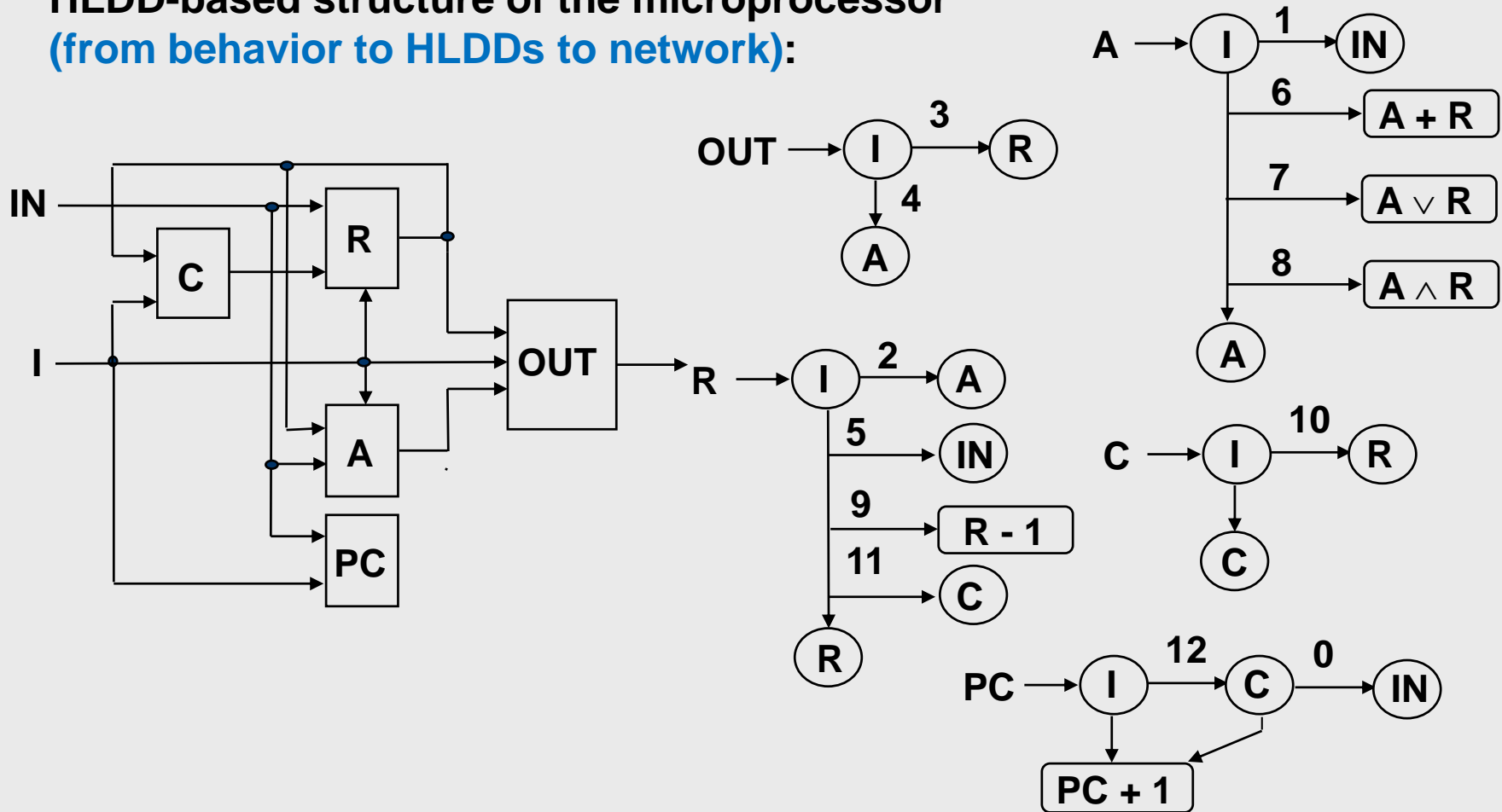HLDD-based structure of the microprocessor
(from behavior to HLDDs to network):





Test Generation for Microprocessors

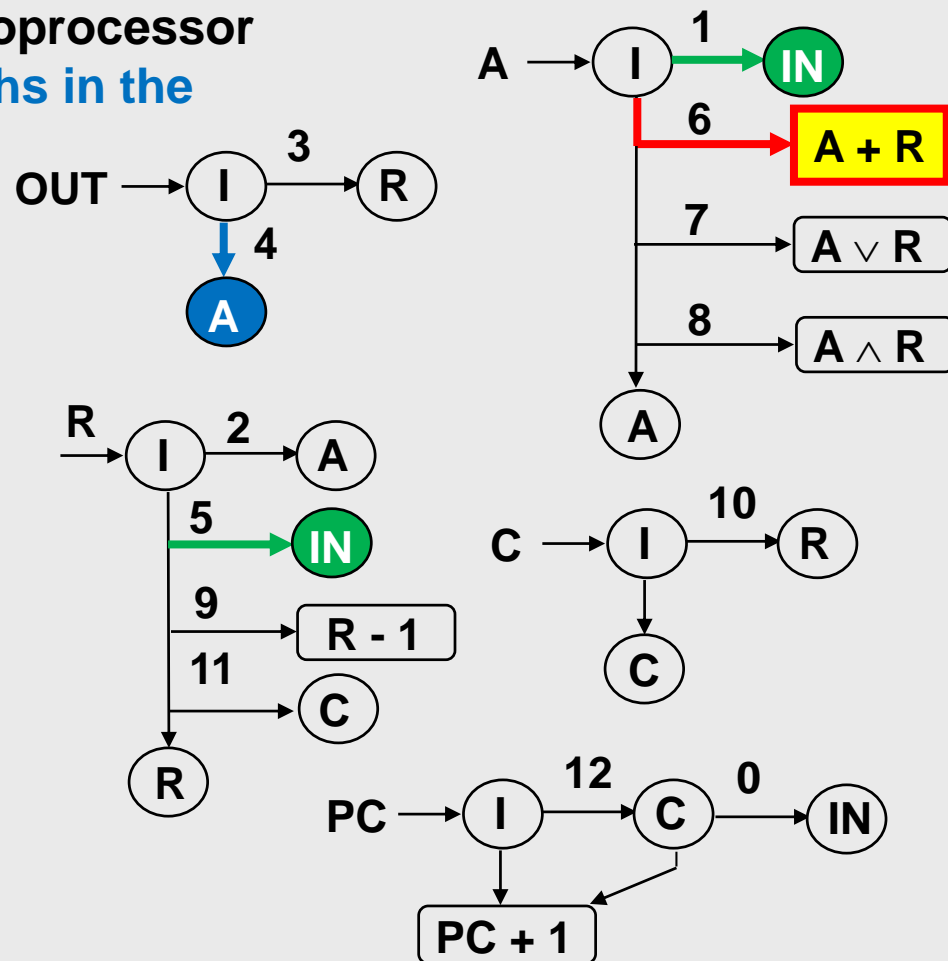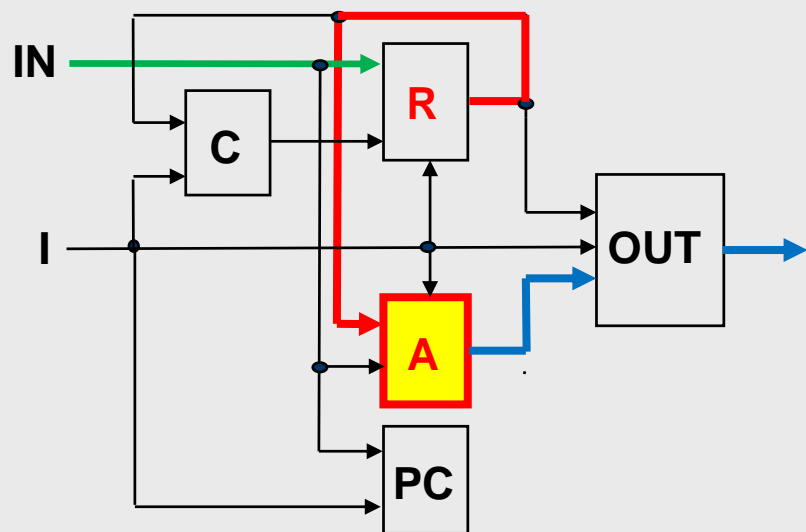HLDD-based structure of the microprocessor
(propagation of faults through paths in the network):



Test Generation for Microprocessors

Scanning test program:

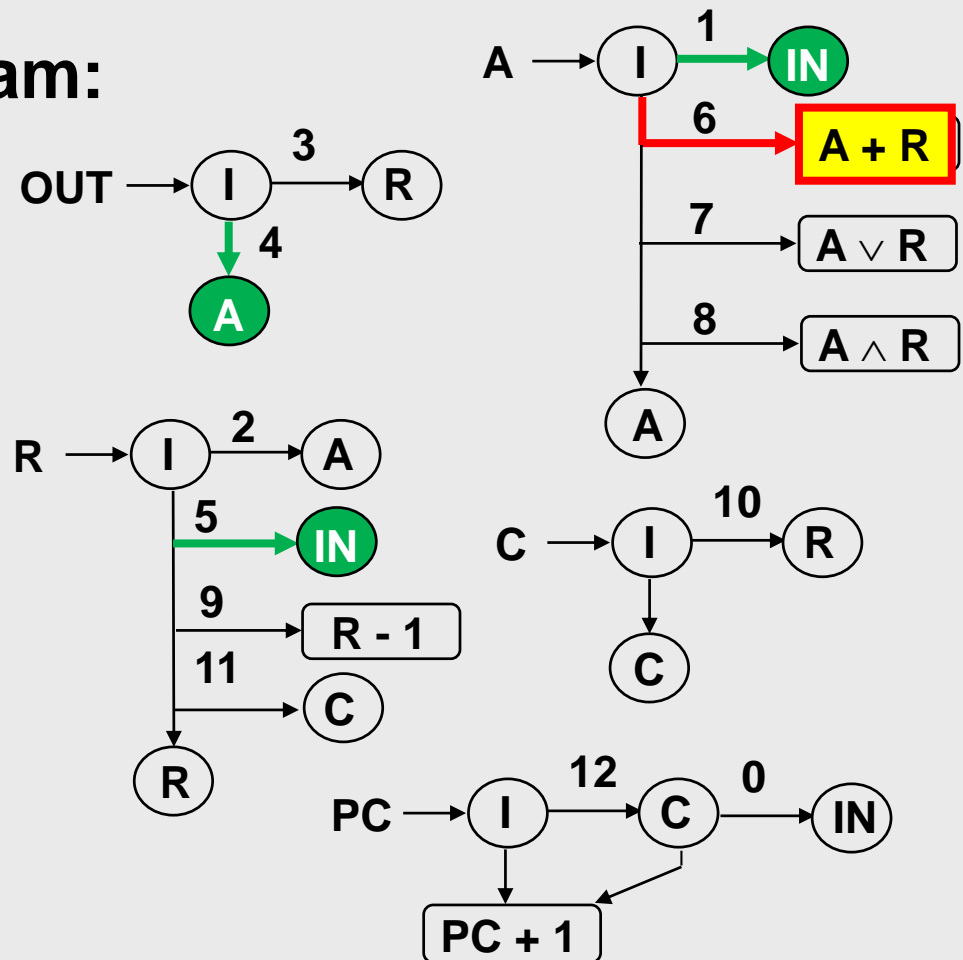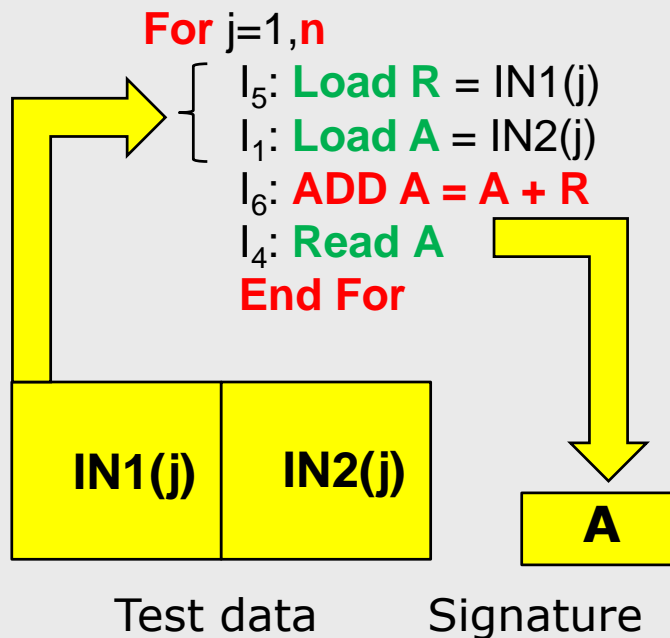

Test Generation for Microprocessors

Conformity test program:

For $D=1,n$


I_5 : Load $R = IN(1)$

I_1 : Load $A = IN(2)$


I_D : D

I_4 : Read A


End For

 

Test data

 

Signature

 

Algorithm:

Control: For $D = 0,1,\dots,12$: I_D

Data: Solution of $IN \neq (A + R) \neq (A \vee R) \neq (A \wedge R)$

Added effects:

- 1) Special type of test compaction:
 - DD model
 - Test program template
 - Automated TPG
- 2) When testing all the functions of A with the same LOAD and READ conditions, the probability of **fault masking** will reduce
- 3) The faults of type “**added erroneous actions**” are as well easily tested

Modeling of Microprocessors with HLDDs

Instruction set

OP	B	Mnemonic	Semantic	RT level operations
0	0	LDA A1, A	READ memory	$R(A1) = M(A), PC = PC + 2$
	1	STA A2, A	WRITE memory	$M(A) = R(A2), PC = PC + 2$
1	0	MOV A1,A2	Transfer	$R(A1) = R(A2), PC = PC + 1$
	1	CMA A1,A2	Complement	$R(A1) = \neg R(A2), PC = PC + 1$
2	0	ADD A1,A2	Addition	$R(A1) = R(A1) + R(A2), PC = PC + 1$
	1	SUB A1,A2	Subtraction	$R(A1) = R(A1) - R(A2), PC = PC + 1$
3	0	JMP A	Jump	$PC = A$
	1	BRA A	Conditional jump (Branch instruction)	IF C=1, THEN $PC = A$, ELSE $PC = PC + 2$

Instruction code:


ADD A1 A2

OP=2. B=0. A1=3. A2=2


$R(A1) = R(A1) + R(A2)$

$R_3 = R_3 + R_2$

$PC = PC + 1$

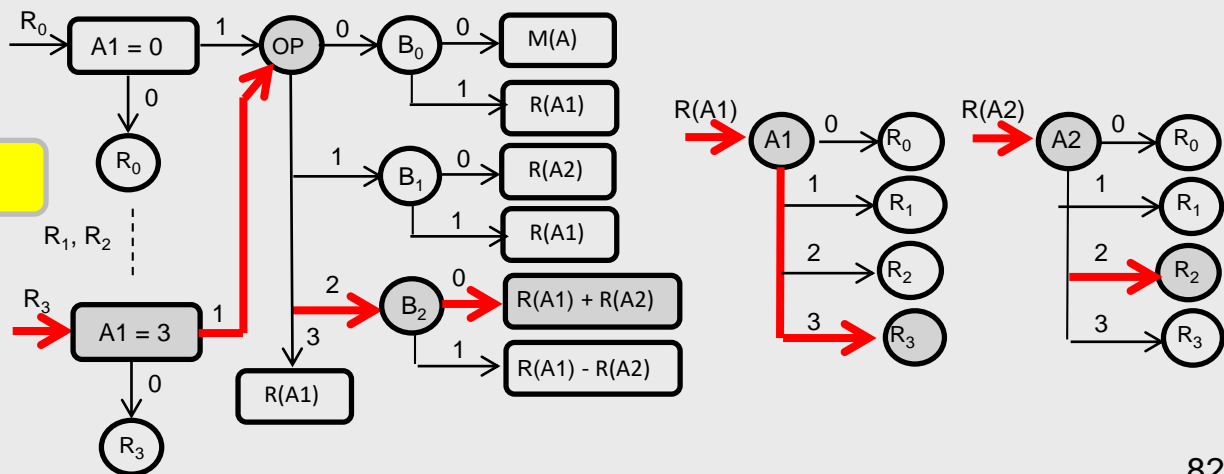


HLDDs for MP InstrSet

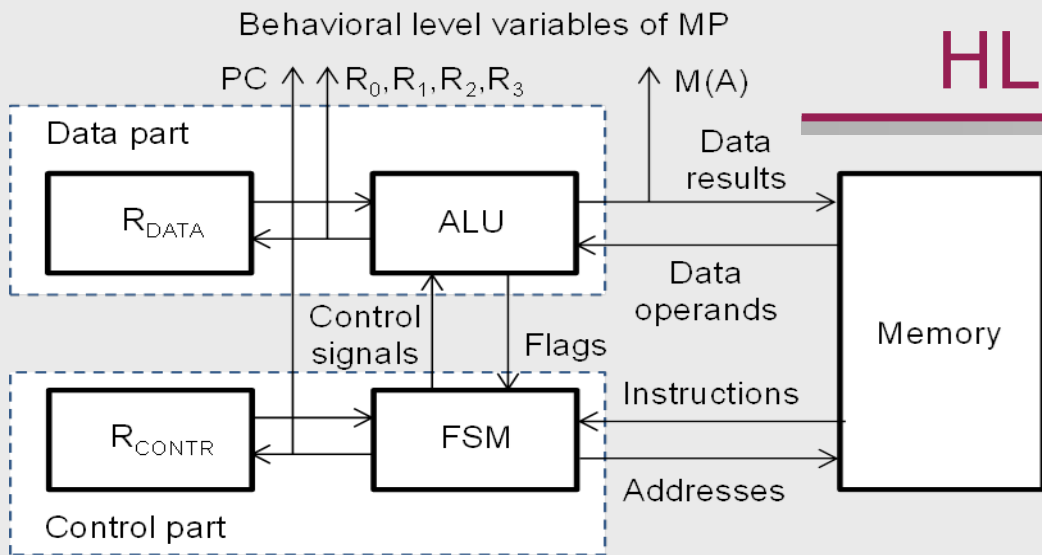


Instruction code:
 ADD A1 A2
 OP=2. B=0. A1=3. A2=2

$R_3 = R_3 + R_2$
 $PC = PC + 1$


Registers and ALU

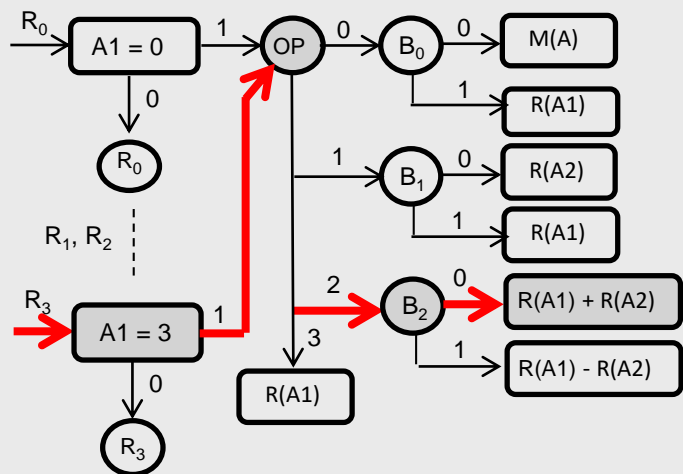


Register Decoding

 

Program Counter

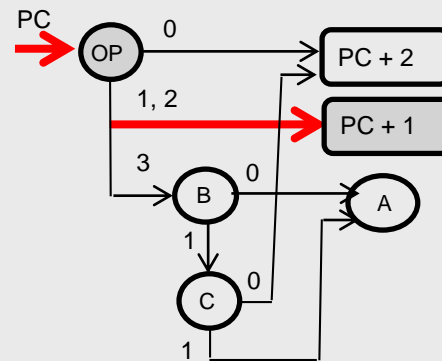


Memory Access

 


Modeling of Microprocessors with HLDDs

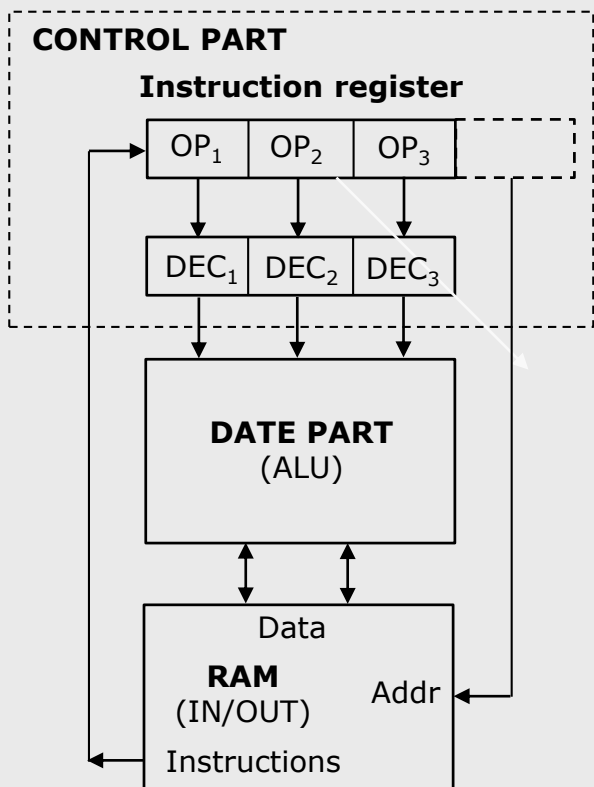Microprocessor instruction set architecture



HLDD

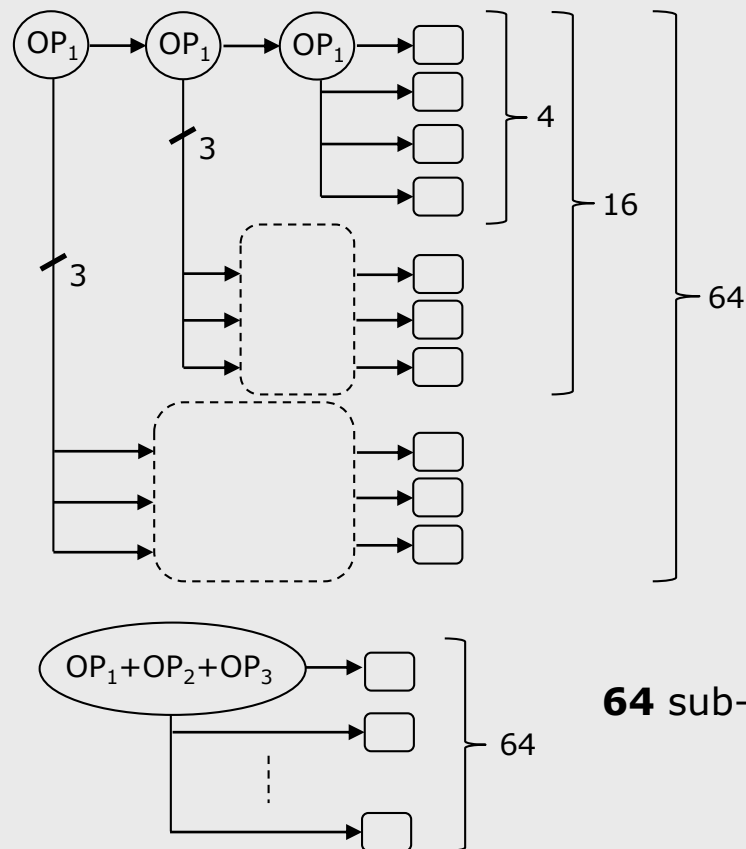12 control sub-tests
64 data part sub-tests



64 sub-tests

Fault Coverage Table and FC Measure

Functional fault model:

 $\forall j [f_j \neq \text{ZERO}]$
 $\forall i, j: \forall k [(f_{i,k} < f_{j,k})]$

Distinguished Operations f_i		Distinguished Operations f_j								
		f_0	f_1	f_2	f_3	f_4	f_5	f_6	f_7	f_8
		MOV	ADD	SUB	CMP	AND	OR	XOR	NOT	NOP
f_0	MOV	00000000	00110000	00010000	00100000	00000000	00100000	00100000	00110000	00000000
f_1	ADD	01001000	00000000	00001000	01001000	01001000	01001000	00000000	00000000	00000000
f_2	SUB	11000110	10100110	00000000	11100000	11000000	11100110	00100110	00100000	00000000
f_3	CMP	00000111	00010111	00010001	00000000	00000000	00000111	00000111	00010000	00000000
f_4	AND	00000111	00110111	00010001	00100000	00000000	00100111	00100111	00110000	00000000
f_5	OR	00000000	00010000	00010000	00000000	00000000	00100111	00100111	00110000	00000000
f_6	XOR	1100					110010			
f_7	NOT	1100					110010			
f_8	NOP	11001111	10110111	00011001	111010					

$$f_{i,k} < f_{j,k}$$

Fault coverage measure:

Percentage of 1-s
in the fault coverage table

1 – means that
a constraint is satisfied
by at least one pair of data
operands


Parwan Microprocessor : Instruction Set

	OP	
LDA	0	AC=M
AND	1	AC=AC^M
ADD	2	AC=AC+M
SUB	3	AC=AC-M
JMP	4	PC=A
STA	5	M=AC
JSR	6	PC=A Jump to subroutine


	OP	I	P	
CLA	7	0	1	AC=0
CMA	7	0	2	AC=¬AC
CMC	7	0	4	C=¬C
ASL	7	0	8	AC=2AC
ASR	7	0	9	AC=AC/2
BRA_N	7	1	0	If negative
BRA_Z	7	1	2	If zero
BRA_C	7	1	4	If carry
BRA_V	7	1	8	If overflow

Parwan: HLDD Model


ALU Data Path

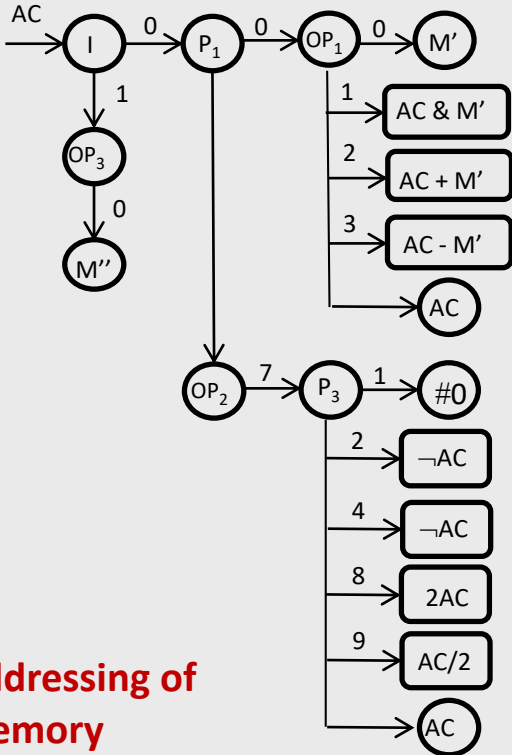


Addressing of memory

 


Output behaviour

 


ALU Flags

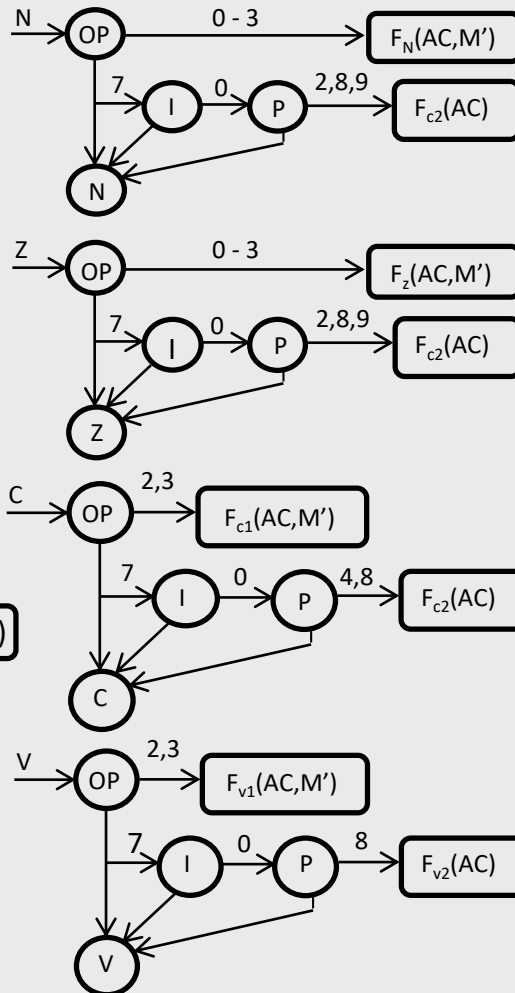


Instruction addressing

 



Next memory page calculation

 


Next PC offset calculation

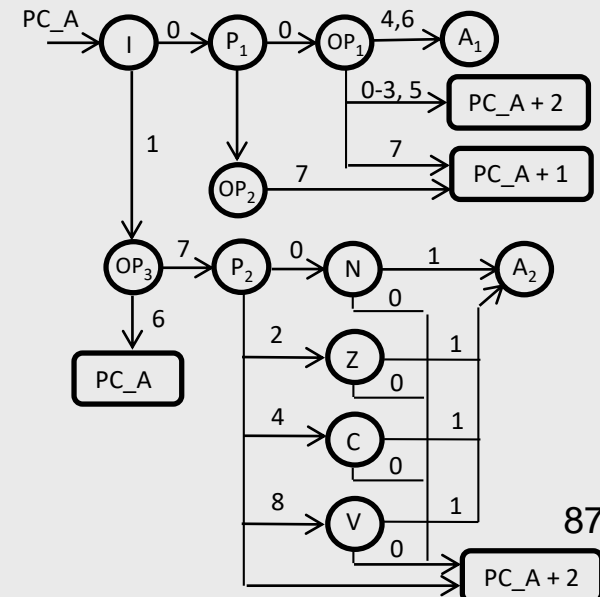


Fault Simulation: With BDDs

  

Problems:

 



The critical path is not continuous

 

The critical path breaks on the fan-out

Fault Simulation with BDDs
 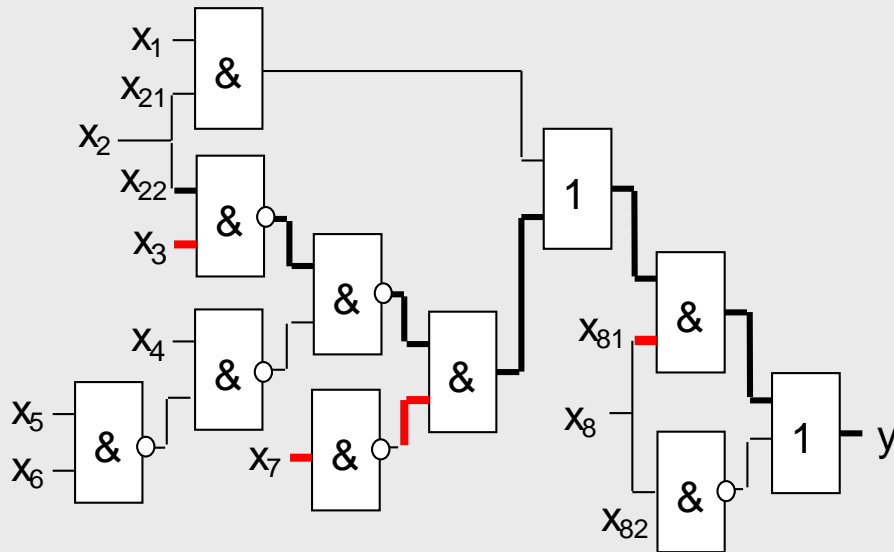
$$y = f(X) = (x_1 x_{21} \vee (x_{22} x_3 \vee x_4 (\overline{x_5} \vee \overline{x_6})) \overline{x_7}) x_{81} \vee \overline{x_{82}}$$



X	x ₁	x ₂	x ₃	x ₄	x ₅	x ₆	x ₇	x ₈	y
X ^t	0	1	1	0	-	-	0	1	1

Tested: $x_{22} \equiv 0, x_3 \equiv 0, x_7 \equiv 1, x_{81} \equiv 0$

Fault Diagnosis with BDDs



Sequential fault diagnosis by Signal Pinpointing

Property 2:

If a test vector X activates in SSBDD a **0**-path (1-path) which traverses a subset of nodes M , then only **0**-nodes (**1**-nodes) have to be considered as fault candidates

Fault diagnosis and fault simulation can be speed-up by using Property 2

Fault diagnosis / Fault simulation:

 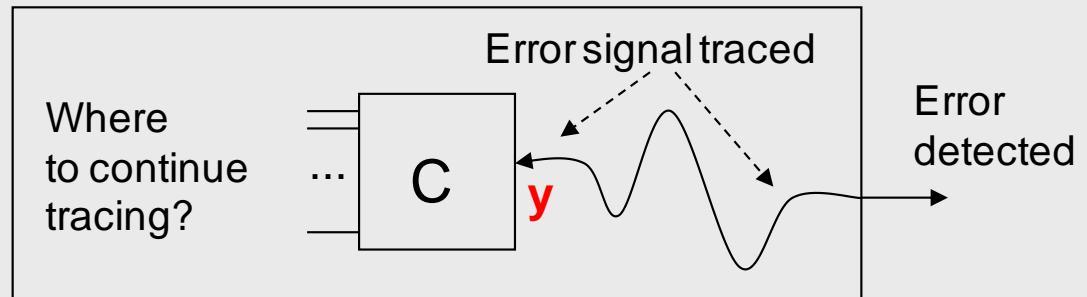

Speeding-up simulation:

$$M = \{1, 2, 3, 4, 6, 7\}$$

$$M^* = \{1, 6, 7\} \text{ – by Property 2}$$

$$M^{**} = \{6, 7\} \text{ – by Property 1}$$

Only **6** and **7** have to be considered