

Overview: Testability Evaluation

Outline




- **Quality Policy of Electronic Design**
- **Tradeoffs of Design for Testability**
- **Testability measures**
 - Heuristic measures
 - Probabilistic measures
- **Calculation of testability**
 - Parker - Mc Cluskey method
 - Cutting method
 - Conditional probabilities based method

Quality Policy

Chips from
manufactory

Yield

   
For example, yield is 60%. Other chips are faulty



Defect level means:

How many faulty chips from
40% escape?

Introduction: The Problem is Money?

 


How to succeed?

Try too hard!

How to fail?

*Try too hard!
(From American Wisdom)*

**Test
coverage
function**

 


Conclusion:

**“The problem of testing
can only be contained
not solved”**

T. Williams

Design for Testability

The problem is - **QUALITY**:

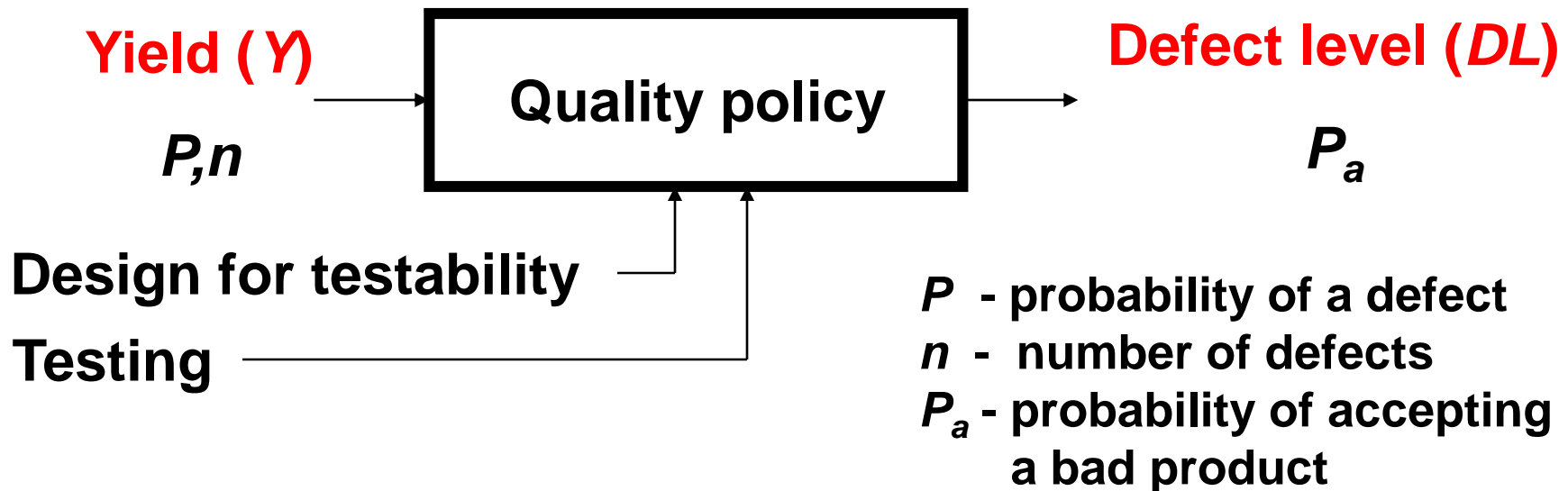

$$Y = (1 - P)^n \quad \text{- probability of producing a good product}$$

Design for Testability

The problem is - **QUALITY**:

Yield (Y)

P, n




Defect level (DL)

P_a

$$DL = \frac{P_a}{(1-P)^n + P_a} = 1 - (1-P)^{n-m} = 1 - Y^{\frac{n-m}{n}} = 1 - Y^{(1-\frac{m}{n})} = 1 - Y^{(1-T)}$$

 - n - number of defects
- m - number of faults tested
- P - probability of a defect
- P_a - probability of accepting a bad product
- T - test coverage





$$P_a = (1-P)^m - (1-P)^n$$

$$Y = (1-P)^n$$

Design for Testability

The problem is - Money:

$$DL = 1 - Y^{(1-T)}$$

  

Goal: $DL \downarrow \leftarrow T \uparrow \leftarrow \text{Testability} \uparrow$

Paradox: $\text{Testability} \uparrow \rightarrow DL \uparrow (Y \downarrow)$

Design for Testability


Technical tradeoff:

Goal: $DL \downarrow \leftarrow T \uparrow \leftarrow \text{Testability} \uparrow$
Paradox: $\text{Testability} \uparrow \rightarrow DL \uparrow (Y \downarrow)$

DFT: Resynthesis or adding extra hardware

Economic tradeoff:
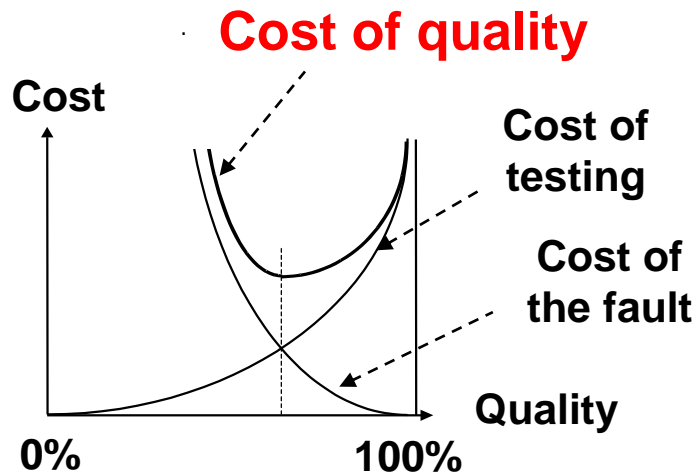
$$C(\text{Design} + \text{Test}) < C(\text{Design}) + C(\text{Test})$$



Performance \downarrow

Logic complexity \uparrow
Area \uparrow
Number of I/O \uparrow


Power consumption \uparrow
Yield \downarrow

Design for Testability

Economic tradeoff:

$$C(\text{Design} + \text{Test}) < C(\text{Design}) + C(\text{Test})$$
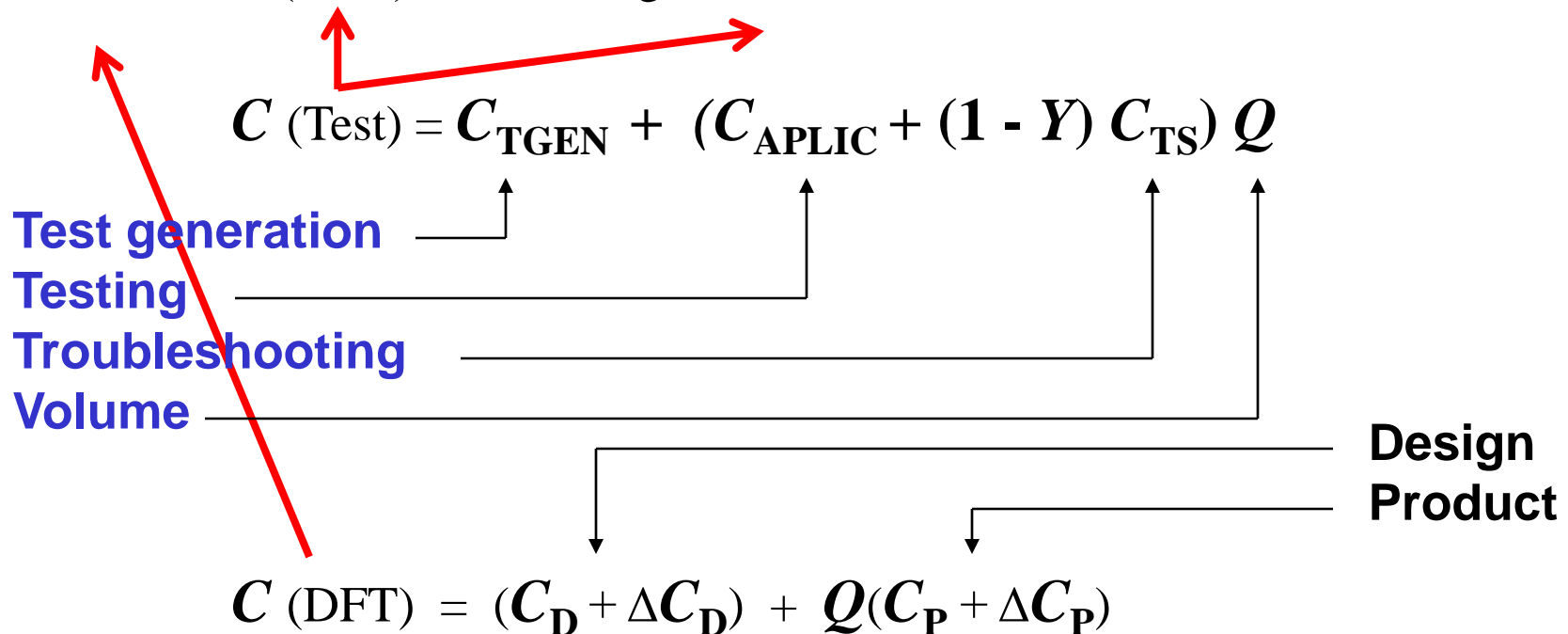
$$C(\text{DFT}) + C(\text{Test}') < C(\text{Design}) + C(\text{Test})$$



Testability Criteria

Qualitative criteria for Design for testability:

Testing cost:

- Test generation time
- Test application time
- Fault coverage
- Test storage cost (test length)
- Availability of Automatic Test Equipment

The cost of re-design for testability:

- Performance degradation
- Area overhead
- I/O pin demand

Testability of Design Types

General important relationships:

1. **T (Sequential logic) < T (Combinational logic)**

Solutions: Scan-Path design strategy

2. **T (Control logic) < T (Data path)**

Solutions: Data-Flow design, Scan-Path design strategies


3. **T (Random logic) < T (Structured logic)**

Solutions: Bus-oriented design, Core-oriented design


4. **T (Asynchronous design) < T (Synchronous design)**

Testability of Design Types

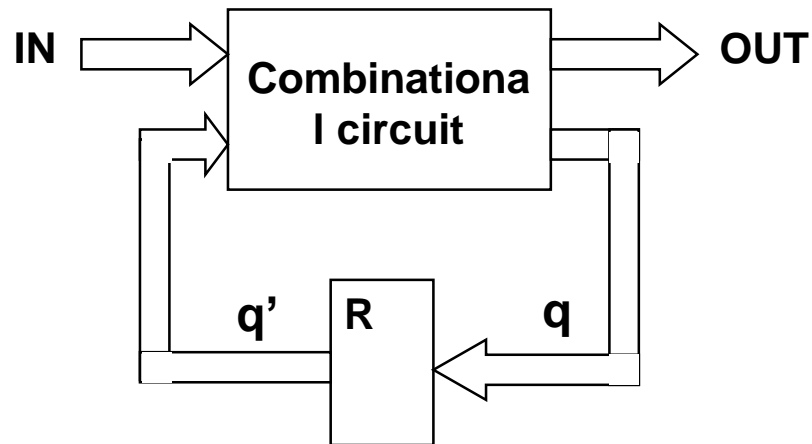1. T (Sequential logic) < T (Combinational logic)



Solution: Scan-Path design strategy

 



Testability of Design Types

2. T (Control logic) < T (Data path)

Solutions:


Scan-Path design strategie

Data-Flow design

 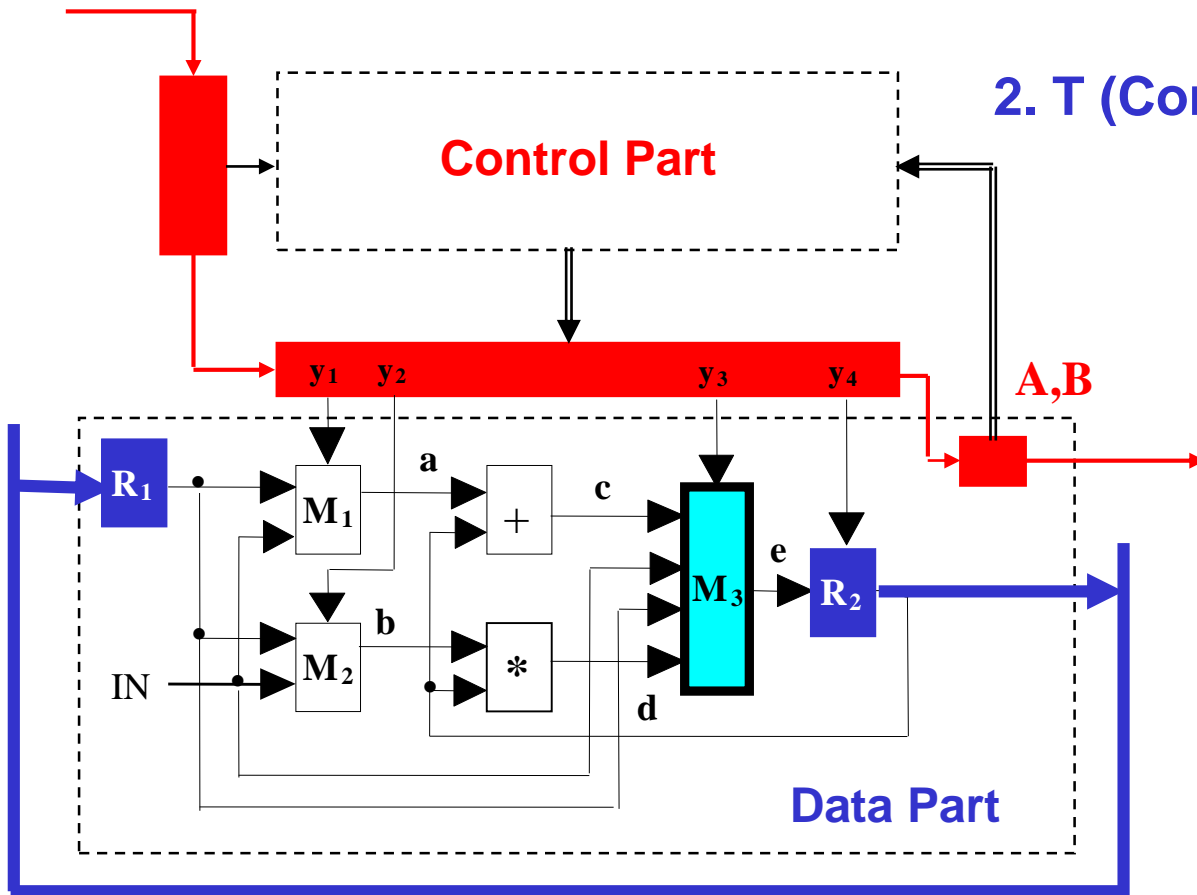



Scan-Path Based Testing

How to test million transistors?

 

H.-J.Wunderlich, U Stuttgart

  All **memory components** are made **“transparent”** via shift registers




Signal path through millions transistors



Testability of Design Types

 3. T (Random logic) $<$ T (Structured logic)

Solutions: Bus-oriented design, Core-oriented design



Testability Estimation Rules of Thumb

Circuits less controllable


- Decoders
- Circuits with feedback
- Counters
- Clock generators
- Oscillators
- Self-timing circuits
- Self-resetting circuits

Circuits less observable


- Circuits with feedback
- Embedded
 - RAMs
 - ROMs
 - PLAs
- Error-checking circuits
- Circuits with redundant nodes

Bad Testability: Fault Redundancy

Redundant gates (bad design):

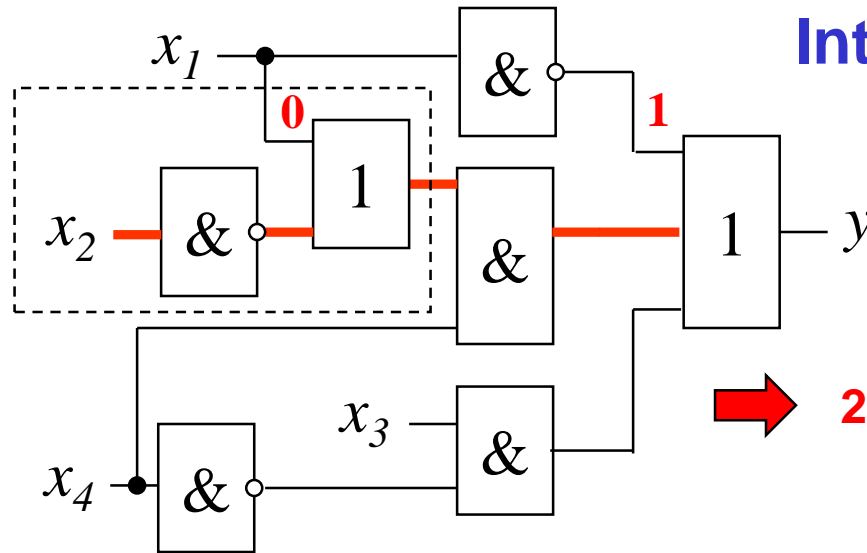

Internal signal dependencies:

 

28 faults

Impossible pattern,
OR \rightarrow XOR is not testable

$$y = \overline{x_1} \vee (x_1 \vee \overline{x_2})x_4 \vee \overline{x_3}x_4$$

$$\frac{\partial y}{\partial x_2} \equiv 0$$

Faults at x_2 is not testable


Optimized function:

$$y = \overline{x_1} \vee x_4 \vee \overline{x_3}$$

6 faults (21%) !


Fault Redundancy

Hazard control circuit:

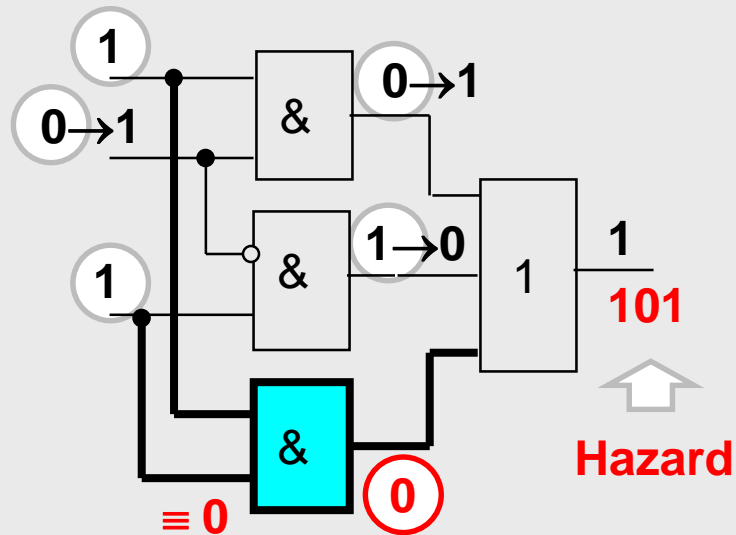

Redundant AND-gate
 Fault $\equiv 0$ is not testable

Error control circuitry:

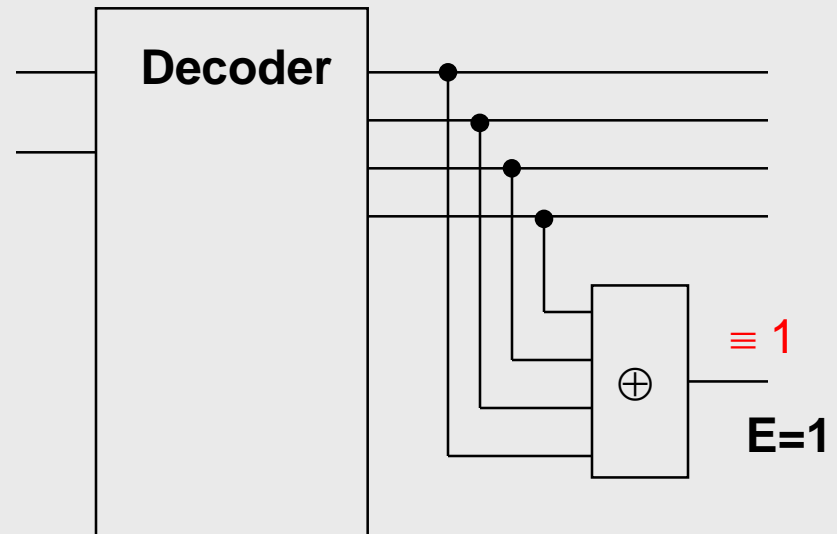

$E = 1$ if decoder is fault-free
 Fault $\equiv 1$ is not testable

Hard to Test Faults

Evaluation of testability:


- Controllability

- $C_0(i)$
- $C_1(j)$

- Observability

- $O_Y(k)$
- $O_Z(k)$

- Testability

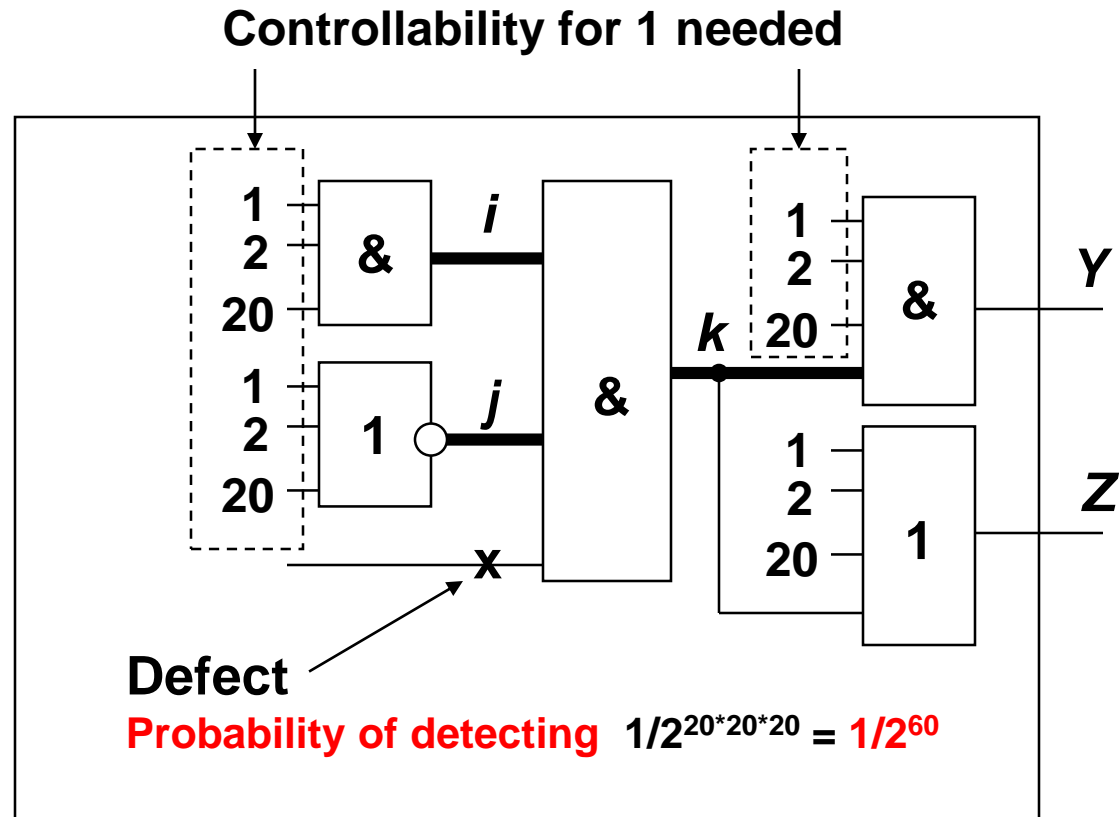

Consequences of Bad Testability

- ✓ **Expected impact** of good testability
 - Reduces cost of deterministic test generation
 - Reduces cost of testing (time, memory space, length of test)
- ✓ **Redundant faults**
 - **don't need to be tested**, because the functionality of the circuit remains correct
 - if you don't know that the not-covered fault is redundant, the lower fault coverage will mean **ambiguity** – **under-estimating** the test result
- ✓ **Hard-to-test faults**
 - cause reduction of the test quality in **random testing**
 - in **deterministic testing** the problem is solved at higher cost

Testability Analysis Methods


- ✓ **Fault simulation** – a very slow but **exact** method
- ✓ **Toggling** – a faster method, but only **approximate**
 - Logic simulation can be repeated a number of times with different data sets
 - Toggling on a node of a digital circuit means „to switch from 0 to 1, or from 1 to 0“
 - Circuit activity can be measured by **counting the toggles**
- ✓ Disadvantage:
 - Toggling is only a means to characterize the **controllability** of signals, but not the real testability
- ✓ **Calculation of testability measures**
 - Heuristic methods
 - Probabilistic methods

Testability Analysis with Fault Simulation

Fault table
As a result of
fault simulation

	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇
T ₁	0	1	1	0	0	0	0
T ₂	1	0	0	1	0	0	0
T ₃	1	1	0	1	0	1	0
T ₄	0	1	0	0	1	0	0
T ₅	0	0	1	0	1	1	0
T ₆	0	0	1	0	0	1	1


Fault detectability spectrogramm

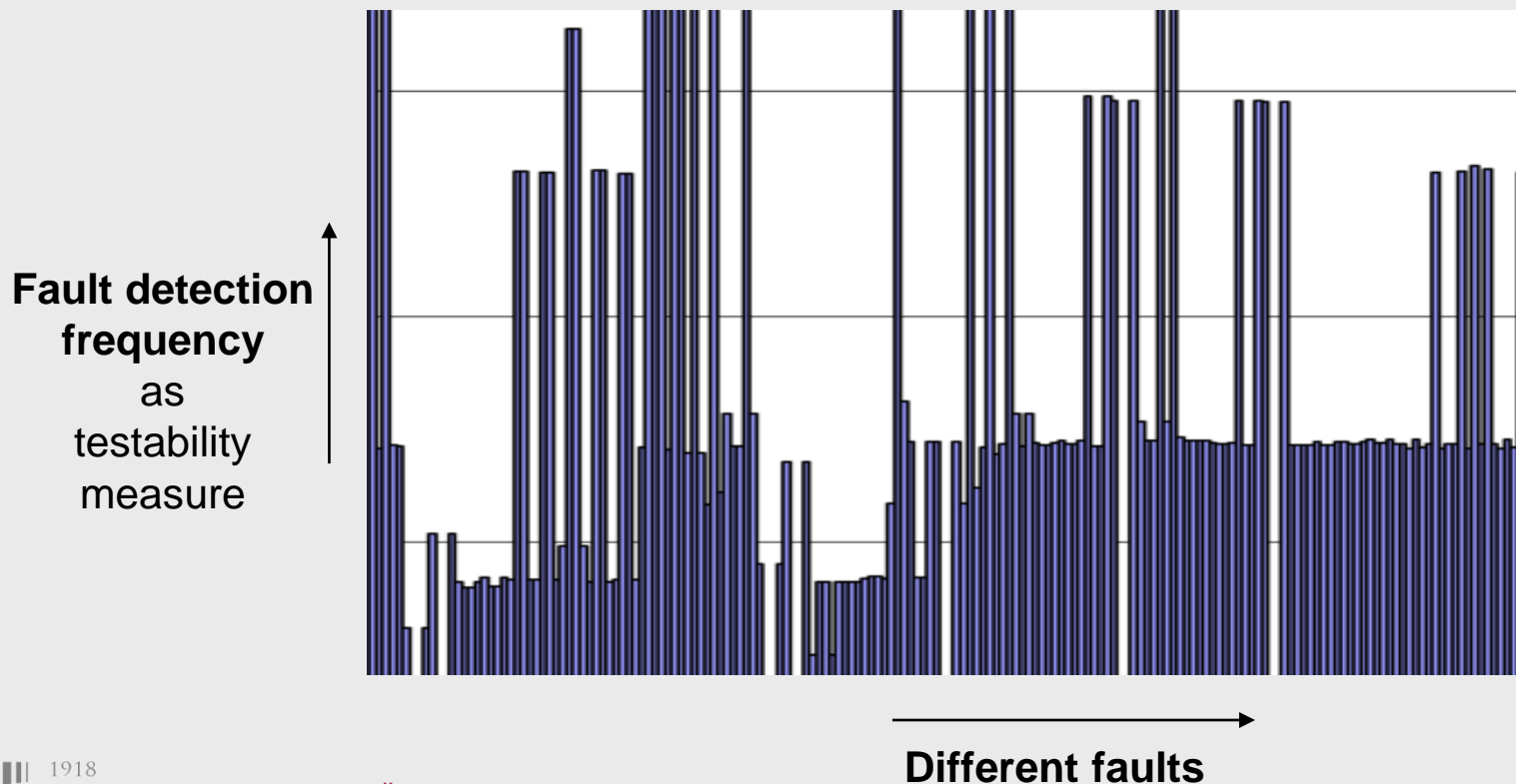

The lower
the frequency,
the lower
the testability

DFT Using Control Points

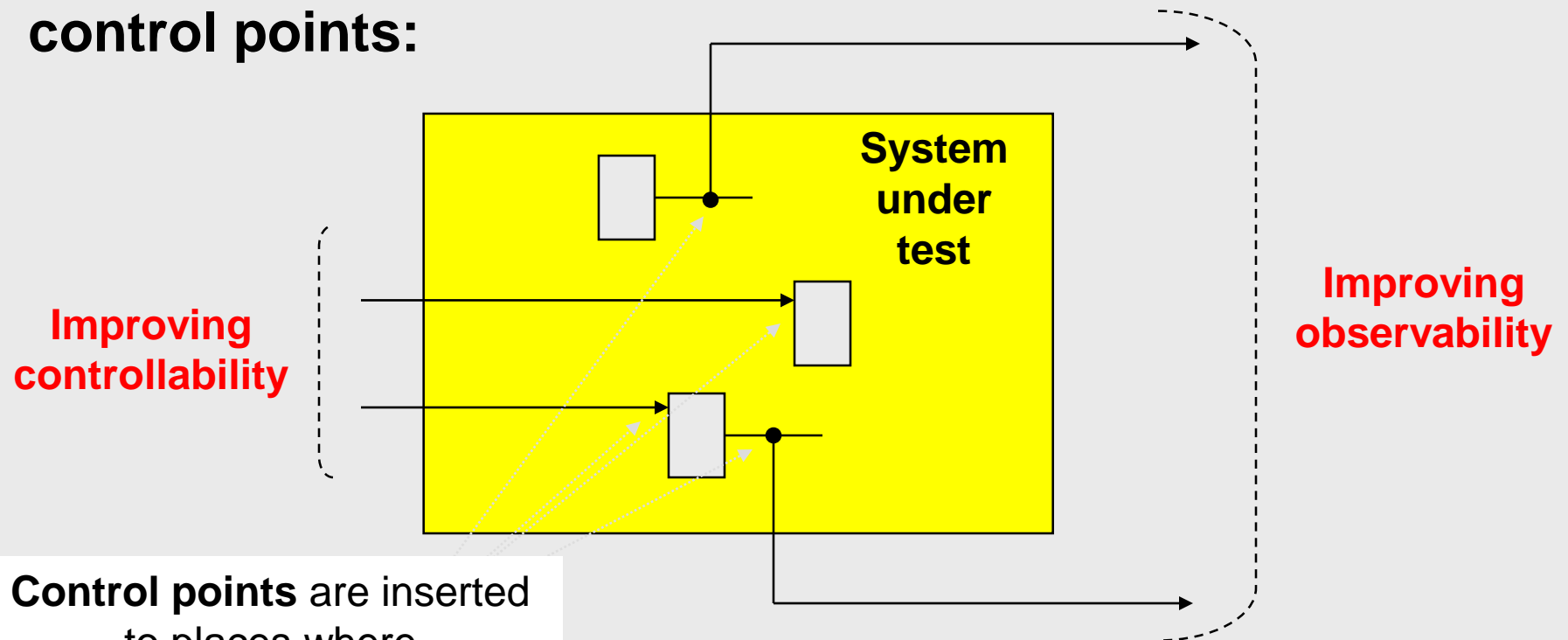To ways for improving testability with inserting of control points:



Control points are inserted to places where controllability or observability are low

To select control points, the testability **measures** are to be calculated


Heuristic Testability Measures

Controllability calculation: AND gate

Measure: minimum number of nodes that must be set to produce 0 or 1

For inputs: $C_0(x) = C_1(x) = 1$

 For other signals: recursive calculation starting from inputs




Heuristic Testability Measures

Controllability calculation: AND gate

Measure: minimum number of nodes that must be set to produce 1

For inputs: $C_0(x) = C_1(x) = 1$

 For other signals: recursive calculation starting from inputs




Heuristic Testability Measures

Controllability calculation: OR gate

Measure: **minimum number of nodes** that must be set to produce 0

For inputs: $C_0(x) = C_1(x) = 1$

 For other signals: **recursive calculation** starting from inputs




Heuristic Testability Measures

Controllability calculation: EXOR gate

Measure: **minimum number of nodes** that must be set in order **to produce 0**

For inputs: $C_0(x) = C_1(x) = 1$

 For other signals: **recursive calculation** starting from inputs







Heuristic Testability Measures

Controllability calculation:

Measure: minimum number of nodes that must be set in order **to produce 0 or 1**

For inputs: $C_0(x) = C_1(x) = 1$

    For other signals: recursive calculation rules:




Heuristic Testability Measures

Observability calculation:

Measure: minimum number of nodes which must be set **for fault propagating**

For outputs: $O(y) = 1$

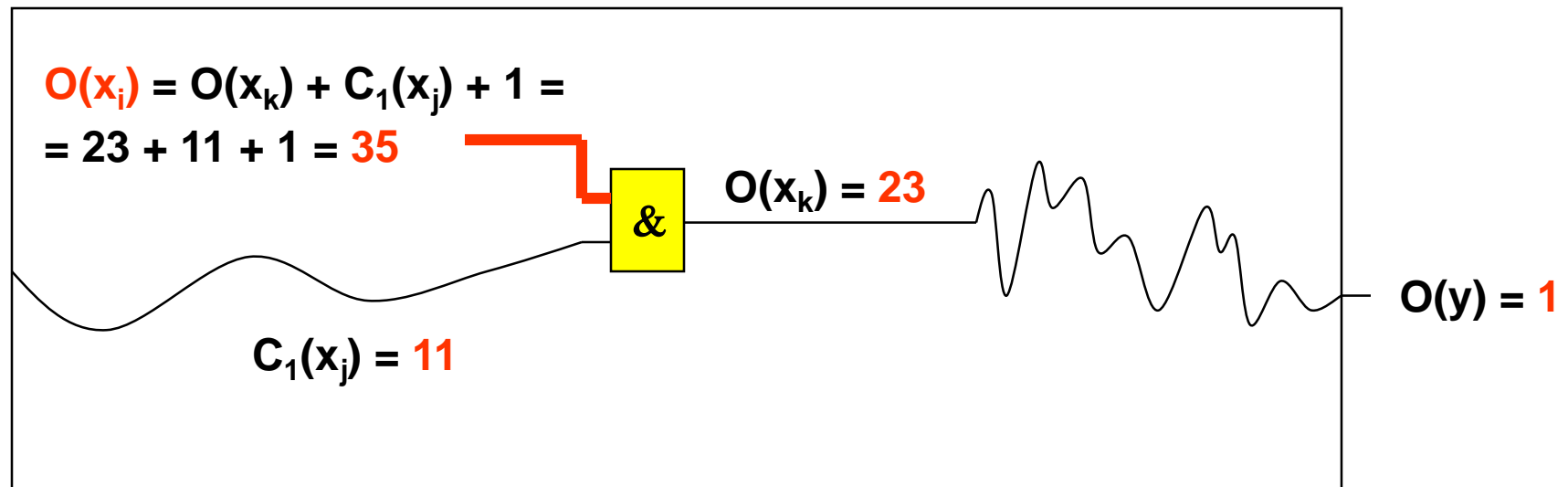For other signals: **recursive calculation** starting from outputs







Heuristic Testability Measures

Observability calculation:

Measure: minimum number of nodes which must be set **for fault propagating**

For outputs: $O(y) = 1$

    For other signals: recursive calculation rules:




Heuristic Testability Measures

Testability calculation:

Measure: sum of controllability and observability


$$T(x \equiv 0) = C_1(x) + O(x)$$

$$T(x \equiv 1) = C_0(x) + O(x)$$

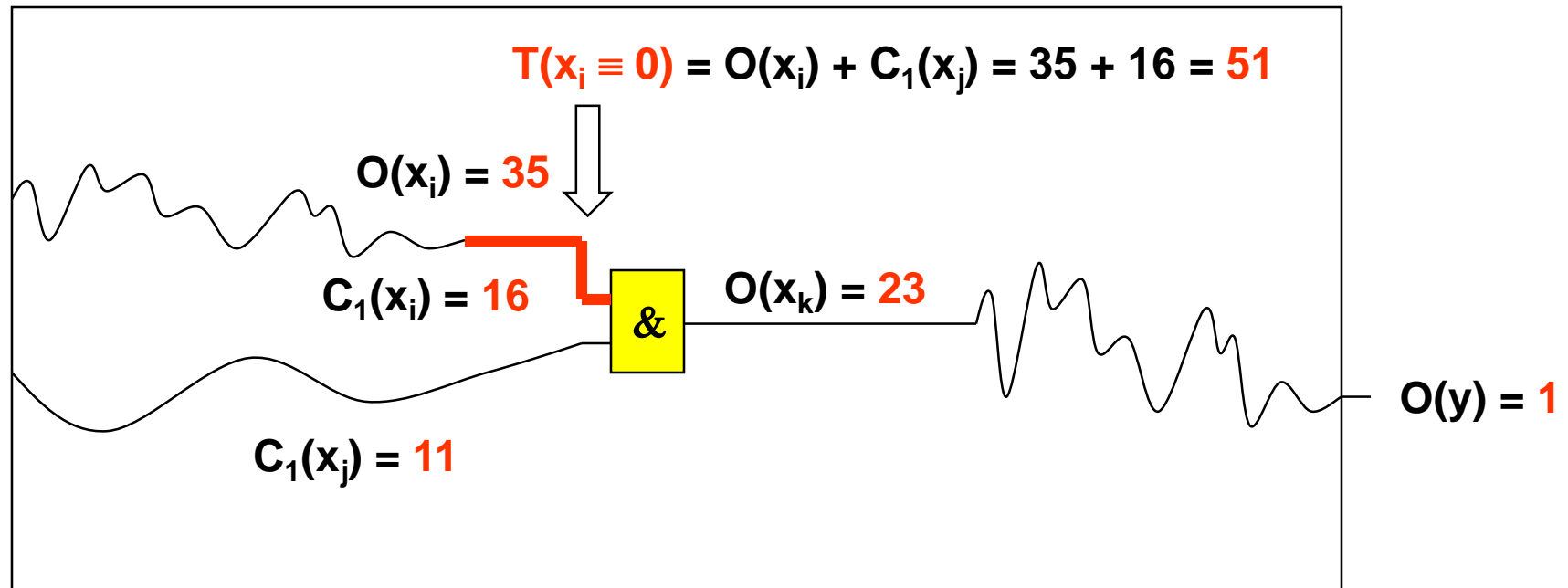

Heuristic Testability Measures

Controllability and observability:

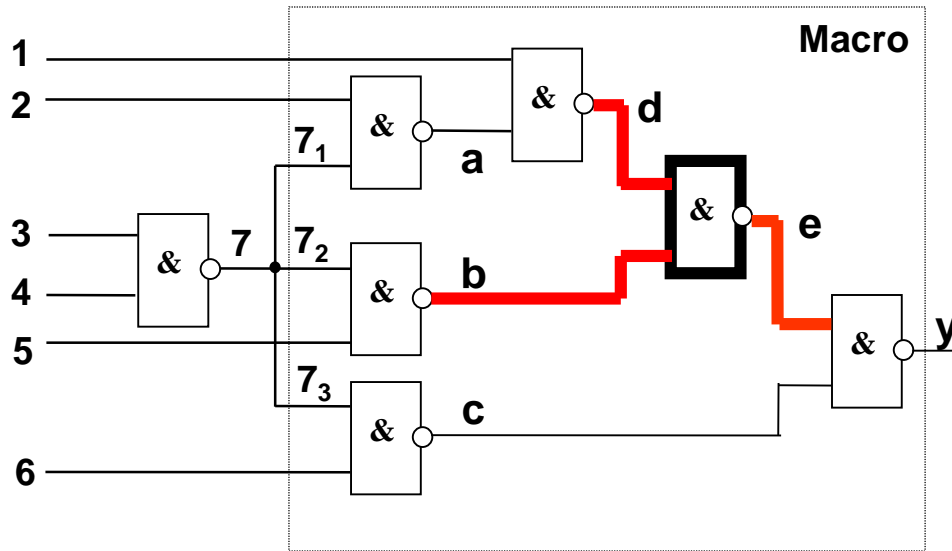


	Controllabilities		Obs.
x	$C_0(x)$	$C_1(x)$	$O(x)$
1	1	1	10
2	1	1	12
3	1	1	11
4	1	1	11
5	1	1	10
6	1	1	10
7	3	2	9
7 ₁	3	2	11
7 ₂	3	2	9
7 ₃	3	2	9
a	4	2	9
b	4	2	7
c	4	2	7
d	4	2	7
e	5	5	4
y	8	5	1

Heuristic Testability Measures

Testability calculation:

$$T(x \equiv 0) = C_1(x) + O(x)$$

$$T(x \equiv 1) = C_0(x) + O(x)$$

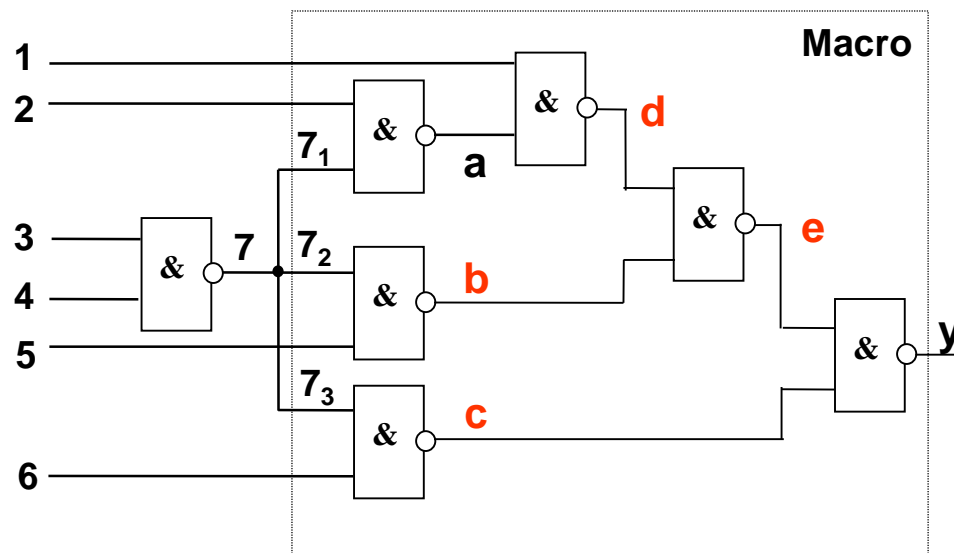

x	Controllabilities		Obs.	Testab.
	$C_0(x)$	$C_1(x)$	$O(x)$	$T(x \equiv 0)$
1	1	1	10	11
2	1	1	12	13
3	1	1	11	12
4	1	1	11	12
5	1	1	10	11
6	1	1	10	11
7	3	2	9	11
7 ₁	3	2	11	13
7 ₂	3	2	9	11
7 ₃	3	2	9	11
a	4	2	9	11
b	4	2	7	9
c	4	2	7	9
d	4	2	7	9
e	5	5	4	9
y	8	5	1	6

Why the testability of y is the lowest?






Probabilistic Testability Measures

Controllability calculation:

Measure: probability to produce 0 or 1 at the given nodes $p_{xi} = p(x_i=1) = 1$


For inputs: $C_0(i) = 1 - p_{xi}$ $C_1(i) = p_{xi}$

     For other signals: recursive calculation rules:




Paradoxes of Probabilistic Measures

Probabilities of reconverging fanouts:

 

 
$$p_y = (1 - p_{x_1}) p_{x_2} + (1 - p_{x_2}) p_{x_1} \\ = 0,25 + 0,25 = \mathbf{0,5}$$




$$p_y = 1 - (1 - p_a)(1 - p_b) \\ = 1 - 0,75 * 0,75 = \mathbf{0,44}$$

Signal correlations:


 


$$p_y = p_{x_1} p_{x_1} = p_x^2 = p_x$$

Calculation of Signal Probabilities

 

SSBDD based algorithm:

  

$$p_y = x_1(1-x_2) + (1-x_1)x_2 = 0,5$$


Parker - McCluskey algorithm:

$$\begin{aligned}
 p_y &= 1 - (1 - p_a) (1 - p_b) = \\
 &= 1 - (1 - p_{x_1}(1 - p_{x_2}))(1 - p_{x_2}(1 - p_{x_1})) = \\
 &= 1 - (1 - p_{x_1} + p_{x_1}p_{x_2}) (1 - p_{x_2} + p_{x_1}p_{x_2}) = \\
 &= 1 - (1 - p_{x_2} + p_{x_1}p_{x_2} - p_{x_1} + p_{x_1}p_{x_2} - p_{x_1}^2 p_{x_2} + \\
 &\quad + p_{x_1}p_{x_2} - p_{x_1} p_{x_2}^2 + p_{x_1}^2 p_{x_2}^2) = \\
 &= 1 - (1 - p_{x_2} + p_{x_1}p_{x_2} - p_{x_1} + p_{x_1}p_{x_2} - p_{x_1} p_{x_2} + \\
 &\quad + p_{x_1}p_{x_2} - p_{x_1} p_{x_2} + p_{x_1} p_{x_2}) = \\
 &= p_{x_2} - p_{x_1}p_{x_2} + p_{x_1} - p_{x_1}p_{x_2} + p_{x_1}p_{x_2} - \\
 &\quad - p_{x_1}p_{x_2} + p_{x_1} p_{x_2} - p_{x_1} p_{x_2}) = \\
 &= p_{x_1} + p_{x_2} - 2p_{x_1}p_{x_2} = 0,5
 \end{aligned}$$

The exponents are removed

Calculation of Signal Probabilities

 Two methods: (1) from INP to OUT, (2) from OUT to INP



For all inputs: $p_k = 1/2$

Fast calculation gate by gate:

$$p_a = 1 - p_1 p_2 = 0,75,$$


$$p_b = 0,75, \quad p_c = 0,43, \quad p_y = 0,22$$

Parker - McCluskey algorithm:

$$\begin{aligned} p_y &= p_c p_2 = (1 - p_a p_b) p_2 = \\ &= (1 - (1 - p_1 p_2) (1 - p_2 p_3)) p_2 = \\ &= p_1 p_2^2 + p_2^2 p_3 - p_1 p_2^3 p_3 = \\ &= p_1 p_2 + p_2 p_3 - p_1 p_2 p_3 = 0,38 \end{aligned}$$

Probabilistic Testability Measures

Parker-McCluskey:

 

For all inputs: $p_k = 1/2$

Observability:


$$\begin{aligned} p(\partial y / \partial a = 1) &= p_b p_2 = \\ &= (1 - p_2 p_3) p_2 = p_2 - p_2^2 p_3 \\ &= p_2 - p_2 p_3 = \mathbf{0,25} \end{aligned}$$

Testability:

$$\begin{aligned} p(\mathbf{a} \equiv 1) &= p(\partial y / \partial a = 1) (1 - p_a) = \\ &= (p_2 - p_2 p_3)(p_1 p_2) = \\ &= p_1 p_2^2 - p_1 p_2^2 p_3 = \\ &= p_1 p_2 - p_1 p_2 p_3 = \mathbf{0,125} \end{aligned}$$

Calculation of Signal Probabilities

Parker - McCluskey algorithm:

 

Conclusions:

The **P-McC** method has a high complexity

In tree-like circuits, the **gate-by-gate** method works accurately

$$\begin{aligned}
 p_y &= 1 - (1 - p_a)(1 - p_b) = \\
 &= 1 - (1 - p_{x_1}(1 - p_{x_2}))(1 - p_{x_2}(1 - p_{x_1})) = \\
 &= 1 - (1 - p_{x_1} + p_{x_1}p_{x_2})(1 - p_{x_2} + p_{x_1}p_{x_2}) = \\
 &= 1 - (1 - p_{x_2} + p_{x_1}p_{x_2} - p_{x_1} + p_{x_1}p_{x_2} - p_{x_1}^2p_{x_2} + \\
 &\quad + p_{x_1}p_{x_2} - p_{x_1}p_{x_2}^2 + p_{x_1}^2p_{x_2}^2) = \\
 &= 1 - (1 - p_{x_2} + p_{x_1}p_{x_2} - p_{x_1} + p_{x_1}p_{x_2} - p_{x_1}p_{x_2} + \\
 &\quad + p_{x_1}p_{x_2} - p_{x_1}p_{x_2} + p_{x_1}p_{x_2}) = \\
 &= p_{x_2} - p_{x_1}p_{x_2} + p_{x_1} - p_{x_1}p_{x_2} + p_{x_1}p_{x_2} - \\
 &\quad - p_{x_1}p_{x_2} + p_{x_1}p_{x_2} - p_{x_1}p_{x_2}) = \\
 &= p_{x_1} + p_{x_2} - 2p_{x_1}p_{x_2} = 0,5
 \end{aligned}$$

Calculation of Signal Probabilities

Cutting method


Idea:

- The complexity of exact calculation is reduced by using lower and higher bounds of probabilities

Technique:

- Reconvergent fan-outs are cut **except of one**
- Probability range of $[0,1]$ is assigned to all the cut lines
- The bounds are propagated by straightforward calculation

 New independent probabilities (no correlation)



Probability to be used in calculations (no correlation)

Lower and higher bounds for the probabilities of the cut lines:


$$p_{7_1} := (0;1), p_{7_2} := (0;1), p_{7_3} := 0,75$$

Calculation of Signal Probabilities

Cutting method

Technique:

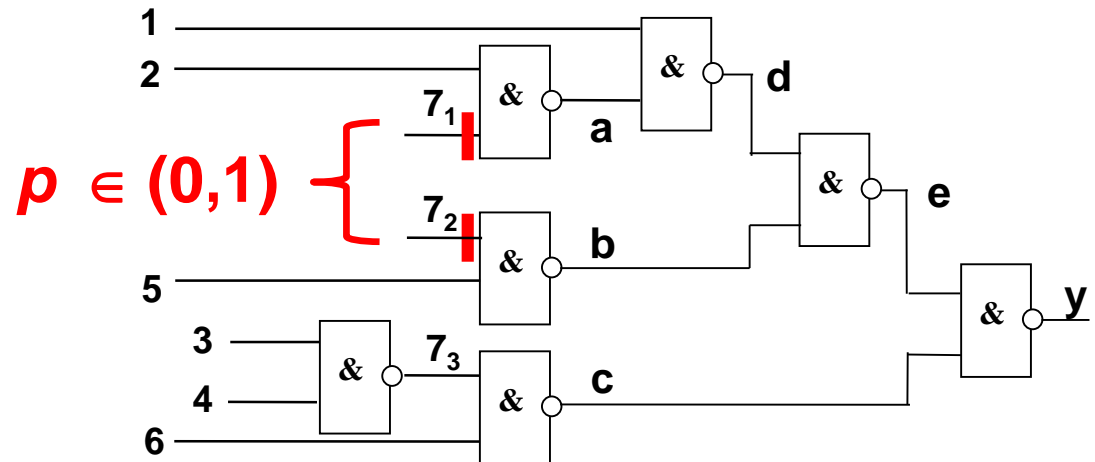- Reconvergent fan-outs are cut **except of one**
- Probability range of $[0,1]$ is assigned to all the cut lines
- The new probabilities are propagated by straightforward calculation




Lower and higher bounds for the probabilities of the cut lines:

$$p_{7_1} := (0;1), \quad p_{7_2} := (0;1), \quad p_{7_3} := 0,75$$

Calculation of Signal Probabilities

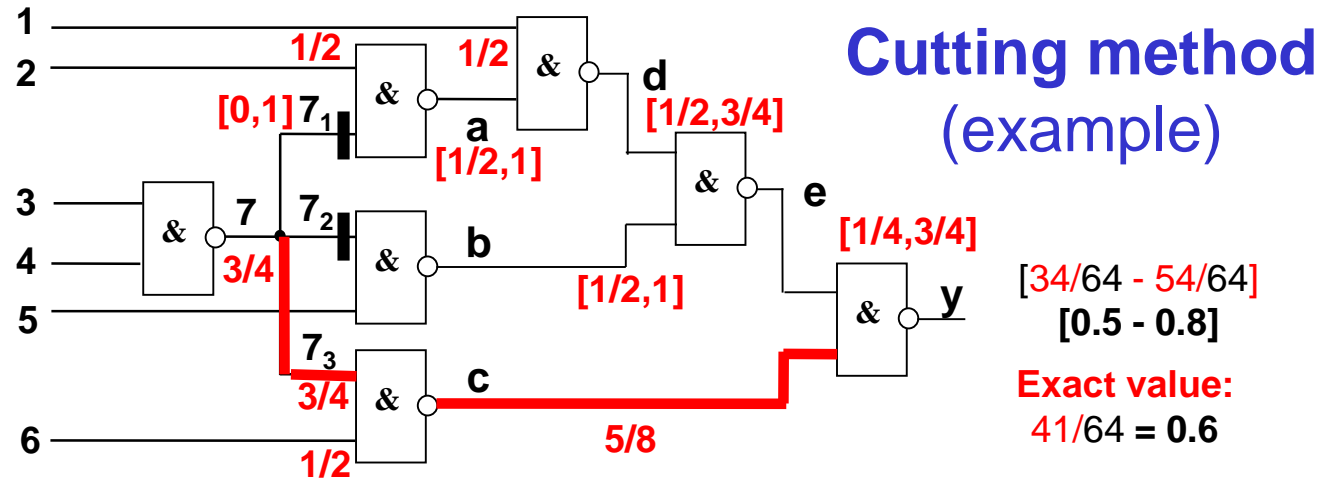- For all inputs: $p_k = 0,5$
- Reconvergent fan-outs are cut except of one – 7_1 and 7_2
- Probability range of $[0,1]$ is assigned to all the cut lines - 7_1 and 7_2
- The bounds are propagated by straightforward calculation




Calculation steps:

p_k	$[p_{LB}, p_{HB})$	Exact p_k	p_k	$[p_{LB}, p_{HB})$	Exact p_k
p_7	$3/4$	$3/4$	p_b	$[1/2, 1]$	$5/8$
p_{7_1}	$[0, 1]$	$3/4$	p_c	$5/8$	$5/8$
p_{7_2}	$[0, 1]$	$3/4$	p_d	$[1/2, 3/4]$	$11/16$
p_{7_3}	$3/4$	$3/4$	p_e	$[1/4, 3/4]$	$19/32$
p_a	$[1/2, 1]$	$5/8$	p_y	$[34/64, 54/64]$	$41/64$

Calculation of Signal Probabilities

Method of conditional probabilities

 

$$P(y) = p(y/x=0) p(x=0) + p(y/x=1) p(x=1)$$

Probability for $- y$


Conditions – $x \in$ set of conditions

$$p(y) = \sum_{i \in (0,1)} p(y/(x=i)) p(x=i)$$

Conditional probability

Calculation of Signal Probabilities

Method of conditional probabilities

 

$$P(y) = p(y/x=0) p(x=0) + p(y/x=1) p(x=1)$$

Idea of the method:

Two conditional probabilities are calculated along the paths (**NB!** not bounds as in the case of the cutting method)

Since **no reconvergent** fanouts are on the paths, no danger for signal correlations

Probability for $-y$

Conditions – $x \in$ set of conditions


$$p(y) = \sum_{i \in (0,1)} p(y/(x=i)) p(x=i)$$

Conditional probability

Calculation of Signal Probabilities

Method of conditional probabilities
 
$$p(y) = \sum_{i \in \{0,1\}} p(y/(x=i)) p(x=i)$$




NB! Conditional probabilities

$P_k \sim [P_k^0 = p(x_k/x_7=0), P_k^1 = p(x_k/x_7=1)]$

are propagated, not bounds

as in the cutting method.

For all inputs: $p_k = 1/2$

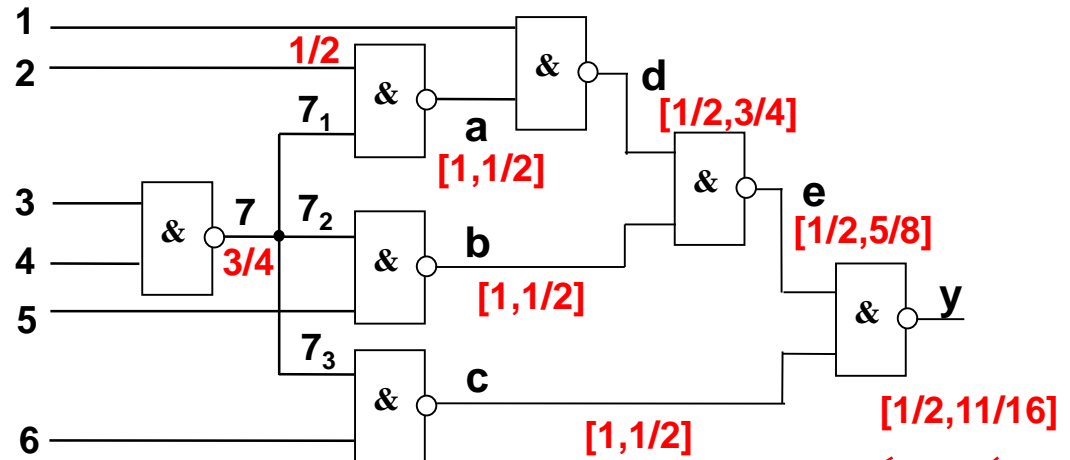

$$p_y = p(y/x_7=0)(1 - p_7) + p(y/x_7=1)p_7 = (1/2 \times 1/4) + (11/16 \times 3/4) = 41/64$$

Random Pattern Test Length


Terminology

- **Detection probabilities:**
 - n -th step detection probability of a fault
 - n -th step detection probability of a fault set
- **Worst fault** - that fault having the lowest detection probability of any fault in the Network (independently of probabilities for other faults)
- **Escape Probability of a Fault Set:** the probability that at least one member of the fault set will not be detected by the random pattern test
 - For an n -step test, the escape probability of a fault set is denoted e_n
- The *escape probability* and the *detection probability* sum to one
- **Escape probability** is the **quality measure** of the random pattern test

Higher escape probabilities will require *longer* random pattern tests

Random Pattern Test Length

 The faults are said to have **conjoint test sets** if their corresponding test sets share at least one vector



A Venn diagram showing the detection probabilities of two faults.

p_1 – is the probability that a randomly selected vector will detect **fault f_1 but not f_2**


p_2 – is the probability that a randomly selected vector will detect **fault f_2 but not f_1**

p_3 – is the probability that the vector will detect both faults

The detection probability of fault f_1 is $p_1 + p_3$, and that of fault f_2 is $p_2 + p_3$

If $p_3 = 0$, then the corresponding test sets are **disjoint**

Random Pattern Test Length

 

A Venn diagram showing the detection probabilities of two faults.

The **escape probability** of the fault-set for the **disjoint case** is given by

$$e_n = (1 - p_1)^n + (1 - p_2)^n - [1 - (p_1 + p_2)]^n.$$

In order to compute the minimum random **test length** n that detects the fault set with **escape probability no larger than threshold** e_t , it is necessary to compute n that satisfies

$$e_n < e_t$$

Random Pattern Test Length

The random test length due to **k faults** with disjoint test sets, **each with** detection probability **p** is bounded by

$$N_{kD}^U = \left\lceil \frac{\ln(e_t/k)}{\ln(1-p)} \right\rceil$$
$$N_{kD}^L = \left\lceil \frac{\ln(e_t/k) - \ln(1 - e_t/2)}{\ln(1-p)} \right\rceil$$

For practical values of **p** and **e_t** (values much less than one) the formula can be approximated by

$$N_{kD}^U \cong \left\lceil \frac{\ln k - \ln e_t}{p} \right\rceil$$

For the case where **$e_t = 10^{-3}$** (the confidence 99,9%)

$$N_{kD}^U \cong \left\lceil \frac{6.9 + \ln k}{p} \right\rceil$$

Example: Random pattern test **$11/p$** can detect as many as **$k = 50$** hard faults, each having a detection probability with a **confidence of 99,9 %**

Literature: Jacob Savir, Paul H. Bardell „On random pattern test length“. IEEE Trans. on Comp., 1984

Random Pattern Test Length

Examples

for the case of confidence of

$$e_t = 99,9\%$$

Test length as the function of the size of the set of hard faults k and for practical values of $p < 1$



k	ln k	ln k - ln e	(Lnk-Lne)/p
1	0	7	690776
10	2	9	921034
20	3	10	990349
30	3	10	1030895

$$N_{kD}^U \cong \left\lceil \frac{\ln k - \ln e_t}{p} \right\rceil$$



Test length as the function of the fault detection probability p for the size of the set of hard faults $k = 1$



k	ln k	p	lne/ln(1-p)
1	0	0,01	687
1	0	0,001	6904
1	0	0,0001	69074
1	0	0,00001	690772


BDDs and Testing of Logic Circuits
  
$$y = x_1 \vee x_2 (x_3 \vee x_4 x_5) \vee x_6 x_7$$



Two types of BDDs


Test generation for: $x_{11} \equiv 0$

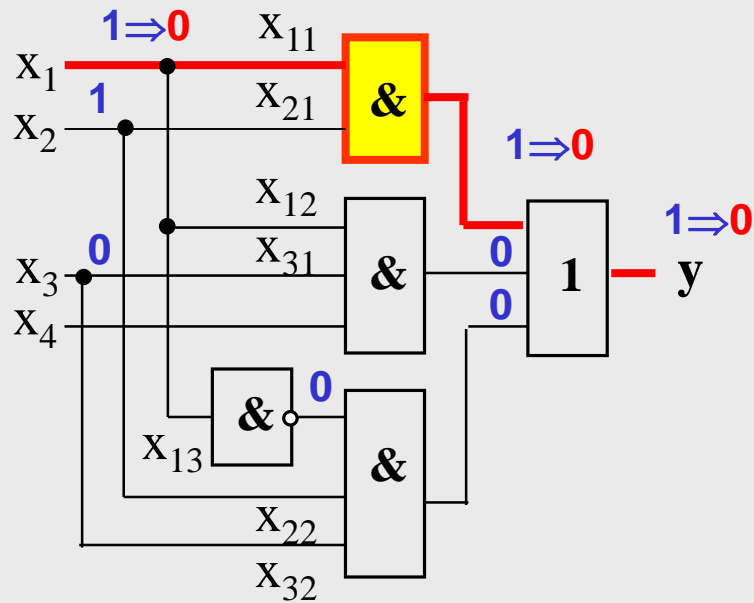


Test pattern:

x_1	x_2	x_3	x_4	y
1	1	0	-	$1 \Rightarrow 0$

Structural BDD:

 




Functional BDD:

 


Calculation of Signal Probabilities with BDDs

Using BDDs:

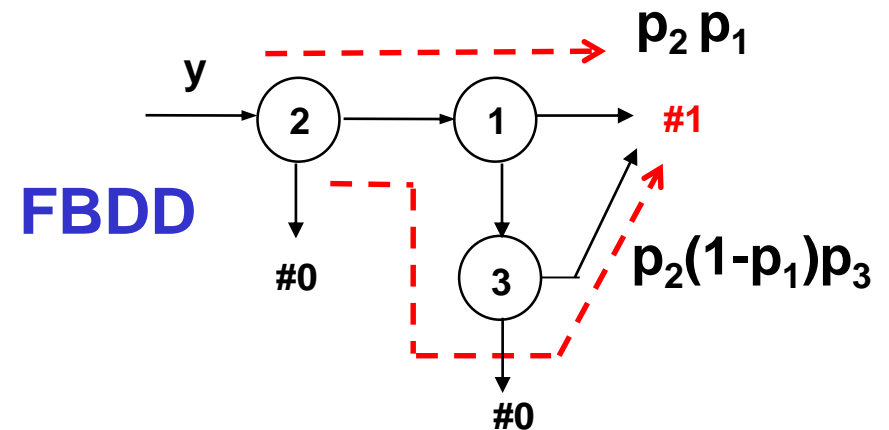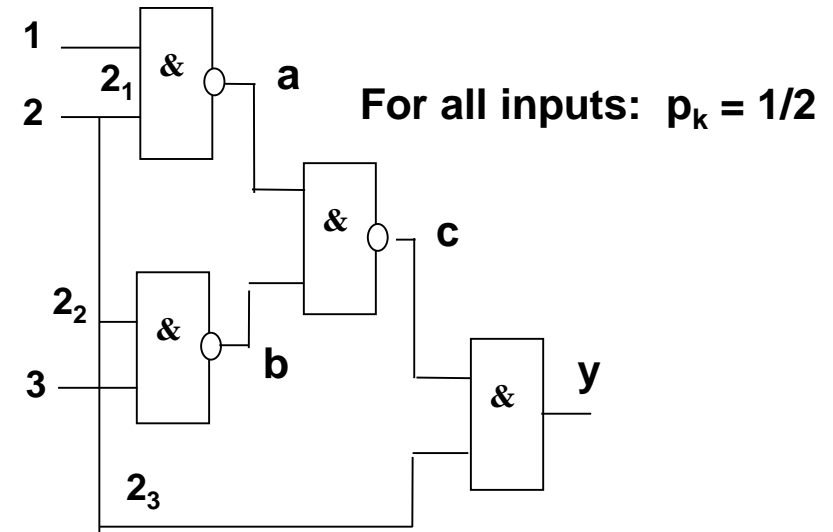
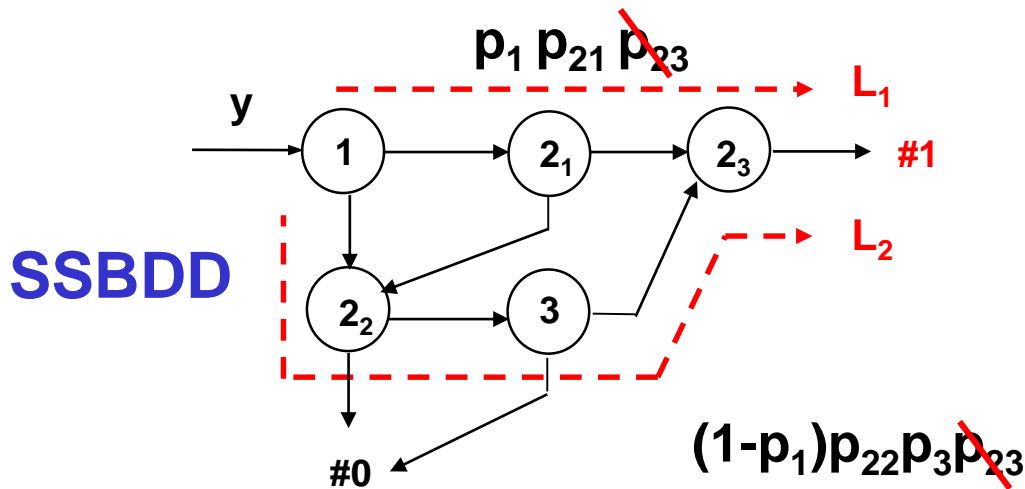
$$\begin{aligned}
 p_y &= p(L_1) + p(L_2) = \\
 &= p_1 p_{21} p_{23} + (1 - p_1) p_{22} p_3 p_{23} = \\
 &= p_1 p_2 + (1 - p_1) p_2 p_3 = 0,38
 \end{aligned}$$



Calculation of Signal Probabilities

 

SSBDD based algorithm:

  

$$p_y = x_1(1-x_2) + (1-x_1)x_2 = 0,5$$


Parker - McCluskey algorithm:

$$\begin{aligned}
 p_y &= 1 - (1 - p_a) (1 - p_b) = \\
 &= 1 - (1 - p_{x_1}(1 - p_{x_2}))(1 - p_{x_2}(1 - p_{x_1})) = \\
 &= 1 - (1 - p_{x_1} + p_{x_1}p_{x_2}) (1 - p_{x_2} + p_{x_1}p_{x_2}) = \\
 &= 1 - (1 - p_{x_2} + p_{x_1}p_{x_2} - p_{x_1} + p_{x_1}p_{x_2} - p_{x_1}^2 p_{x_2} + \\
 &\quad + p_{x_1}p_{x_2} - p_{x_1} p_{x_2}^2 + p_{x_1}^2 p_{x_2}^2) = \\
 &= 1 - (1 - p_{x_2} + p_{x_1}p_{x_2} - p_{x_1} + p_{x_1}p_{x_2} - p_{x_1} p_{x_2} + \\
 &\quad + p_{x_1}p_{x_2} - p_{x_1} p_{x_2} + p_{x_1} p_{x_2}) = \\
 &= p_{x_2} - p_{x_1}p_{x_2} + p_{x_1} - p_{x_1}p_{x_2} + p_{x_1}p_{x_2} - \\
 &\quad - p_{x_1}p_{x_2} + p_{x_1} p_{x_2} - p_{x_1} p_{x_2}) = \\
 &= p_{x_1} + p_{x_2} - 2p_{x_1}p_{x_2} = 0,5
 \end{aligned}$$



The exponents are removed

Example: RT Level Probabilistic Testing

Functional testing

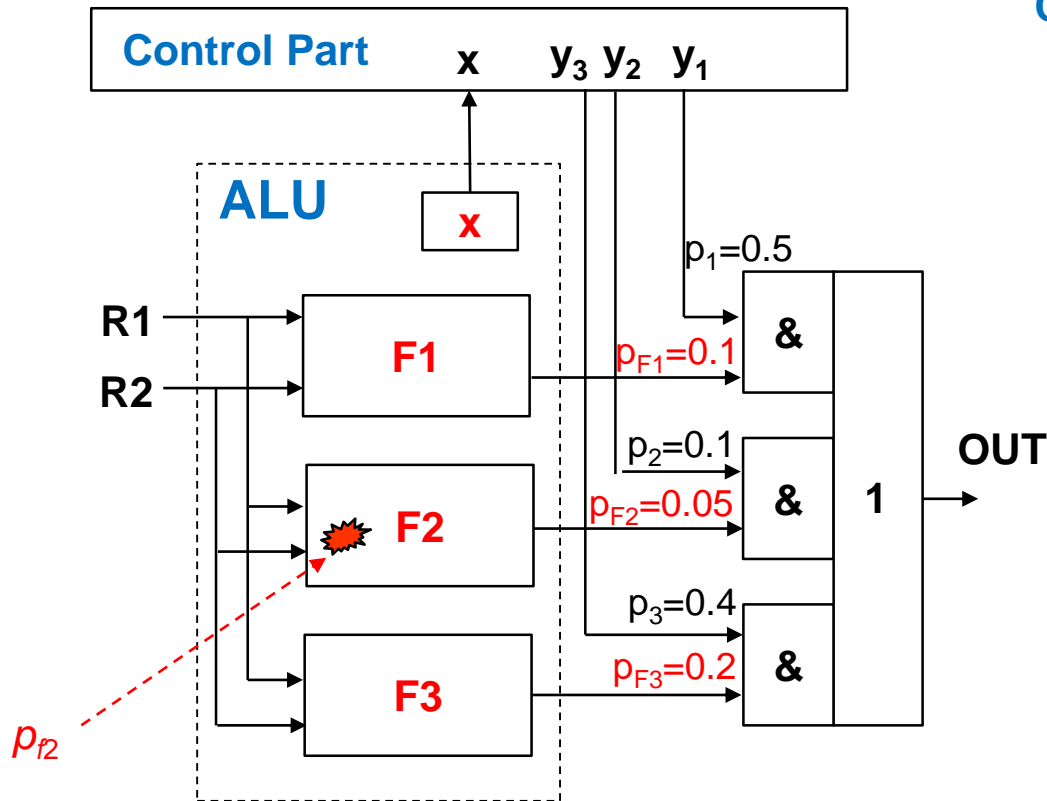

Control Flow

  

$$P(\text{OUT} = F_1) = p_1 = 0.5$$


$$P(\text{OUT} = F_2) = p_2 = p_q * p(x=0) = 0.5 * 0.2 = 0.1$$

$$P(\text{Det of } f_2) = p_2 * p_{F2} = 0.1 * 0.05 = 0.005$$

Generalization of BDDs


Binary DD

 2 terminal nodes and
2 edges from each node



General case of DD


 
$n \geq 2$ terminal nodes and
 $n \geq 2$ edges from each node



Novelty: Boolean methods can be generalized in a straightforward way to higher functional levels

Register Transfer Level DDs

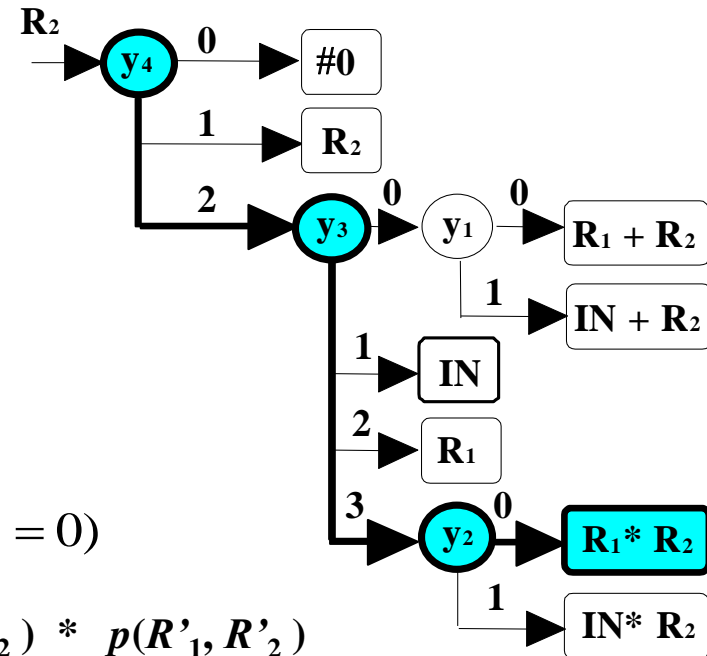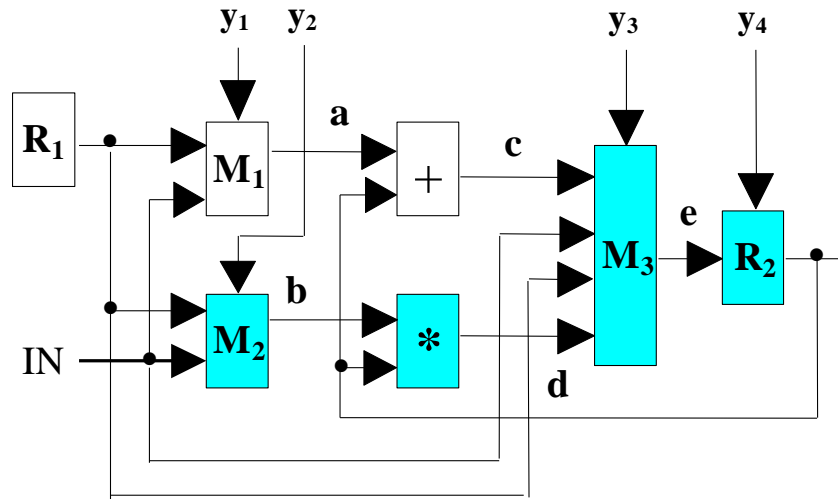Hierarchical calculation of probabilities:



Probability of $p(R_2 = R_1' \times R_2')$

$$p(R_2 = R_1' \times R_2') = p(y_4 = 2) \times p(y_3 = 3) \times p(y_2 = 0)$$

Probability of testing $R_1 * R_2 \rightarrow p(R_2 = R_1' * R_2') * p(R_1', R_2')$


$p(R_1, R_2)$ – can be calculated for the low gate-level multiplier model

All $p(y = k)$ – can be calculated for the low level control part model

Register Transfer Level DDs



LFSR-based BIST

LFSR:

 

Probabilities:

0.5 0.5 0.25 0.5

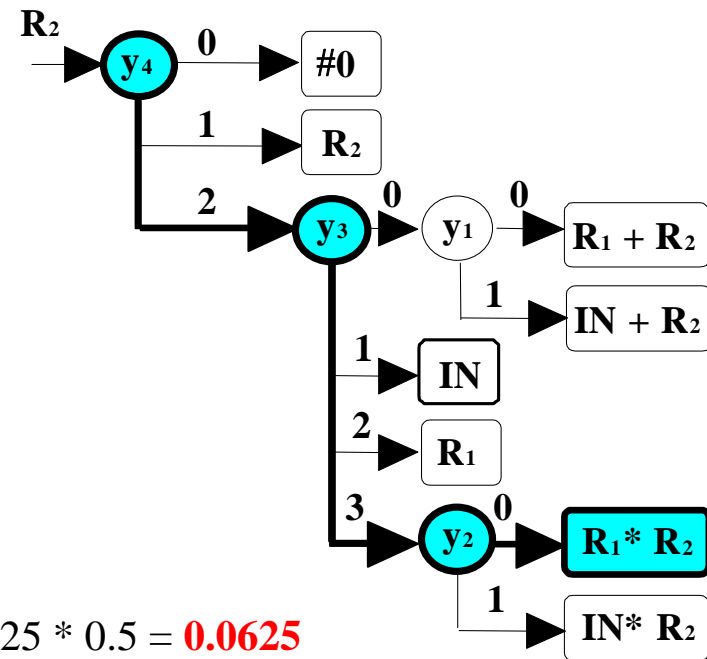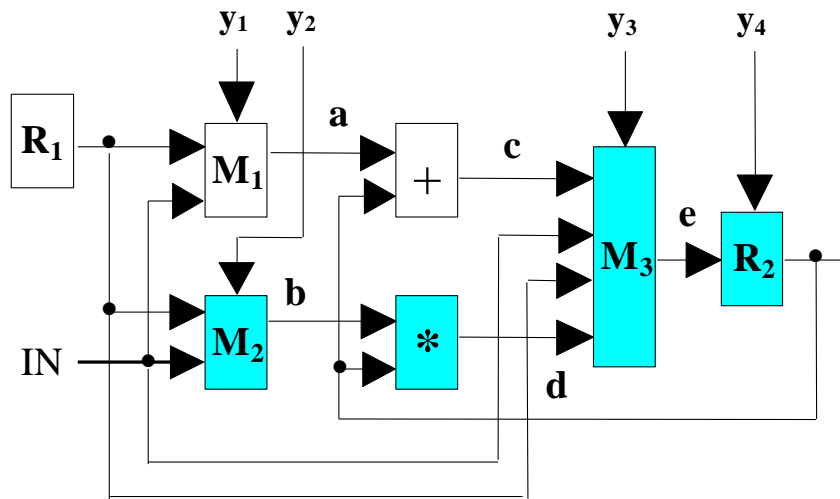


Probability of activating th test $R_1 * R_2 = 0.5 * 0.25 * 0.5 = 0.0625$

Calculating Probabilities on BDDs

$$p_y = \sum_{L_k \in L(1)} \prod_{x \in X_k} p_x$$

Set of paths

Set of nodes on the path

 


Example:

$$L_1 = (1, 2_1, 2_3)$$

$$L_2 = (1, 2_2, 3, 2_3)$$

 
$$p_y = p_1 p_2 + (1 - p_1) p_2 p_3 = 0,375$$



Calculating Probabilities for RT-Level Circuits

Gate-level calculation:
 
$$p_y = \sum_{L_k \in L(1)} \prod_{x \in X_k} p_x$$



Compare


RT-level calculation:

$$P(y=z(m^T)) = \sum_{L_i \in L(m_0, m^T)} \prod_{x \in X_i} P(x)$$

Set of paths

Set of nodes on the path

DD for RT Level Data Path:

 

Calculating Observabilities RT-Level Data Paths

Gate-level calculation:

$$p_y = \sum_{L_k \in L(1)} \prod_{x \in X_k} p_x$$

RT-level calculation:

$$P(y=z(m^T)) = \sum_{L_i \in L(m_0, m^T)} \prod_{x \in X_i} P(x=e)$$

Example:

$$P(R_2 = R_1 * R_2) = P(y_4=2) P(y_3=3) P(y_2=0) = 0.3 * 0.25 * 0.5 = 0.04$$

DD for RTL Data Path:

