 



Course Work (Simplified): Built-In Self-Test

Problems:

- **BIST modeling and simulation**
 - **Test pattern generation** (quality?, test length?)
 - **Response verification**
- **Pseudorandom test**
 - very long tests?
- **Hybrid test solutions**
- **Response compression**



Course Work: Research Object

 

1. Design of a combinational circuit for the following functionality

If $x = 0, z = 0$, then $Y = k_1A + k_2B$, else

if $x = 0, z = 1$, then $Y = k_3A - k_1C$, else

if $x = 1, z = 0$, then

$$Y = (k_1A \vee k_1B \wedge k_2C) \oplus (k_3C \vee \text{NOT}(k_3A) \wedge k_1B),$$

else


if $x = 1, z = 1$, then $Y = k_4A^2 + k_5A + k_6$

Coefficients k_i can be found on the next slide

Course Work: Versions of Research Object


Vers. No.	k ₁	k ₂	k ₃	k ₄	k ₅	k ₆	Vers no.	k ₁	k ₂	k ₃	k ₄	k ₅	k ₆
1	1	1	1	0,1	0,2	0,5	8	1	1	1	1,5	0,1	0,5
2	1	1	0	0,1	0,2	1,0	9	1	1	0	1,5	0,1	1,0
3	1	0	1	0,1	0,2	2,0	10	1	0	1	1,5	0,4	2,0
4	1	0	0	0,1	0,2	3,0	11	1	0	0	1,5	0,4	3,0
5	0	1	1	0,1	1,0	0,5	12	0	1	1	1,5	0,8	0,5
6	0	1	0	0,1	1,0	1,0	13	0	1	0	1,5	0,8	1,0
7	0	0	1	0,1	2,0	2,0	14	0	0	1	1,5	1,5	2,0
15	1	1	1	0,2	0,4	1,0	20	0	0	1	0,5	0,4	1,0
16	1	1	1	0,1	0,4	1,2	21	0	0	1	1,0	0,8	1,5
17	1	1	0	0,2	0,4	0,5	22	0	1	1	0,5	1,2	0,5
18	1	0	1	0,2	0,4	1,0	23	0	1	1	1,0	0,3	1,0
19	0	0	1	0,3	2,0	1,0	24	1	0	1	0,4	1,0	1,5

Course Work: Design of Interface

 

2. Design of the experimental bench. Use three different interface versions for experiments: 1 bit, 2-bit and 4- or more bit interfaces for respective n-bit Signature Analyzers

The types of interface:

 


Course Work: Design of a Testable Circuit

 3. Enter the designed gate-level (AND, OR, NOT) circuit into the computer by CADENCE circuit editor
4. Testability analysis. Generate test patterns with Turbo-Tester (TT) ATPG to achieve the fault coverage as close to 100% as possible

Course Work: Design of a Test Generator

**BILBO - Built- In Logic
Block Observer:**



7. Generate test patterns by the BILBO tool for 10 different **polynomials**, and find the best structure for the LFSR

Choose 5 primitive, and 5 non-primitive polynomials


Report for all 10 experiments

- a) the maximum achievable fault coverage, and
- b) fix the minimum test length needed for that

Calculate the increase of the circuit size
(in number of 2-input gates)
due to adding of self-test circuitry


Course Work: Design of a Test Generator

CSTP - Circular Self-Test Path:

 

 8. Repeat the previous task for the case of using CSTP ("Circular Self Test Path")

Course Work: Design of a Response Analyzer



9. Carry out experiments with the test sets found in tasks 4 and 7

for 4 Signature Analyzers (SA):
1-bit, 2-bit, 4-bit, and 8-bit

Calculate the fault coverages for both tests


Draw the graphics $P = f(SA)$

P – is the fault coverage and
SA – is the number of bits in the Signature Analyzer

Draw 4 graphics $P = f(T)$ for 4 SAs

T (test length) – changes from 0% to 100% of fault coverage

 Explain the graphics (dependence on two factors: test quality $P = f(T)$, and response analysis quality $P = f(SA)$)



Course Work: Store-and-Generate BIST

- 11. Compare the results in tasks 4, 7, and 8. Which solution is the best and why?**
- 12. Present the results of experiments**